


**Part I. Lecture Multiple Choice (43 points total)**

1. (5 pts.) The voltage between the cathode and the screen of a television set is 22 kV. If we assume a speed of zero for an electron as it leaves the cathode, what is its speed just before it hits the screen? ( $m_e = 9.1 \times 10^{-31}$  kg;  $q_e = 1.6 \times 10^{-19}$  C)

- A.  $8.8 \times 10^7$  m/s
- B.  $2.8 \times 10^6$  m/s
- C.  $6.2 \times 10^7$  m/s
- D.  $7.7 \times 10^{15}$  m/s
- E.  $5.3 \times 10^7$  m/s


2. (3 pts.) Which points in the diagram are at the same potential?

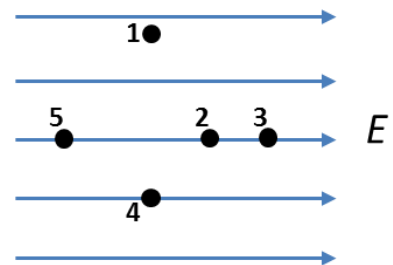- A. 2 and 5
- B. 2, 3, and 5
- C. 2 and 4
- D. 1 and 5
- E. 1 and 4



3. (5 pts.) You assemble the system of point charges  $q_1 = 1 \mu\text{C}$ ,  $q_2 = 2 \mu\text{C}$ , and  $q_3 = 3 \mu\text{C}$  at the corners of an equilateral triangle whose side  $s = 30$  cm. What is the electrostatic potential energy of the system? (assume  $U = 0$  at infinity)

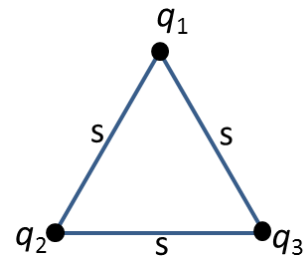- A. 1.10 J
- B. 0.990 J
- C. 0.631 J
- D. 0.330 J
- E. 0.123 J




4. (4 pts.) A parallel plate capacitor filled with air is connected to a battery. When a dielectric is inserted between the plates of the capacitor

- A. only the capacitance changes.
- B. only the voltage across the capacitor changes.
- C. only the charge on the capacitor changes.
- D. both the capacitance and the voltage change.
- E. both the capacitance and the charge change.

**Diagram pertains to the next two questions:**

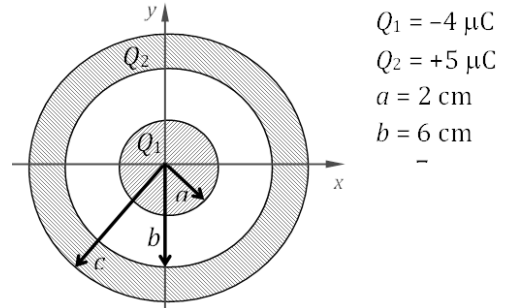A solid conducting sphere of radius  $a$  is centered on the origin, and carries a total charge  $Q_1$ . Concentric with this sphere is a conducting spherical shell of inner radius  $b$  and outer radius  $c$ , which carries a total charge  $Q_2$ . The value of parameters are given in the figure.



5. (5 pts.) Calculate the magnitude of the electric potential difference between the radius  $r = b$  (the inner surface of the conducting shell) and the origin.


- A.  $|V_b - V_0| = 1.50 \times 10^5 \text{ V}$
- B.  $|V_b - V_0| = 4.50 \times 10^5 \text{ V}$
- C.  $|V_b - V_0| = 6.00 \times 10^5 \text{ V}$
- D.  $|V_b - V_0| = 12.0 \times 10^5 \text{ V}$
- E.  $|V_b - V_0| = 18.0 \times 10^5 \text{ V}$

6. (3 pts.) If the inner conducting sphere were replaced with an insulating sphere having the same total charge  $Q_1$  distributed uniformly throughout its volume, the magnitude of the potential difference  $|V_b - V_0|$  would

- A. increase
- B. decrease
- C. stay the same


7. (5 pts.) All four capacitors have equal values of  $50 \mu\text{F}$ . Calculate the equivalent capacitance of this network of capacitors.

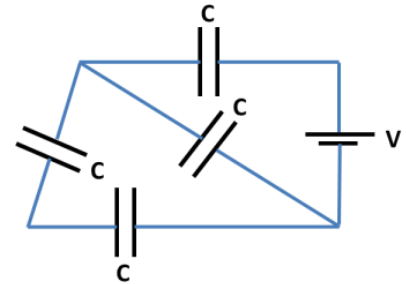- A.  $50 \mu\text{F}$
- B.  $30 \mu\text{F}$
- C.  $75 \mu\text{F}$
- D.  $100 \mu\text{F}$
- E.  $83 \mu\text{F}$



8. (5 pts.) A current of  $1.2 \text{ A}$  flows from A to B. Therefore, the magnitude of the potential difference between points A and B is approximately

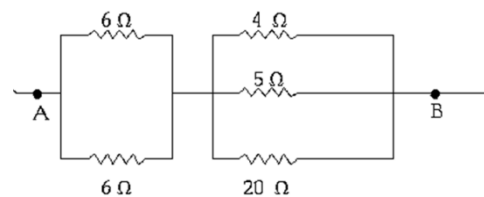
- A.  $1.0 \text{ V}$
- B.  $4.2 \text{ V}$
- C.  $4.6 \text{ V}$
- D.  $6.0 \text{ V}$
- E.  $20 \text{ V}$



Name \_\_\_\_\_  
*last* *first*

Student ID Number \_\_\_\_\_

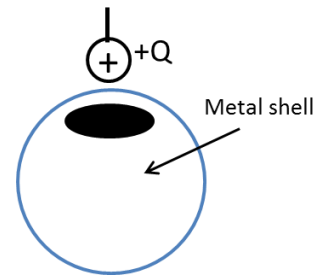
9. (4 pts) A metal ball of charge  $+Q$  is lowered into an uncharged metal shell and allowed to rest on the bottom of the shell. When the charges reach equilibrium,



- A. the outside of the shell has a charge of  $-Q$  and the ball has a charge of  $+Q$ .
- B. the outside of the shell has a charge of  $+Q$  and the ball has a charge of  $+Q$ .
- C. the outside of the shell has a charge of zero and the ball has a charge of  $+Q$ .
- D. the outside of the shell has a charge of  $+Q$  and the ball has zero charge.
- E. the outside of the shell has a charge of  $+Q$  and the ball has a charge of  $-Q$ .

10. (4 pts) Parallel plate capacitor  $C_1$  has plate area  $A$  and separation distance  $d$ . Capacitor  $C_2$  is made by starting with  $C_1$  and first reducing the plate separation to  $d/2$ . Next, a dielectric with  $\kappa=3$  and plate area  $A/2$  is inserted into the middle, as shown. What is  $C_2$  in terms of  $C_1$ ?

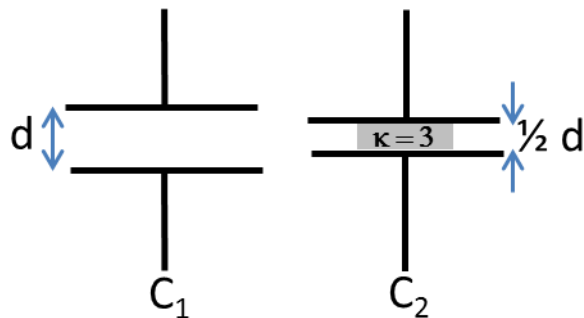
- A.  $C_2 = C_1 / 4$
- B.  $C_2 = C_1$
- C.  $C_2 = 2 C_1$
- D.  $C_2 = 3 C_1$
- E.  $C_2 = 4 C_1$



**II. Lab questions [12 pts]**



For problems 10–12, assume that the battery and ammeter are ideal and that all bulbs are identical.

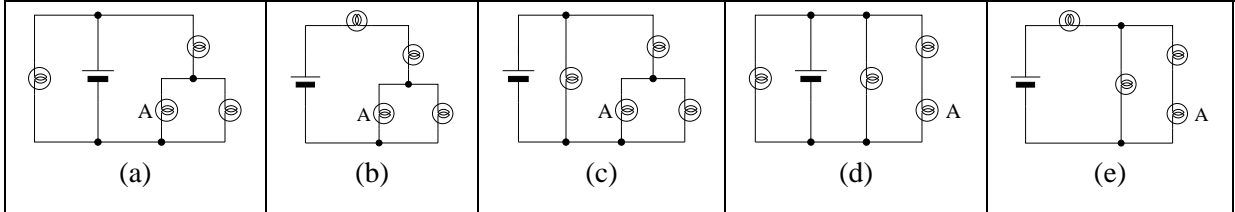11. [4 pts] In which circuit below is bulb A **brightest**?



12. [4 pts] In which circuit **above** is the **power delivered by the battery** the **lowest**?

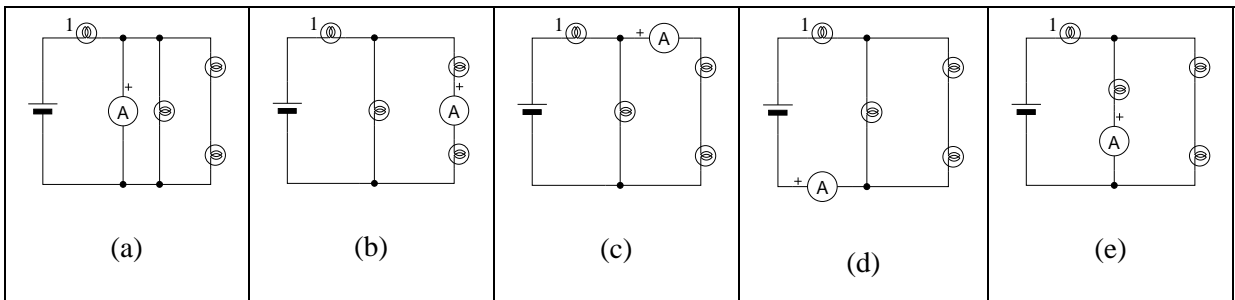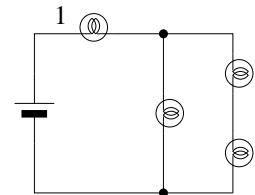13. [4 pts] An ammeter is to be **added to the circuit at right** in order to measure the current through the bulb labeled 1. Which placement of the ammeter will **correctly** measure the current through bulb 1?




Name \_\_\_\_\_ Student ID Number \_\_\_\_\_  
*last first*

**The next four problems are related.**

**Kirchhoff Laws.** Study the circuit and answer the following questions.

X. (3 pts) Use the Kirchhoff Current Law to relate the three currents at **point P**.

P:

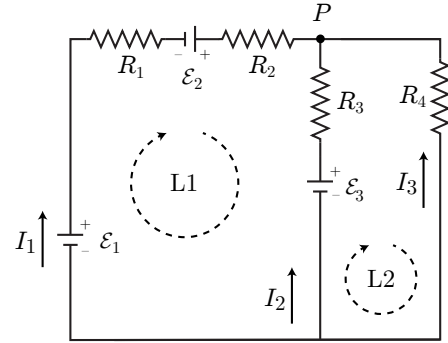

X. (6 pts) Use the Kirchhoff Voltage Law to write equations for the sum of the **voltage drops** around loops L1 and L2. Express all equations in terms of the parameters defined in the figure above.

L1:


L2:

X. (9 pts) Assume that all emf sources supply 5 V and all resistors have a resistance of 100 Ohms.  $I_1$  is found to be 0.03 A. What are the remaining currents? (Show your work and put your final answers in the provided box.)

	$I_2$	$I_3$
(Amps)		

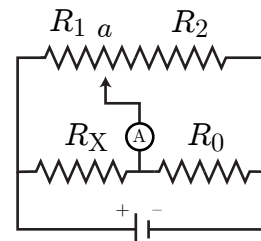X. (7 pts) **Wheatstone Bridge: Measuring the resistance.**

The variable resistor is adjusted by moving the contact position  $a$ .  $a$  is the position relative to the total length of the resistor such that the resistance from the LHS of the resistor to the contact point is  $R_1 = a R_{Tot}$  and resistance from the contact point to the RHS of the resistor is  $R_2 = (1-a) R_{Tot}$ .



The contact position  $a$  is varied until there is **no current** flowing through the ammeter (A). What is the resistance of  $R_X$  as a function of  $R_0$ ,  $a$ , and  $R_{Tot}$ ?