


# More capacitors

Lecture 10

# Review: Capacitance

- **Capacitance:** Capacity (or efficiency) of conductor to hold charge at a potential difference.

$$Q = CV$$


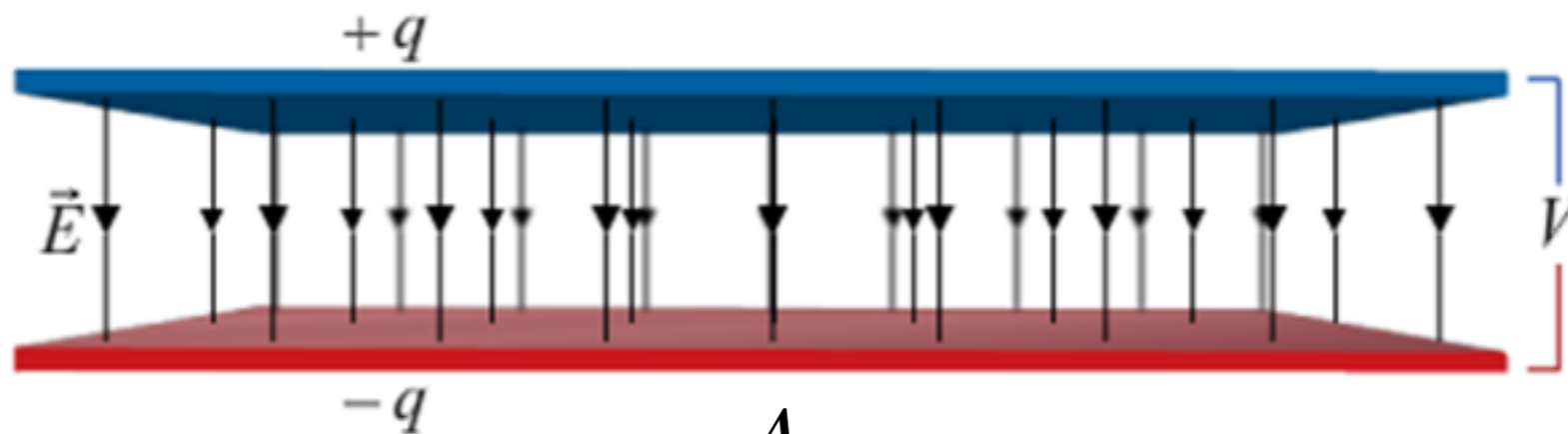


$$C = \frac{A\epsilon_0}{d}$$


- Units: Farad = C/V.
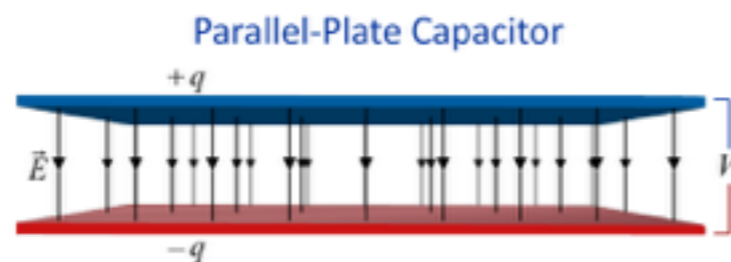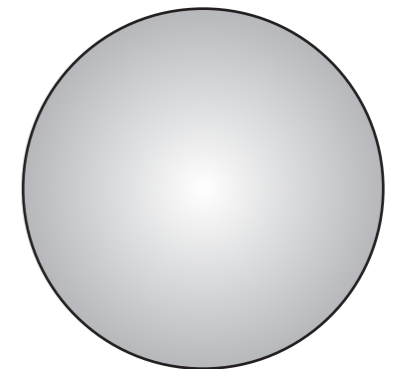
# Capacitors


- Not just planes...  
spheres, cylinders, plates,  
isolated conductor...



Spherical Capacitor

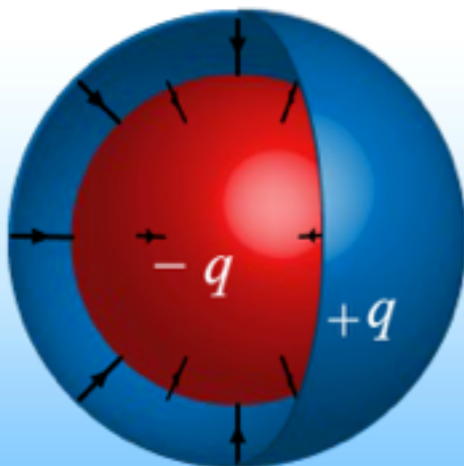


Cylindrical Capacitor

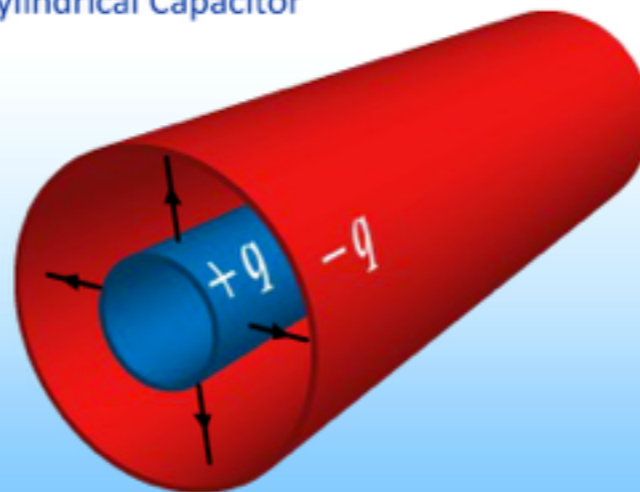

**Capacitance**  
depends only  
on geometry  
(not charge).

# Concentric Spheres

Spherical Capacitor

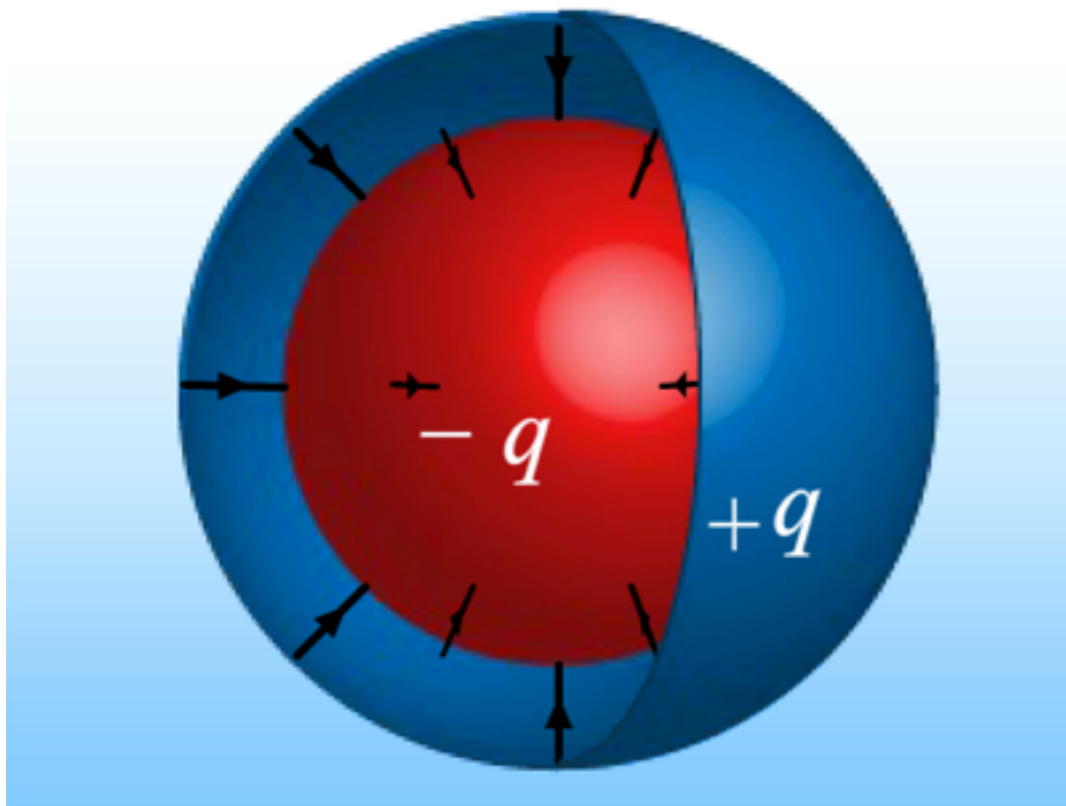

$$Q = CV$$


on overhead...

$$C = \frac{4\pi R_1 R_2 \epsilon_0}{R_1 - R_2}$$

limit?

# Concentric Cylinders

Cylindrical Capacitor

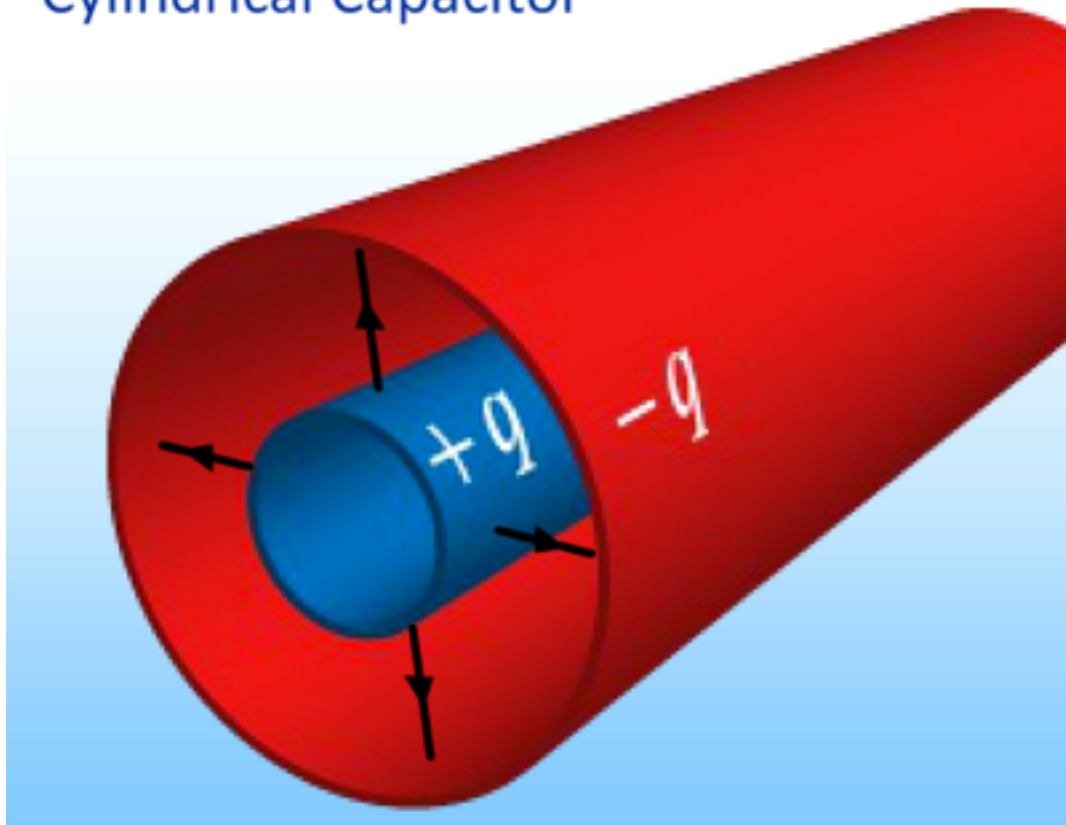


$$Q = CV$$

on overhead...

$$C = \frac{2\pi L\epsilon_0}{\log R_1/R_2}$$

limit?

# FlipIt Physics

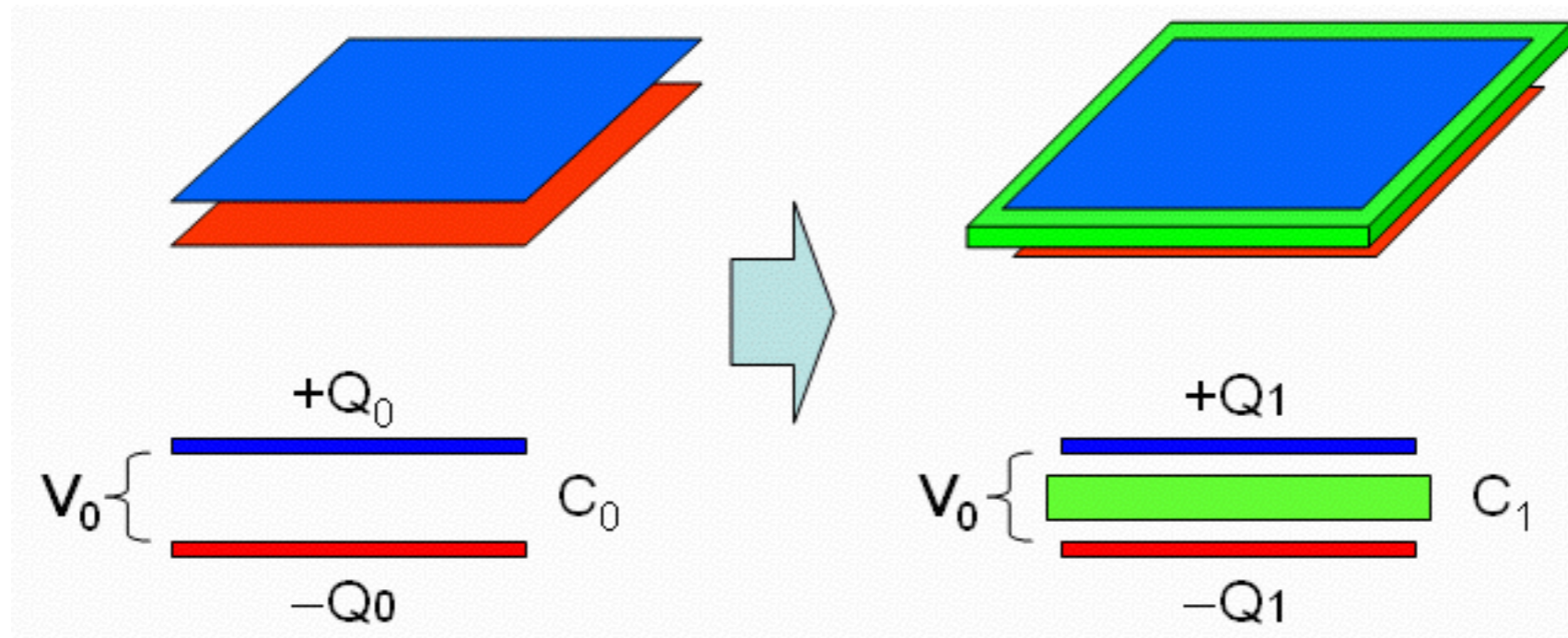


1) Compare  $Q_1$  and  $Q_0$ .

- $Q_1 < Q_0$
- $Q_1 = Q_0$
- $Q_1 > Q_0$

Submit

Graph

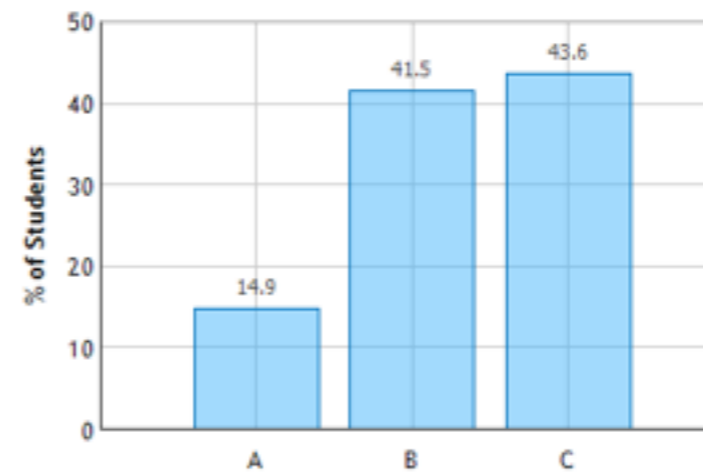Charged Parallel Plates: Question 1 (N = 94)




# Energy is stored in the **E field**

- How do we think about Electric Potential Energy?
  - **Work** required to build **charge distribution**
  - ... but where is the energy stored?
  - in the **Electric Field**
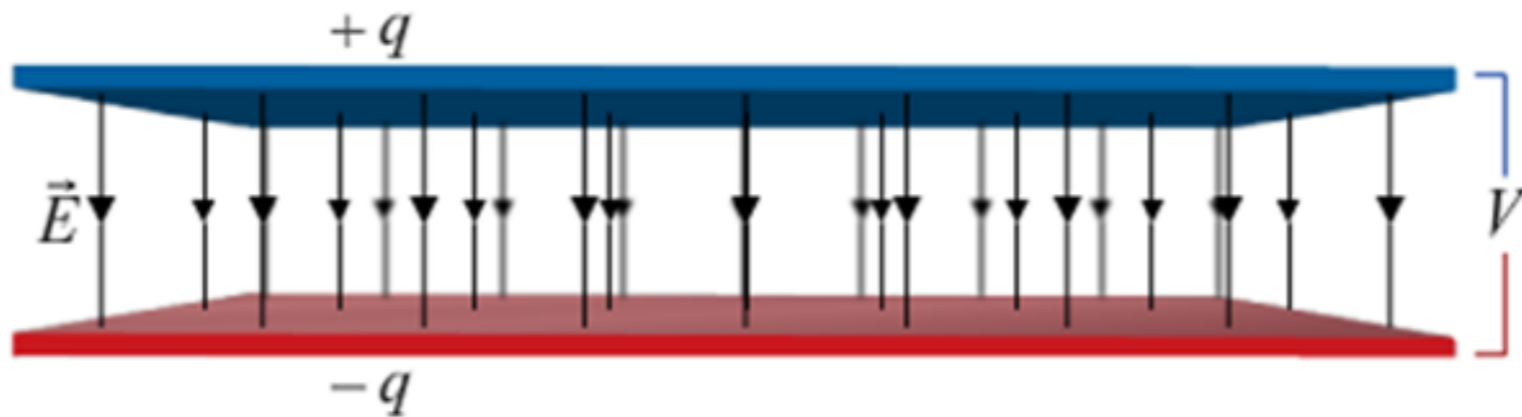
# Energy is stored in the **E** field

- Use a capacitor to compute the energy...




- **E is constant** inside capacitor so it will be easy to deduce the dependence on  $E$

(overhead)


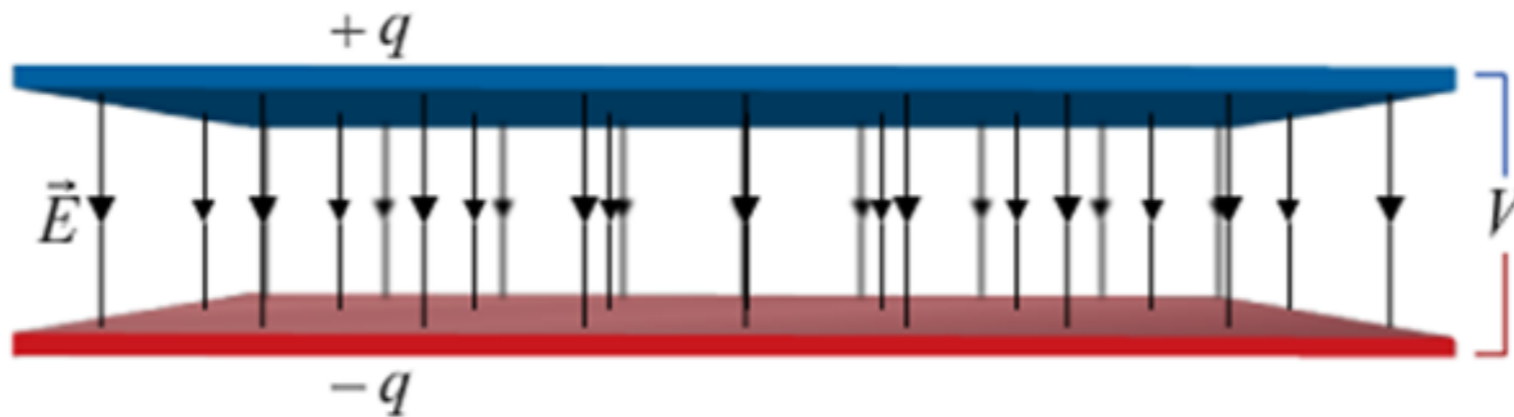
# Energy is stored in the **E** field

- Use a capacitor to compute the energy...




- **E is constant** inside capacitor so it will be easy to deduce the dependence on E

(overhead)

$$u = \frac{1}{2} \epsilon_0 E^2$$

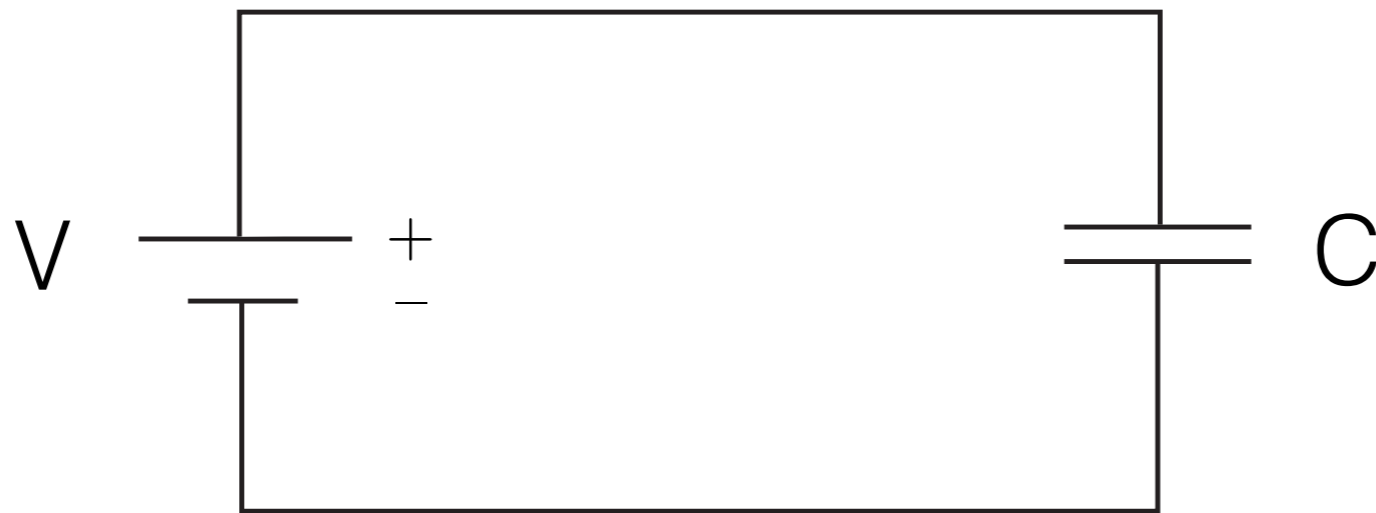
# Capacitors in circuits

- Circuit Diagram:
  - Voltage Supply/Battery
  - Capacitor
  - ... More symbols later ...



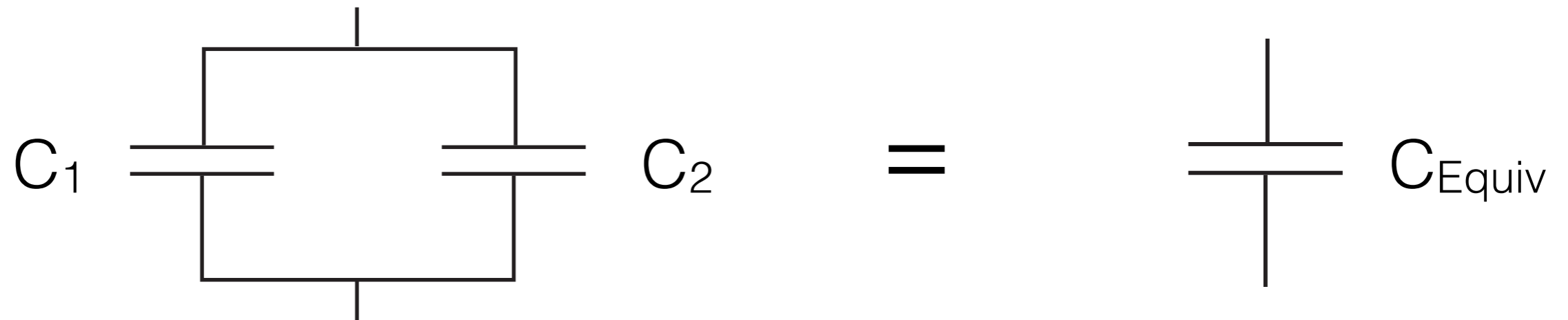
# Parallel vs Series


- **Parallel** configuration of capacitors:



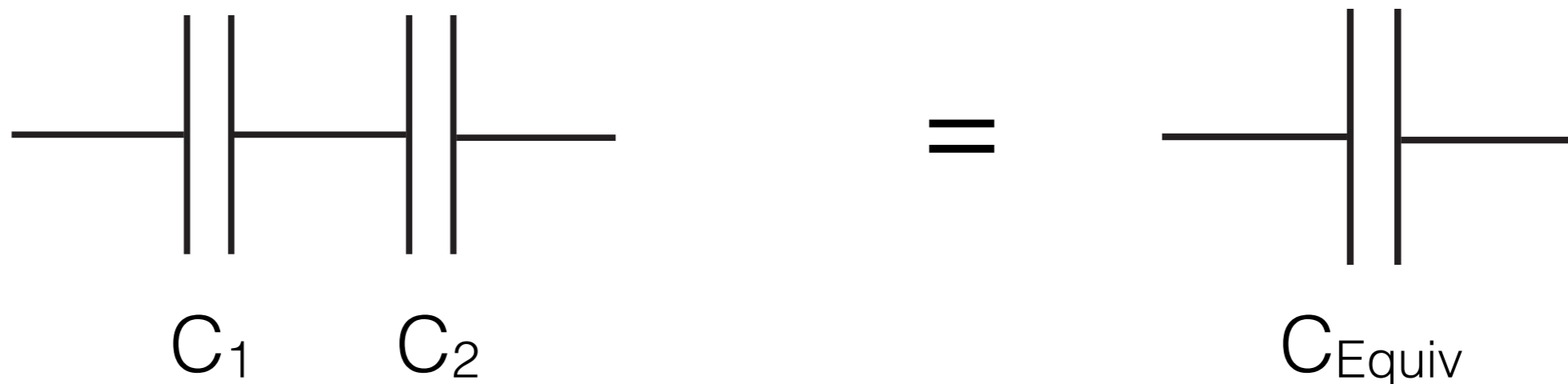- **Series** configuration of capacitors:


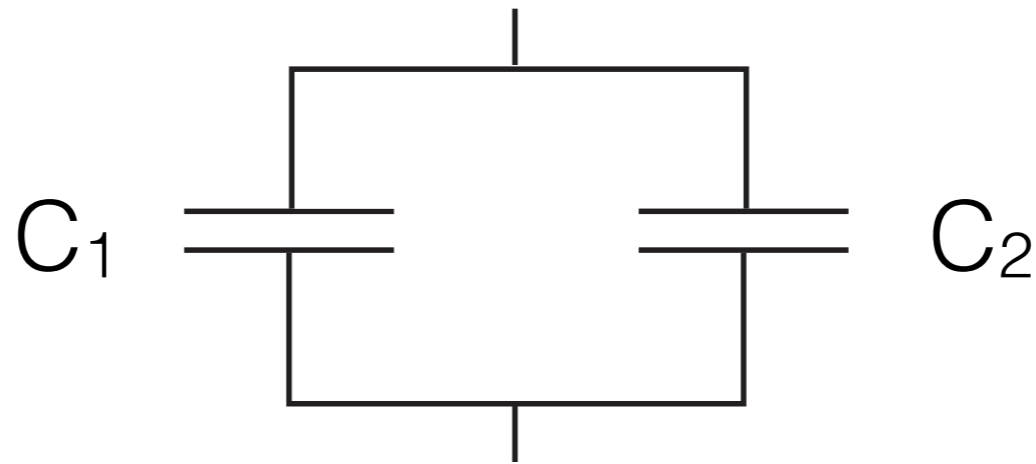
# Equivalent Capacitance for **Parallel Capacitors**



(overhead)


(~ Springs in parallel.)

$$C_{\text{Equiv}} = C_1 + C_2 = \sum_i C_i$$
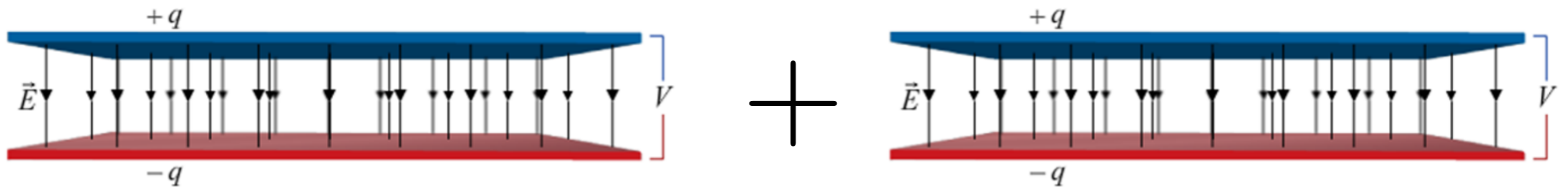
# Equivalent Capacitance for Parallel Capacitors


$$C_{\text{Equiv}} = C_1 + C_2 = \sum_i C_i$$

- Intuitive explanation:  $C = \frac{A\epsilon_0}{d}$



- **Areas** just **add** therefore so does capacitance!
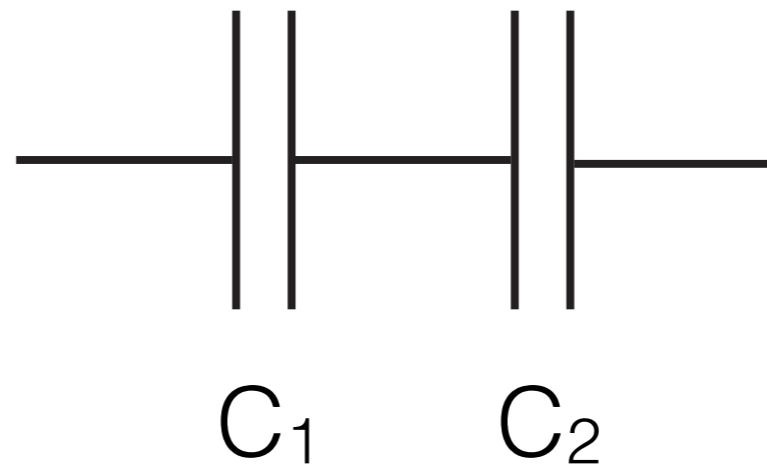
# Equivalent Capacitance for **Series Capacitors**



(overhead)

(~ Springs in series.)


$$C_{\text{Equiv}}^{-1} = C_1^{-1} + C_2^{-1} = \sum_i C_i^{-1}$$

# Equivalent Capacitance for Series Capacitors

$$C_{\text{Equiv}} = C_1 + C_2 = \sum_i C_i$$

- Intuitive explanation:

$$C = \frac{A\epsilon_0}{d}$$

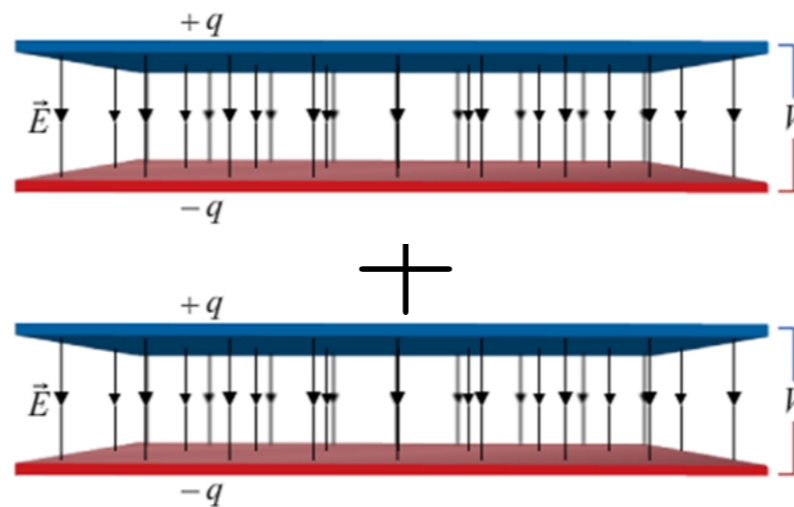

Conductor sandwich!

- **Distances** just **add** therefore so does inverse capacitance!