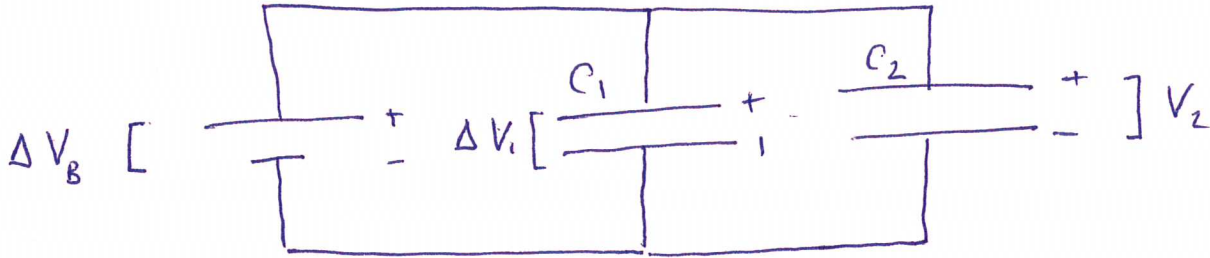


Capacitors in Parallel




$$\Delta V_B = \Delta V_1 = \Delta V_2 = \Delta V$$

$$Q_1 = C_1 \Delta V \quad Q_2 = C_2 \Delta V$$

$$Q_{TOT} = Q_1 + Q_2 = (C_1 + C_2) \Delta V$$
$$= C_{Equiv} \Delta V$$


$$\boxed{C_{Equiv} = C_1 + C_2}$$

Capacitors in Series

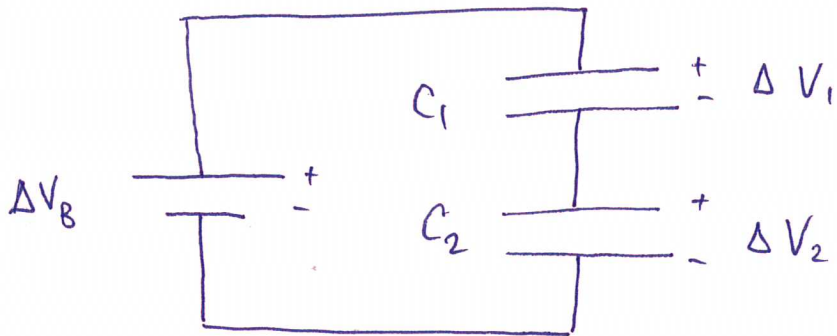

$$\Delta V_B = \Delta V_1 + \Delta V_2$$

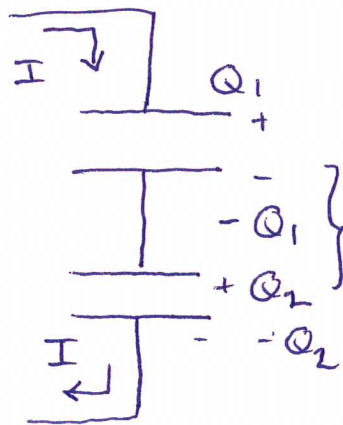But we assume $Q_1 + Q_2 = 0$ before circuit is charged. $\Rightarrow Q_1 = Q_2 = Q$



after charging

these must sum to 0!

$$\Delta V_B = \frac{Q}{C_1} + \frac{Q}{C_2} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) Q = \frac{Q}{C_{\text{equiv}}}$$

$$C_{\text{equiv}}^{-1} = C_1^{-1} + C_2^{-1}$$


Compute energy require to charge a capacitor

why isn't the answer

$$U = QV ?$$

depends on Q

easier

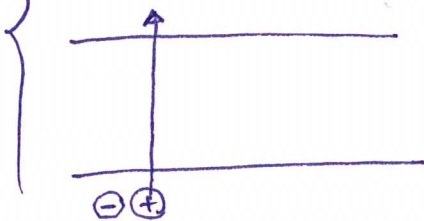

$$dU = V dQ$$

$$V = V(Q) !$$


$$V = \frac{Q}{C}$$

$$U_0 = \int_0^{U_0} dU = \int_0^{Q_0} dQ \frac{Q}{C} = \frac{1}{2} \frac{Q_0^2}{C}$$

$$= \frac{1}{2} C V_0^2 = \frac{\epsilon_0 A}{2d} (dE)^2$$

$$= \frac{1}{2} \epsilon_0 (Ad) E^2$$

Volume between plates.

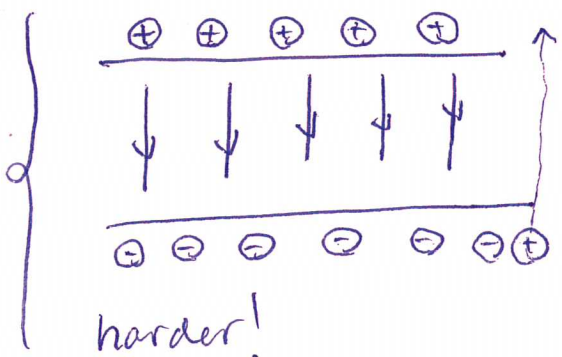


harder!

$$\Rightarrow U = \int d^3x \frac{1}{2} \epsilon_0 E^2$$

Energy Density energy density.

$$u \equiv \frac{1}{2} \epsilon_0 E^2$$

Capacitance of a Cylindrical Capacitor

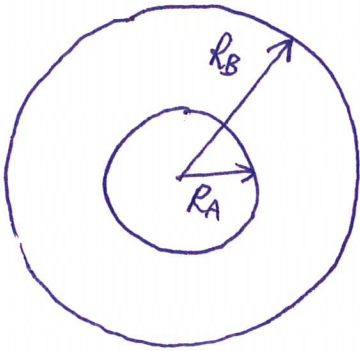

$$\vec{E} = (-\hat{r}) \frac{Q}{L} \frac{1}{2\pi\epsilon_0 r}$$

$$\Delta V = - \int_{R_A}^{R_B} dr \hat{r} \cdot (-\hat{r}) \frac{Q}{L} \frac{1}{2\pi\epsilon_0 r}$$

$$= \frac{Q R_A \log \frac{R_B}{R_A}}{2\pi R_A L \epsilon_0}$$

$$\Delta V = \frac{Q}{2\pi\epsilon_0 L} \log \frac{R_B}{R_A}$$

$$C = \frac{2\pi L \epsilon_0}{\log \frac{R_B}{R_A}}$$

limit as $R_A \rightarrow R_B^- \Rightarrow R = \frac{1}{2}(R_B + R_A)$ $\delta R = R_B - R_A$

$$C = \frac{2\pi L R \epsilon_0}{R \log \frac{1 + \frac{\delta R}{2R}}{1 - \frac{\delta R}{2R}}} = \frac{A \epsilon_0}{R \left(\frac{\delta R}{R} \right)} = \frac{A \epsilon_0}{\delta R}$$