#### Kirchhoff Circuit Laws

Lecture 13

### Electromotive force

- **EMF**: Historical name for **voltage gain** in a battery
- Work done per unit charge to increase/decrease its potential

$$[\mathcal{E}] = \mathcal{V}$$

## One more analogy...



#### Power: Supplied and Dissipated

• Power supplied by a source of emf (voltage supply)

P = IV

• Power dissipated by a ohmic resistor (to heat):

$$P = IV = RI^2 = V^2/R$$

• Units: [Power] = J/s = Watts = W

#### Pre-lecture



• The 'real' batteries and the resistors in both cases illustrated above are identical. In which case is the voltage across the terminals of the battery closest to the ideal battery voltage VO?

#### Kirchhoff Laws:

• Current Rule: 
$$\sum I_{in} = \sum I_{out}$$

DH: "What goes in must come out."

• Voltage Rule:  $\sum \Delta V = 0$  around any loop

DH: "What goes up must come down."

• (Can be tricky to implement.)

Name	St	udent ID	Score
last	first		
For the next <b>th</b>	ree questions consider the	following	

experiment: All capacitors start uncharged. Capacitor 1 with capacitance  $C_1$  is charged to *V* using a battery. Once capacitor 1 is charged, it is disconnected from the battery and then used to charge capacitor 2 with capacitance  $C_2$ . (I.e. the switch is connected first to terminal A and then to terminal B.)



11. [2 points] When the switch is initially in the A position, what is the charge on capacitor 1?

**A.** 
$$Q_1 = C_1 V$$
, **B.**  $Q_1 = C_2 V$ , **C.**  $Q_1 = 0$ , **D.**  $Q_1 = (C_1 + C_2)V$ , **E.**  $Q_1 = \frac{C_1 C_2}{C_1 + C_2}V$ ,

12. [2 points] When the switch is in the B position, what is the total charge on both capacitors Q?

**A.** 
$$Q = C_1 V$$
, **B.**  $Q = C_2 V$ , **C.**  $Q = 0$ , **D.**  $Q = (C_1 + C_2)V$ , **E.**  $Q = \frac{C_1 C_2}{C_1 + C_2}V$ ,

# Solving Circuit Problems

- 1. Use equivalent resistance & re-order components
- 2. Define and draw current arrow in all wires
- Define and draw loops for voltage rule (covering all wires)
- Apply Kirchhoff Rules to generate equations (tricky)
- Solve algebraic equations for currents (time consuming)

Kirchhoff's Current Rule  $I_1 + I_2 = I_3$ 



