

# Kirchhoff Circuit Laws


Lecture 13

# Announcements


- Exam next Thursday
  - Covers material up to and including today's lecture
  - No RC circuit material
- At a conference on Monday (guest lecturer)
- Office Hours (for next week only)  
Wednesday 3-4 PM
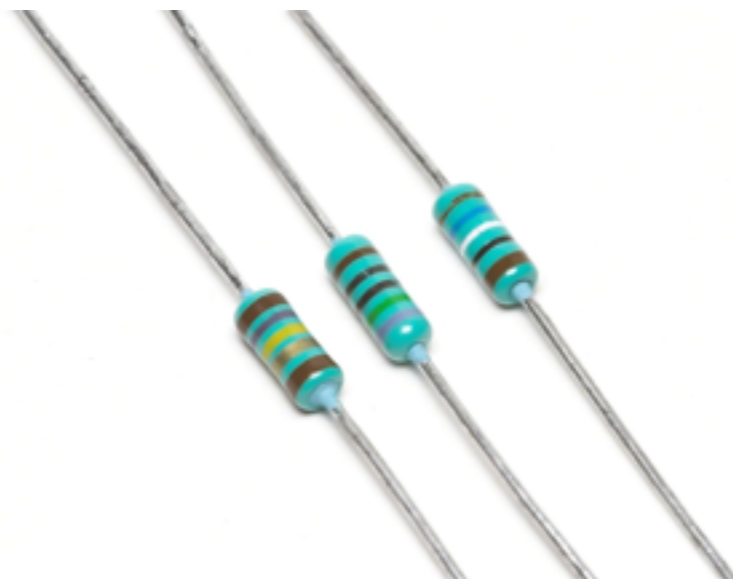
# Units


- $[I] = [\text{Current}] = [\text{Charge} / \text{Time}] = \text{C/s}$   
Ampere = A = Amp
- $[V] = [\text{Energy/Charge}] = \text{J/C} = \text{Volts} = \text{V}$
- $[R] = [\text{Resistance}] = \text{V/A} = \text{Ohms} = \Omega$



# One more analogy...

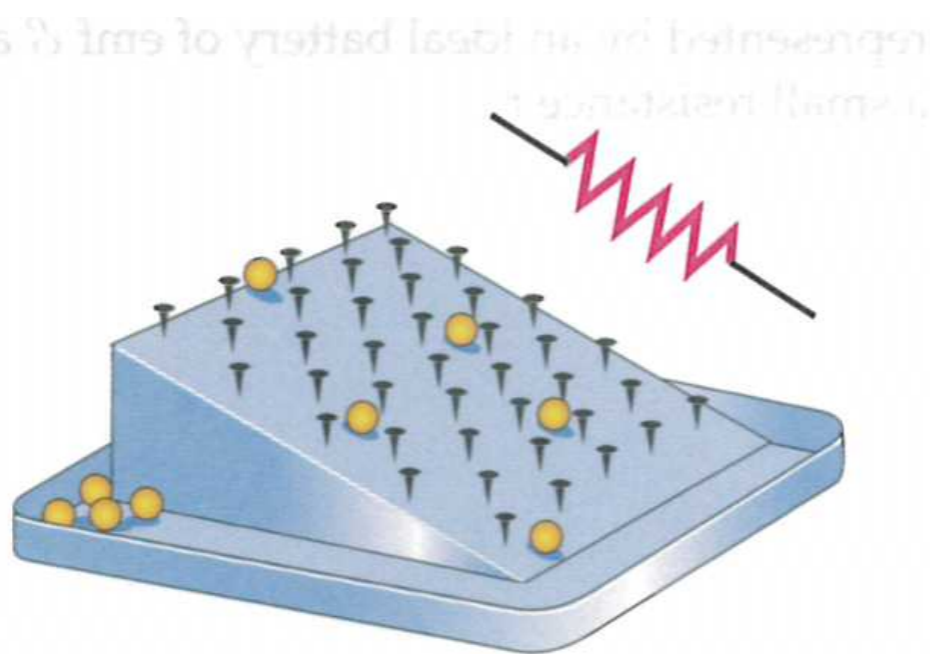

(a)

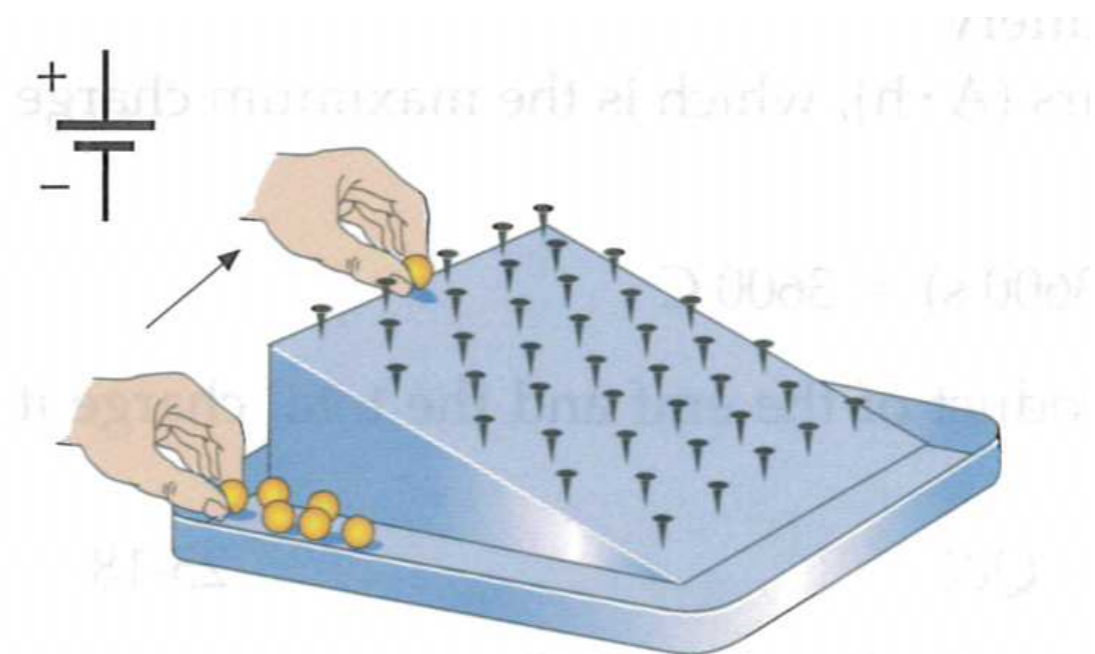

(b)

# Electromotive force

- **EMF**: Historical name for **voltage gain** in a battery
- Work done per unit charge to increase/decrease its potential

$$[\mathcal{E}] = \mathcal{V}$$

# Power: Supplied and Dissipated

- Power supplied by a source of emf (voltage supply)

$$P = IV$$

- Power dissipated by a ohmic resistor (to heat):

$$P = IV = RI^2 = V^2/R$$

- Units: [Power] = J/s = Watts = W

# Kirchhoff Laws:

- **Current Rule:**  $\sum I_{\text{in}} = \sum I_{\text{out}}$

DH: “What goes in must come out.”

- **Voltage Rule:**  $\sum \Delta V = 0$  around any loop

DH: “What goes up must come down.”

- (Can be tricky to implement.)

# Solving Circuit Problems

1. Use equivalent resistance & re-order components
2. Define and draw current arrow in all wires
3. Define and draw loops for voltage rule  
(covering all wires)
4. Apply Kirchhoff Rules to generate equations  
**(tricky)**
5. Solve algebraic equations for currents  
**(time consuming)**