RC Circuits!

Lecture 15

Exams will **not** be returned...

• Regrade of problem III.

FlipIt Lecture thoughts...

- "Everything looks good here, but it would have been nice to know this stuff before the lab this week, #5."—Oops.
- "Can you explain what a capacitor really is?"
- "How it is used in everyday life such as circuits?"

Behaves like a **short circuit** for small t and a **open circuit** at long t...



RC Demo

Charging: Overview of the action.





Charging: Overview of the action.



My capacitor heuristic:

- Small t (large v) →
 C is a short circuit
- Large t (small v) →
 C is an open circuit



Charging: Setting up the equations



Kirchhoff Voltage Law: $-V_b + IR + Q C = 0$

Aside: Does current really flow through a capacitor?



- Current through 3 surface
- The current through the gap is always 0!
- "Current through the capacitor"
 = change in Q on plates

Aside: Does current really flow through a capacitor?



"Current through the capacitor"
 = change in Q on plates

$$I = \frac{dQ}{dt}$$

Charging: Setting up the equations



Kirchhoff Voltage Law: $-V_b + R \frac{dQ}{dt} + Q/C = 0$

Initial State:

Q = 0

Charging: Solving the equations

Overhead.

Charging: Solution

RC time constant: $\tau \equiv RC$



Quick check of the units....

• RC time constant units:

 $[\tau] = [R][C] = [V][I]^{-1}[Q][V]^{-1} = [dQ/dt]^{-1}[Q] = s$

Discharging: Overview of the action.



RC

 \overrightarrow{RC}

Discharging: Setting up the equations



Kirchhoff Voltage Law:

$$RI + Q/C = 0$$

Initial State:

 $Q(0) = CV_b$

Discharging: Solution

RC time constant: $\tau \equiv RC$



Energy flow in an RC circuit.

- Power: P = IV
- Energy stored: $U = \frac{1}{2}CV^2$





$$P_{Battery}(t) = V_b I_o e^{-t/RC}$$

$$P_R(t) = R I_o^2 e^{-\frac{2t}{RC}}$$

$$P_{C}(t) = \left[\frac{q_{o}}{C}(1 - e^{-t/RC})\right] \left[I_{o}e^{-t/RC}\right]$$