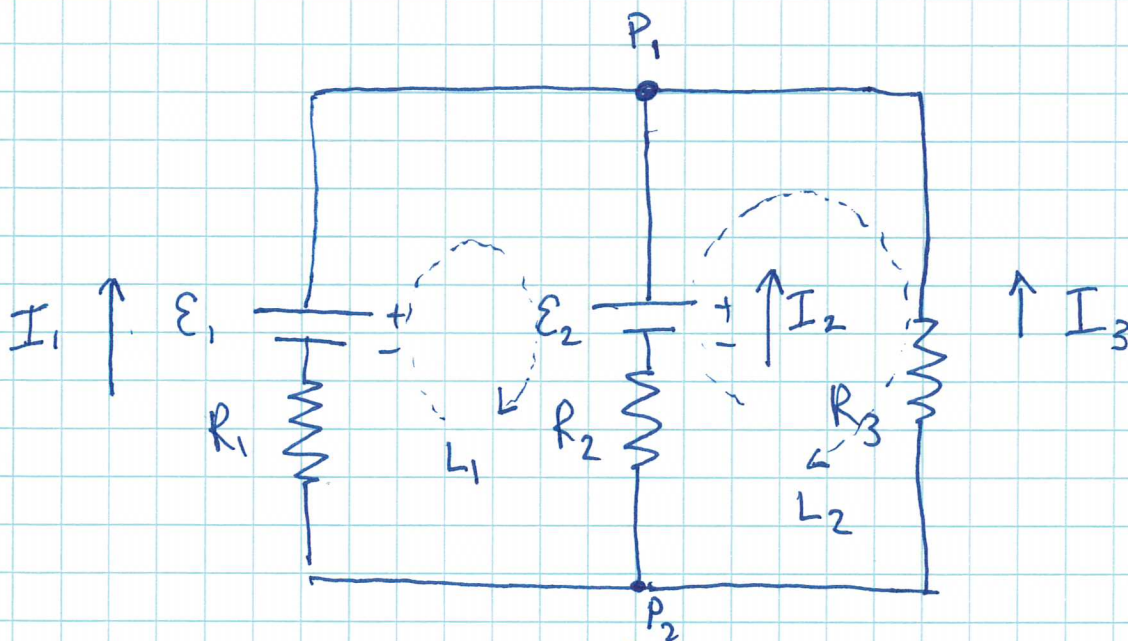
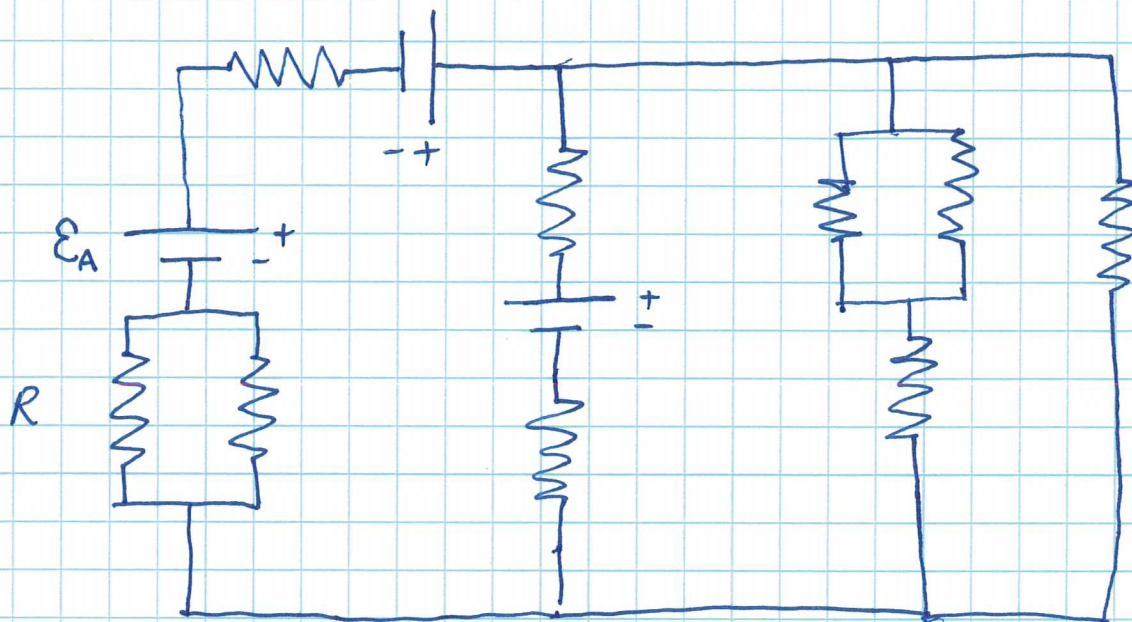




~~Voltage drop: $\oint dV = 0$~~

Kirchhoff Current Law:

$$I_1 + I_2 + I_3 = 0$$

Direction of current arrows matters.

@ Point P_i

Kirchoff Voltage Law:

Sum of voltage drops = 0.

Direction of current & Loop orientation both matter.

$$L_1: R_1 I_1 - \epsilon_1 + \epsilon_2 - R_2 I_2 = 0$$

↑
current arrow
aligned with
loop direction

signs
different
due to
orientation
versus

loop orientation.

current arrow
not aligned w/
loop direction

$$L_2: R_2 I_2 - \epsilon_2 - R_3 I_3 = 0$$

what happens if we add $L_1 + L_2$ Eqn's ?Solve: $I_3 = -I_1 - I_2 \rightarrow "L_2"$

$$R_2 I_2 - \epsilon_2 + R_3 I_1 + R_3 I_2 = 0$$

$$(R_2 + R_3) I_2 = \epsilon_2 - R_3 I_1$$

$$I_2 = \frac{1}{(R_2 + R_3)} \epsilon_2 - \frac{R_3}{R_2 + R_3} I_1 \rightarrow "L_1"$$

$$R_1 I_1 - \epsilon_1 + \epsilon_2 - \frac{R_2}{R_2 + R_3} \epsilon_2 + \frac{R_2 R_3}{R_2 + R_3} I_1 = 0$$

$$\left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right) I_1 = \epsilon_1 - \epsilon_2 \left(1 - \frac{R_2}{R_2 + R_3} \right)$$

$$I_1 = \frac{1}{\left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right)} \left[\epsilon_1 - \epsilon_2 \left(1 - \frac{R_2}{R_2 + R_3} \right) \right]$$

(3)

all resistors are 1Ω and $\mathcal{E}_1 = 10V$ $\mathcal{E}_2 = 5V$.

$$I_1 = \left(\frac{1}{1 + \frac{1}{2}} \right) \frac{5V}{\Omega} \left[2 - \left(1 - \frac{1}{2} \right) \right]$$

$$= A \left(\frac{2}{2} \right) 5 \left(\frac{3}{2} \right) = 5A$$

$$I_2 = \frac{1}{2\Omega} 5V - \frac{1\Omega}{2\Omega} 5A = 0A$$

$$I_3 = -5A.$$