

RC Circuits!



Lecture 15

Announcements


- Exam on Thursday.
 - Check the website
 - Practice exam & solutions
 - Seating chart
 - Study hard!

RC Demo

Charging: Overview of the action.

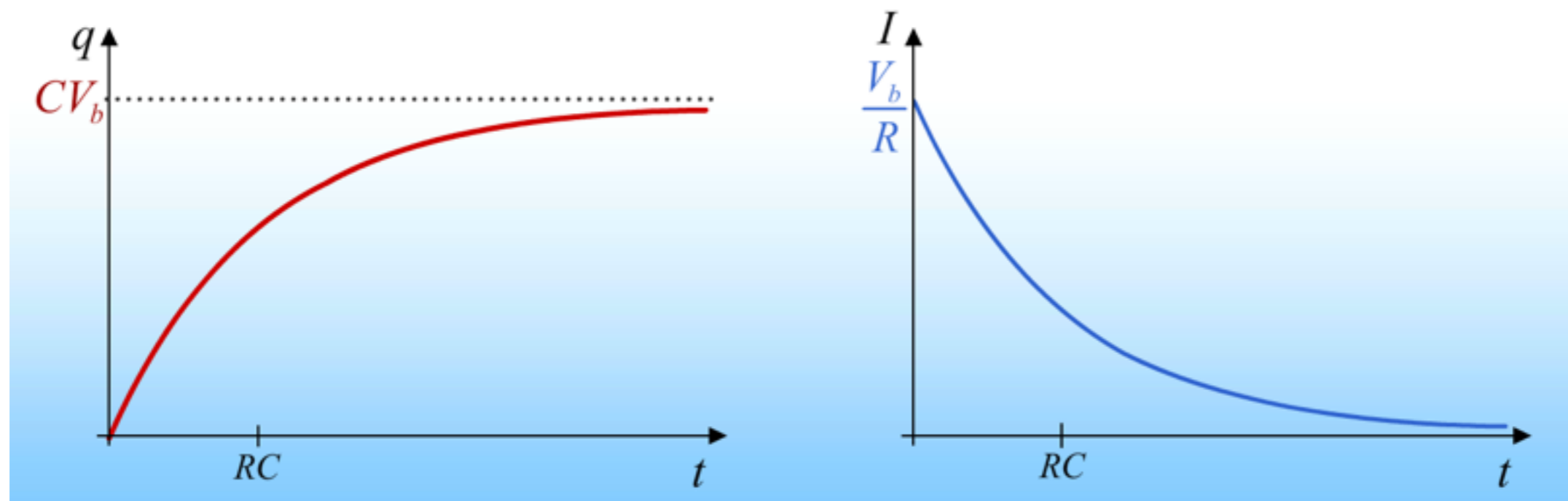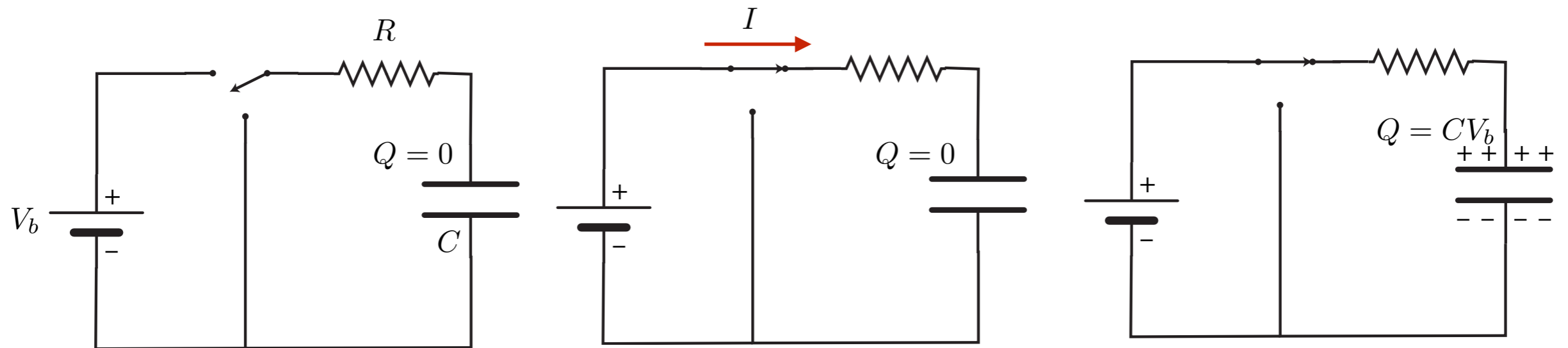


Charging: Overview of the action.

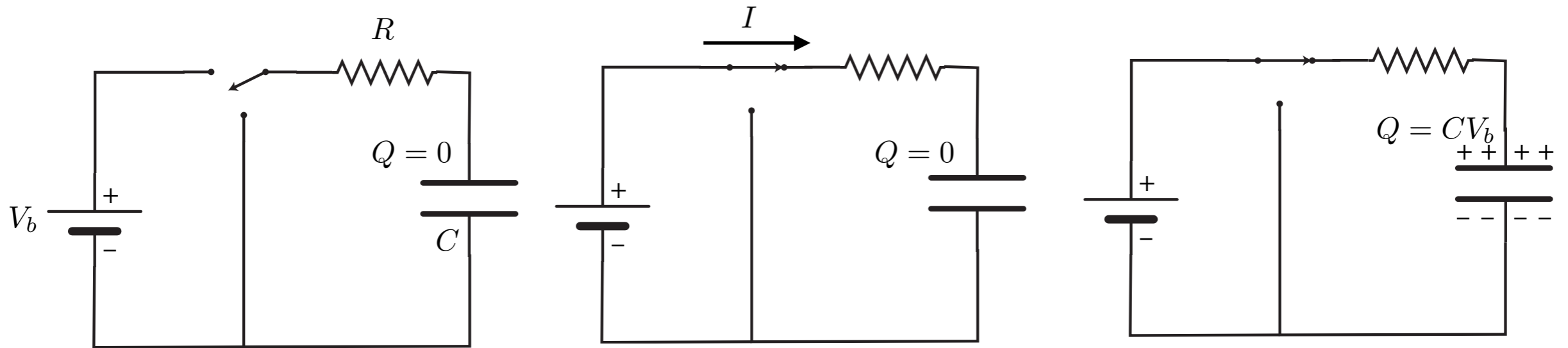


My capacitor heuristic:

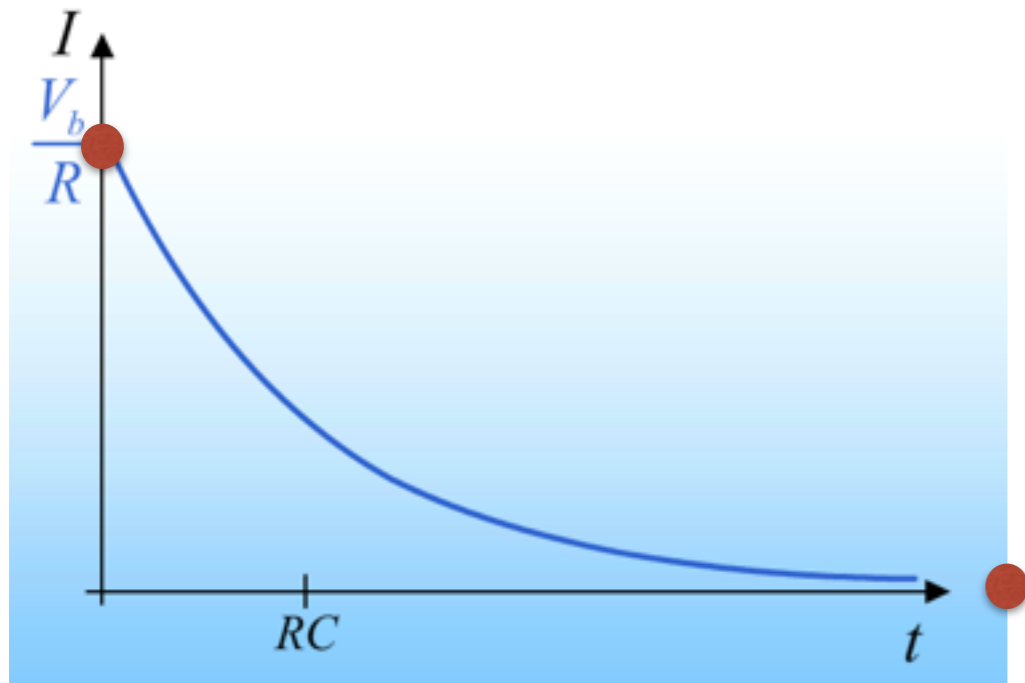- Small t (large v) \rightarrow
C is a short circuit
- Large t (small v) \rightarrow
C is an open circuit





Charging: Setting up the equations

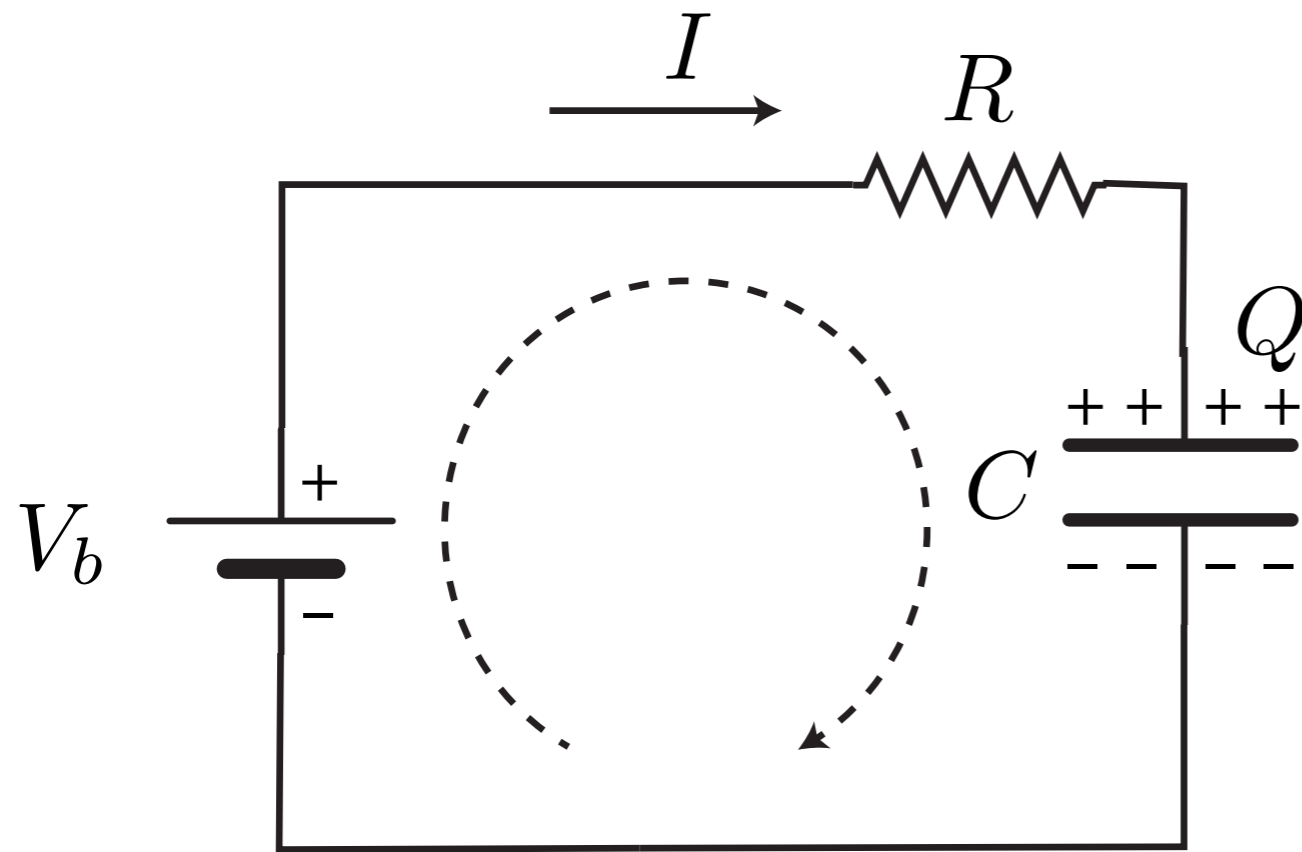


Kirchhoff Voltage Law:

$$-V_b + IR + Q/C = 0$$

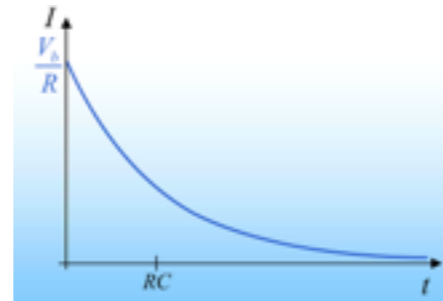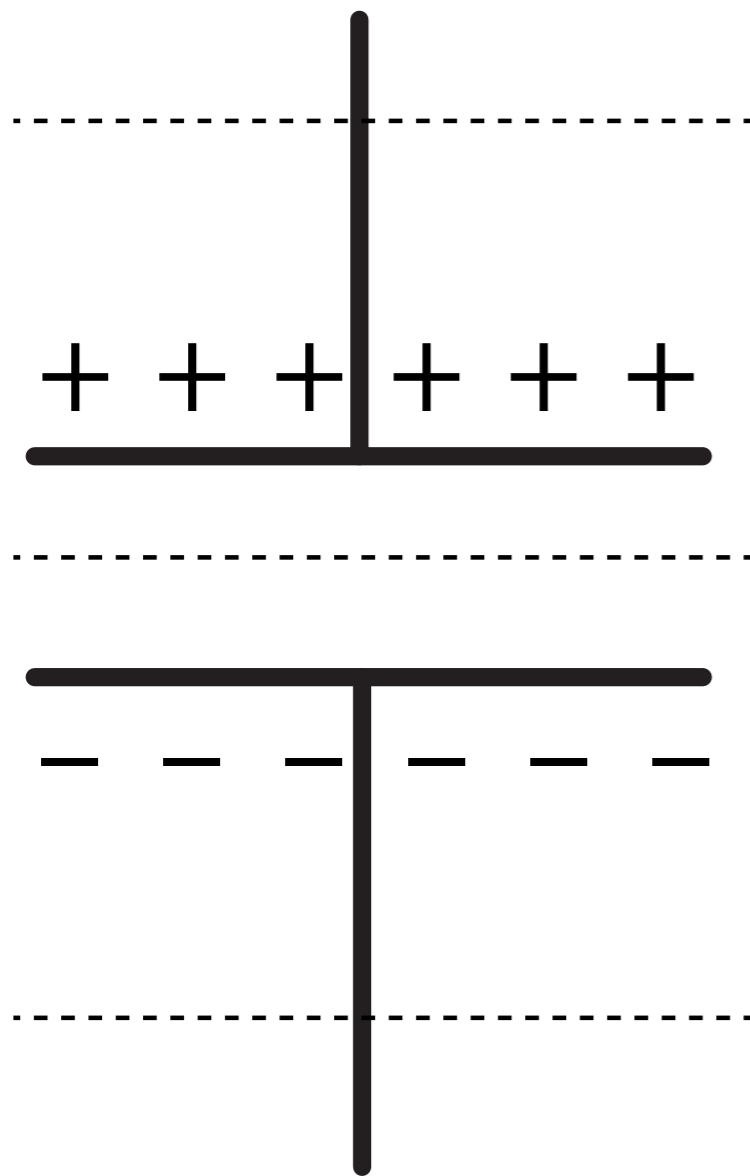Aside: Does current really flow through a capacitor?





$$I(t) = 0$$

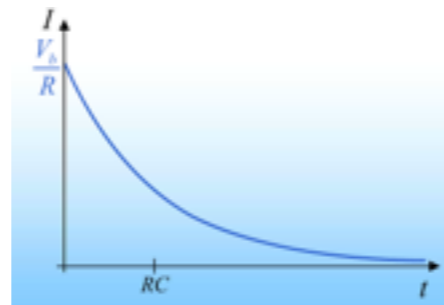


- Current through 3 surface
- The current through the gap is always 0!
- “Current through the capacitor” = change in Q on plates

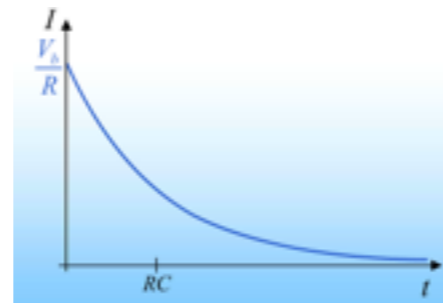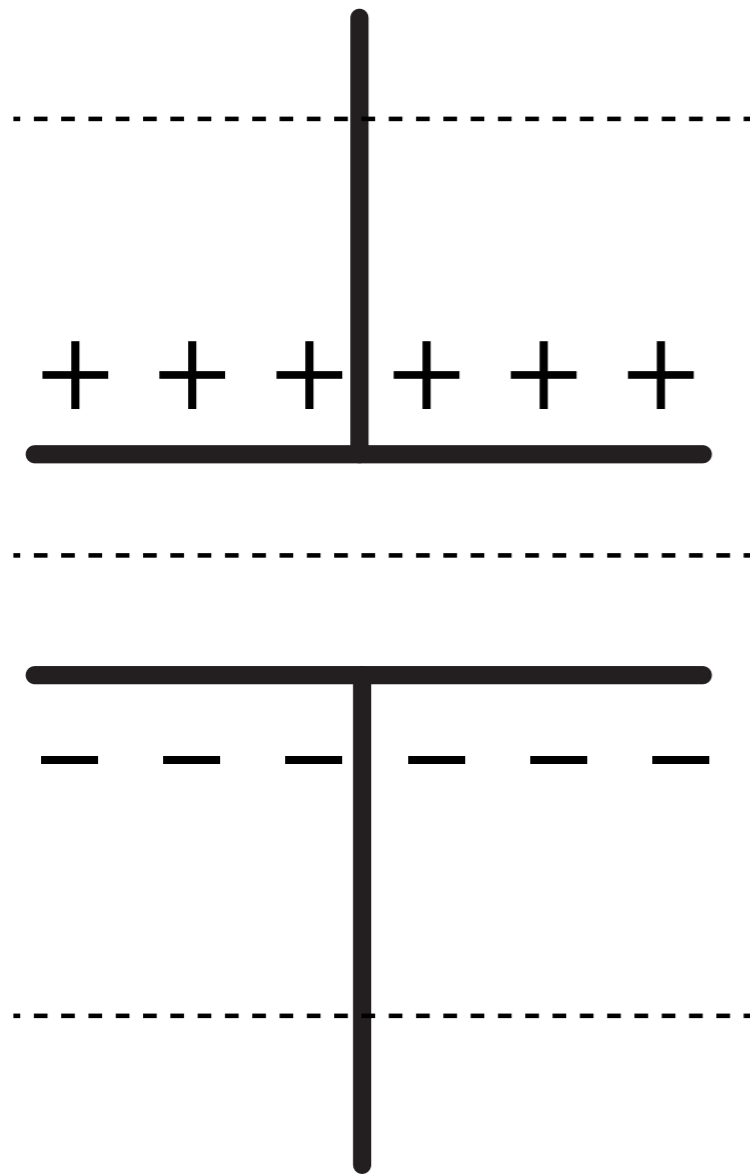Aside: Does current really flow through a capacitor?




- “Current through the capacitor”
= change in Q on plates

$$I(t) = 0$$

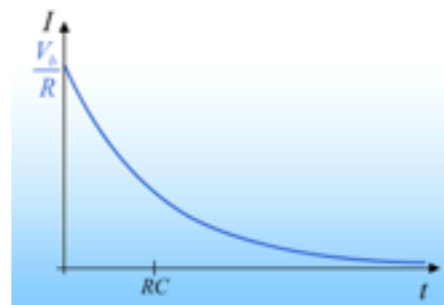

$$I = \frac{dQ}{dt}$$

Charging: Setting up the equations

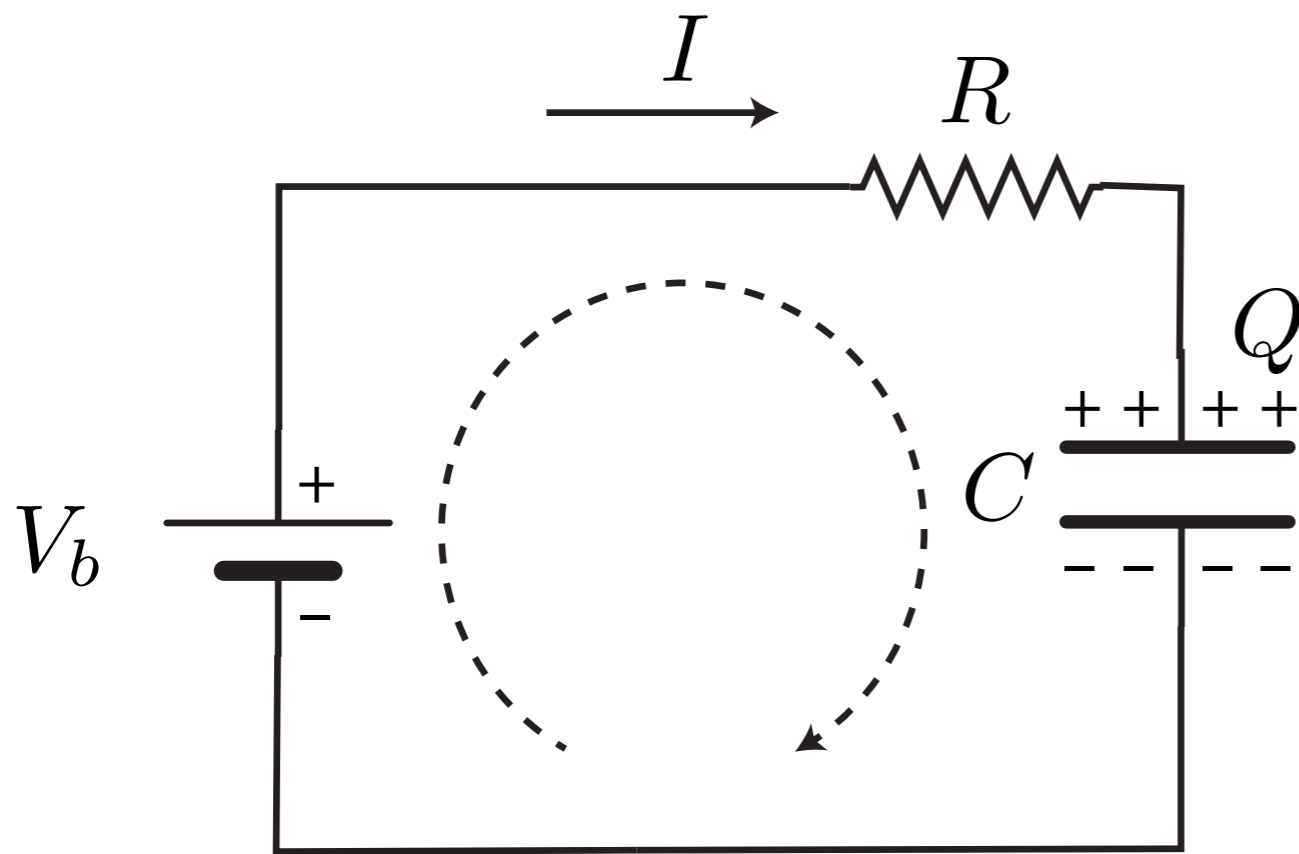

Kirchhoff Voltage Law:

$$-V_b + R \frac{dQ}{dt} + Q/C = 0$$

Initial State:

$$Q = 0$$

Charging: Solving the equations




Overhead.

Charging: Solution

RC time constant: $\tau \equiv RC$

$$Q(t) = CV_b \left[1 - e^{-t/\tau} \right]$$
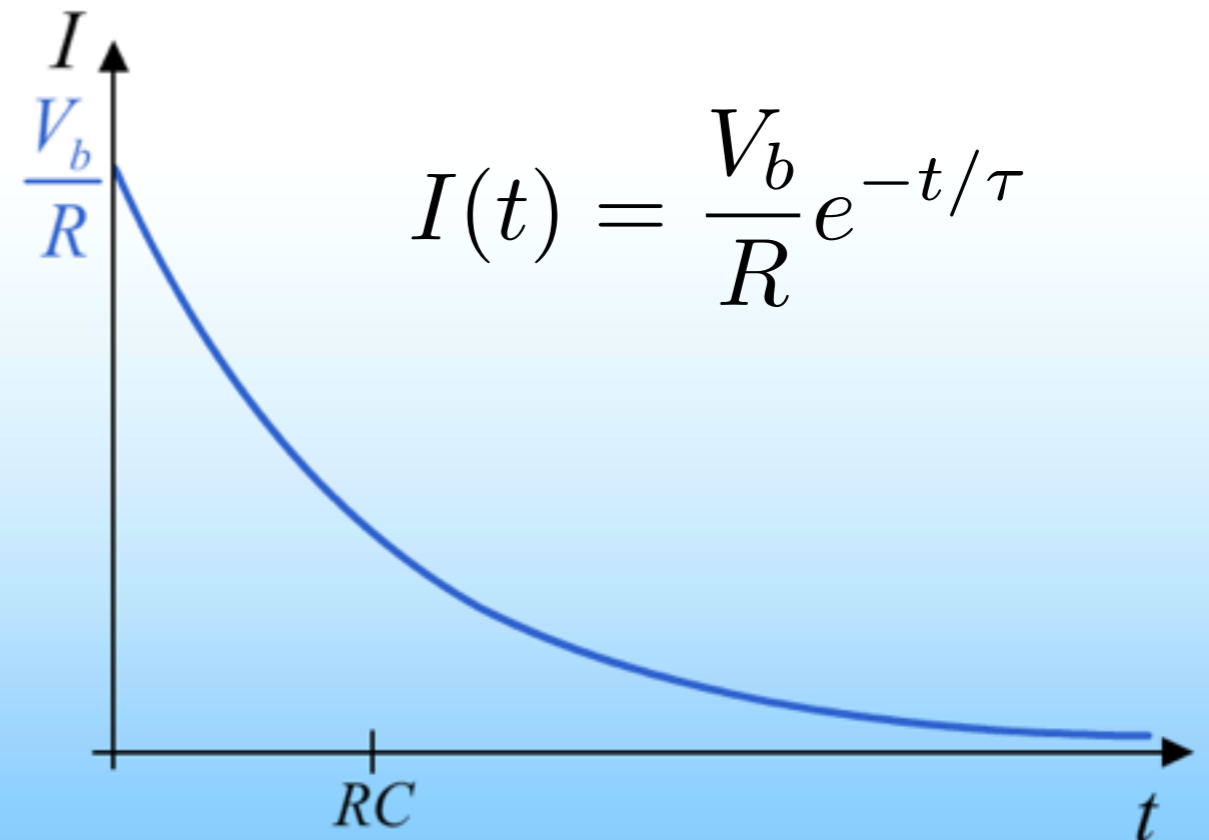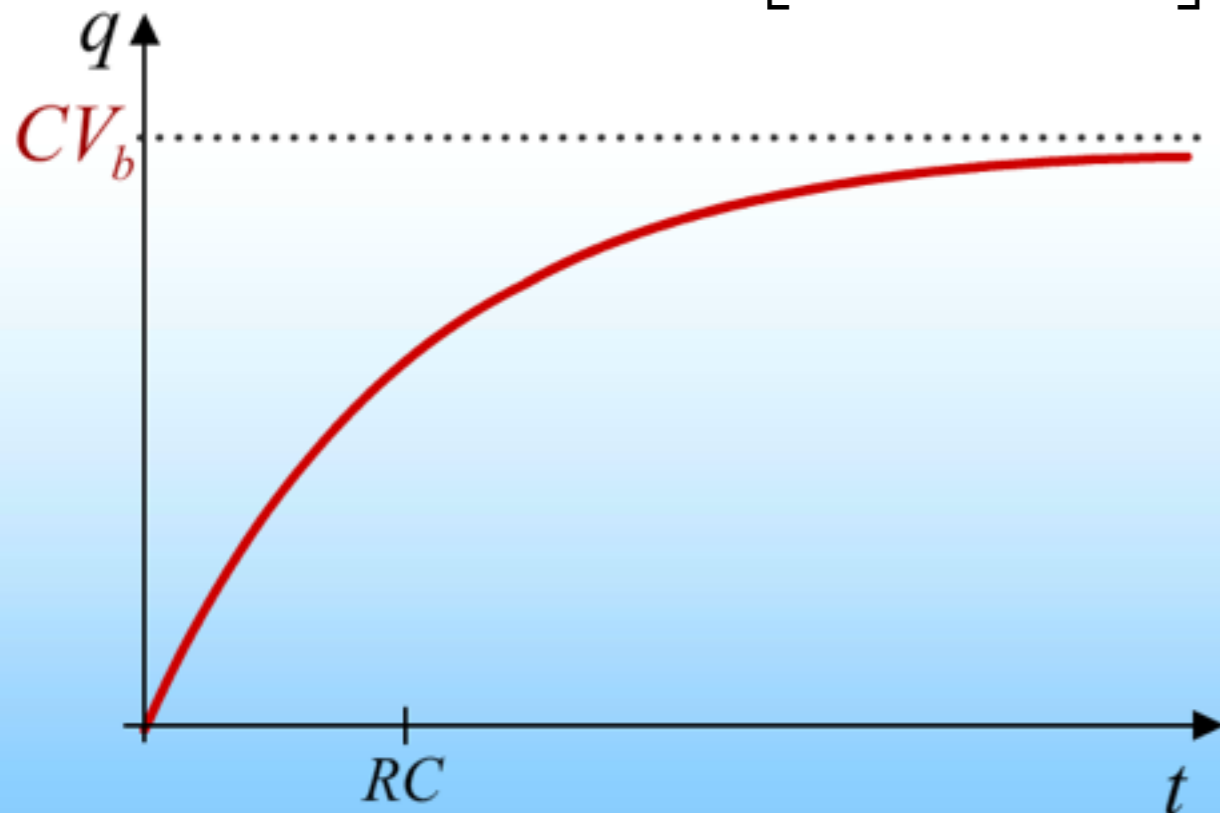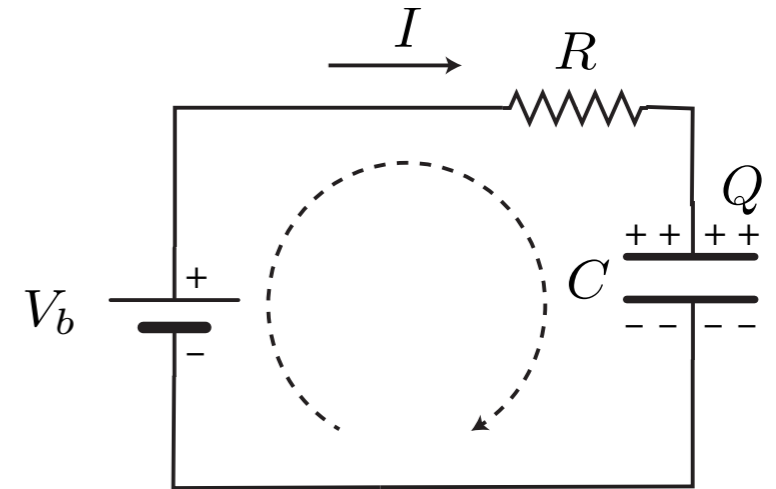
$$V_C(t) = V_b \left[1 - e^{-t/\tau} \right]$$






$$I(t) = \frac{V_b}{R} e^{-t/\tau}$$

Quick check of the units....


- RC time constant units:

$$[\tau] = [R][C] = [V][I]^{-1}[Q][V]^{-1} = [dQ/dt]^{-1}[Q] = s$$

Discharging: Overview of the action.

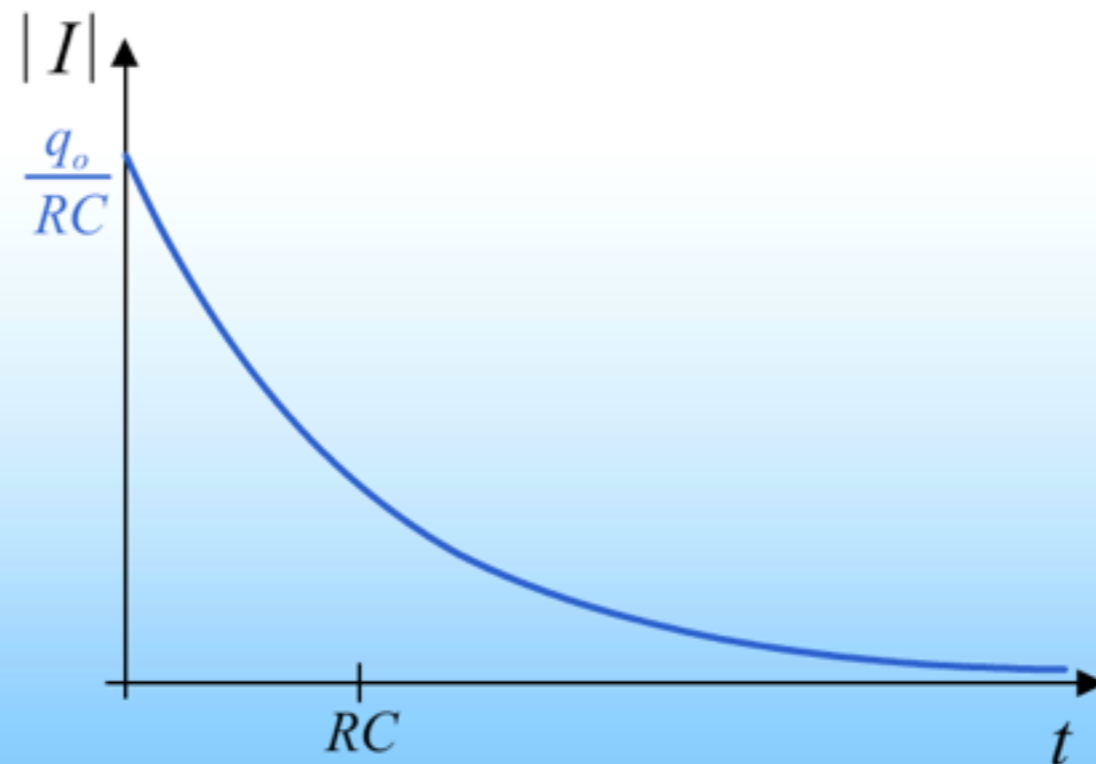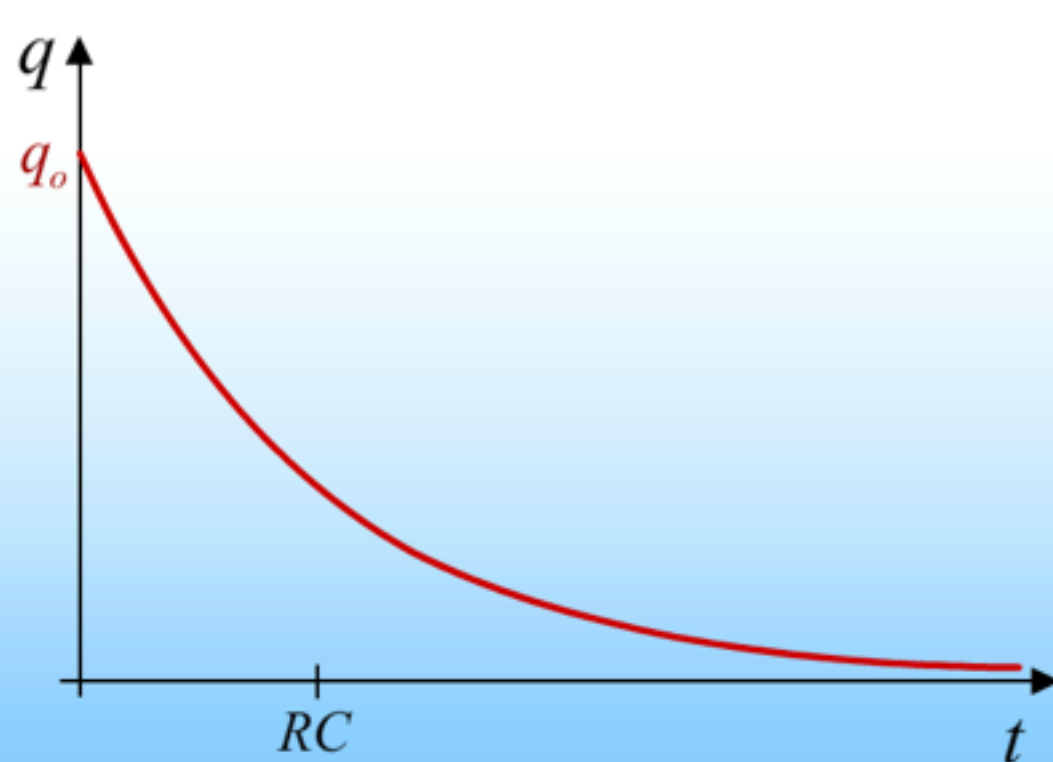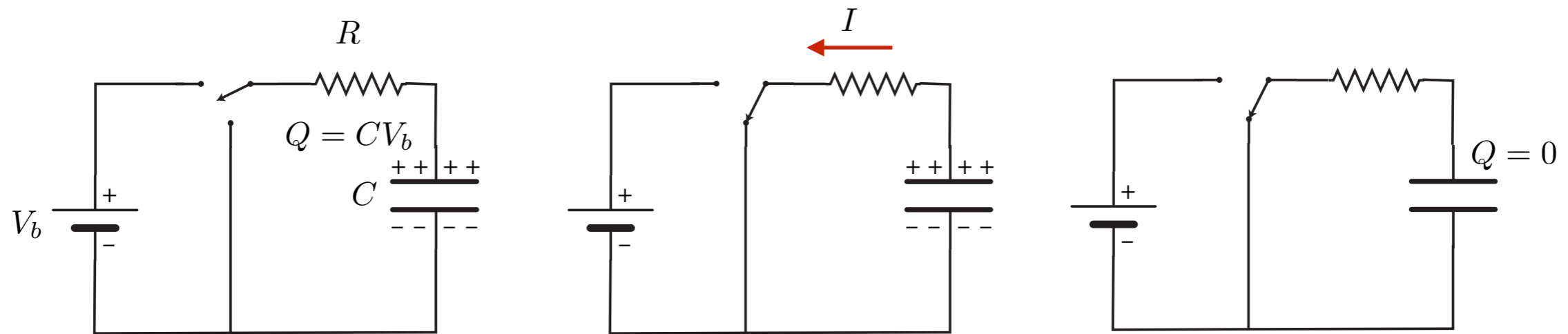

Discharging: Setting up the equations

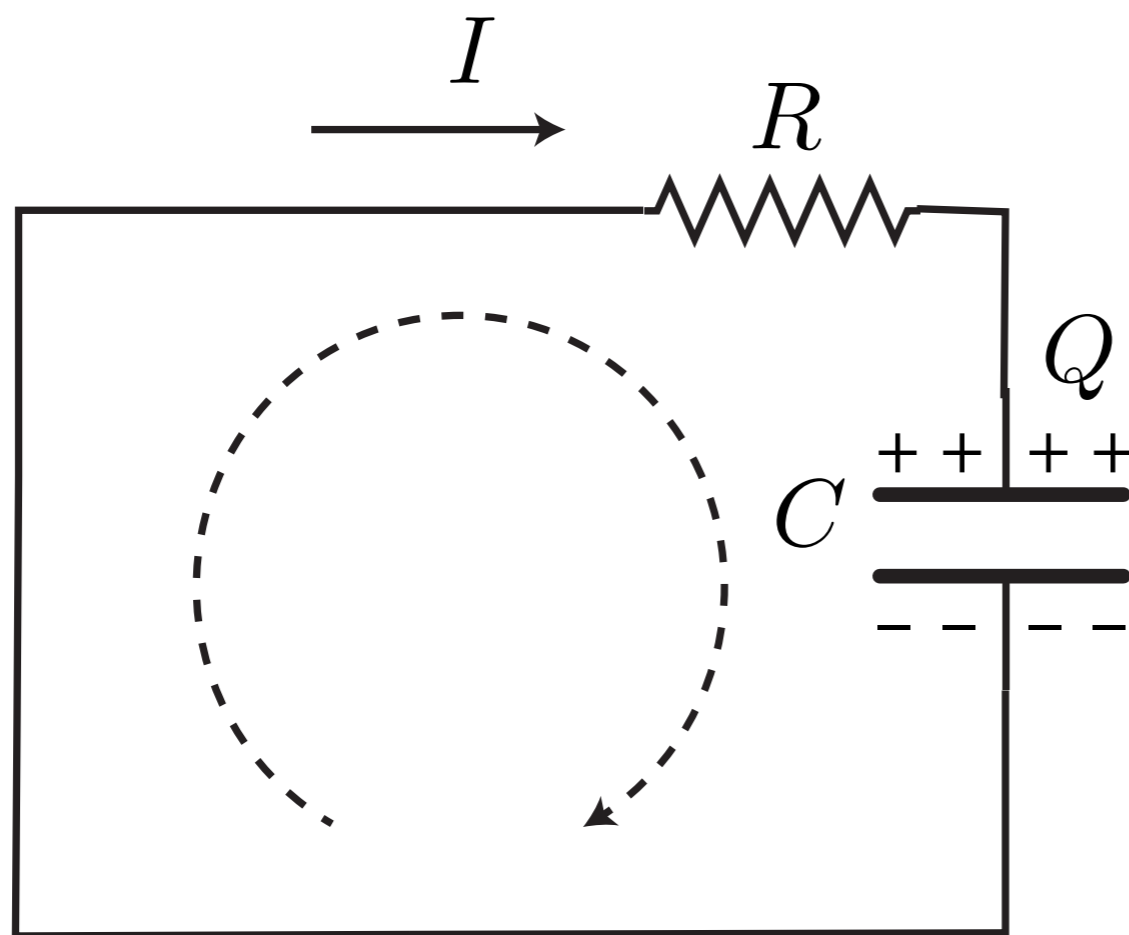

Kirchhoff Voltage Law:




$$RI + Q/C = 0$$

Initial State:

$$Q(0) = CV_b$$



Discharging: Solution

RC time constant: $\tau \equiv RC$

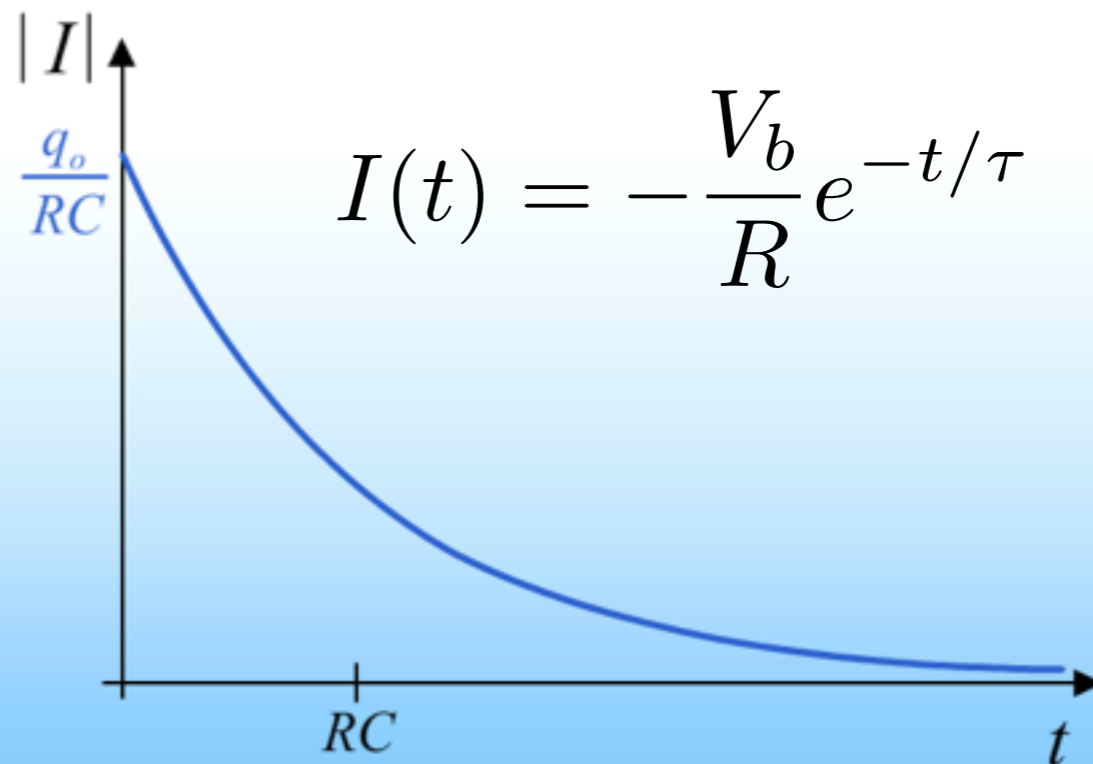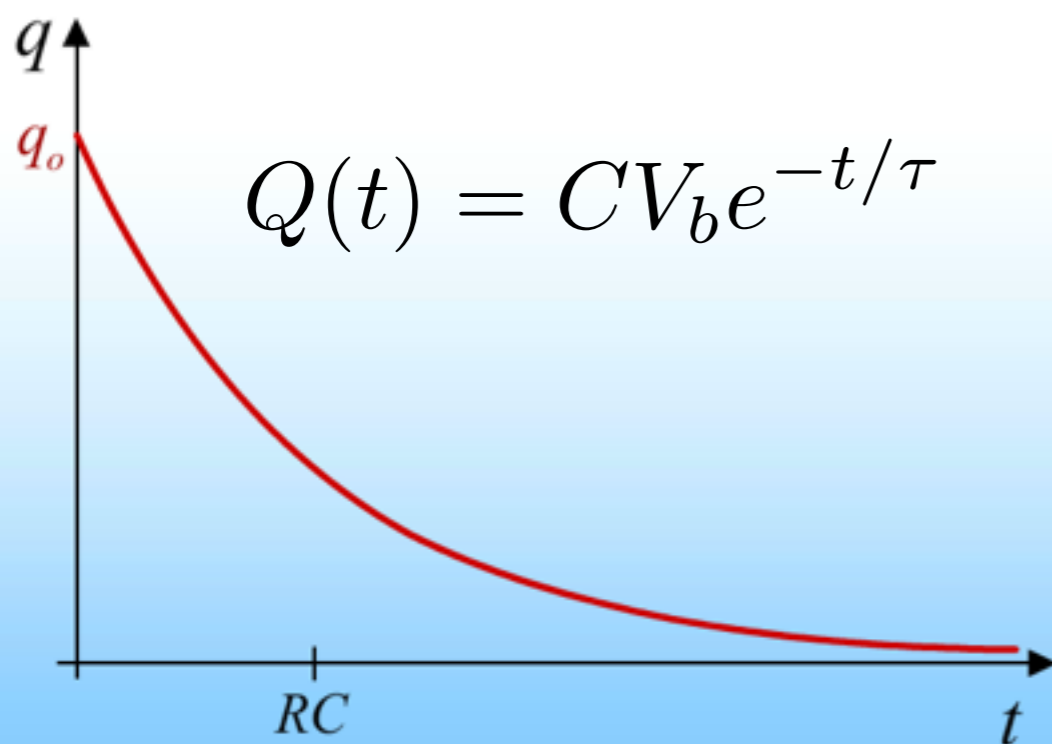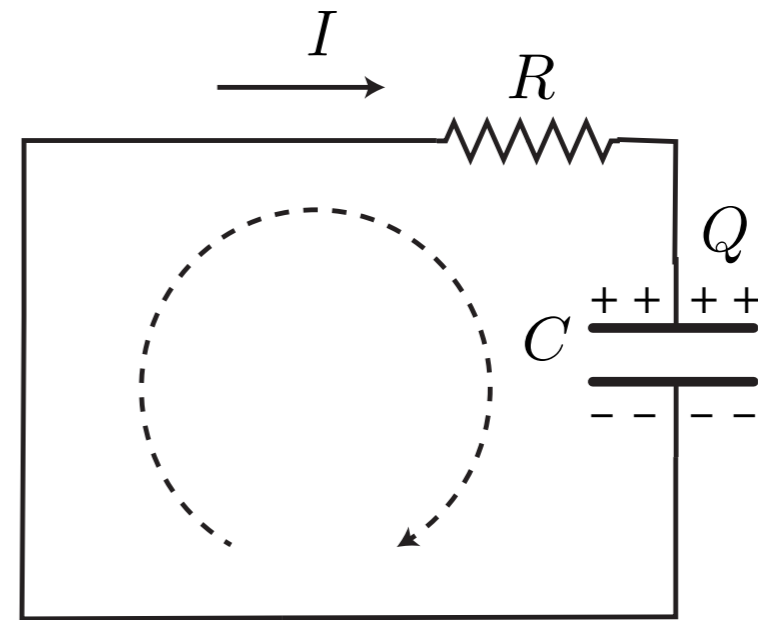

Energy flow in an RC circuit.

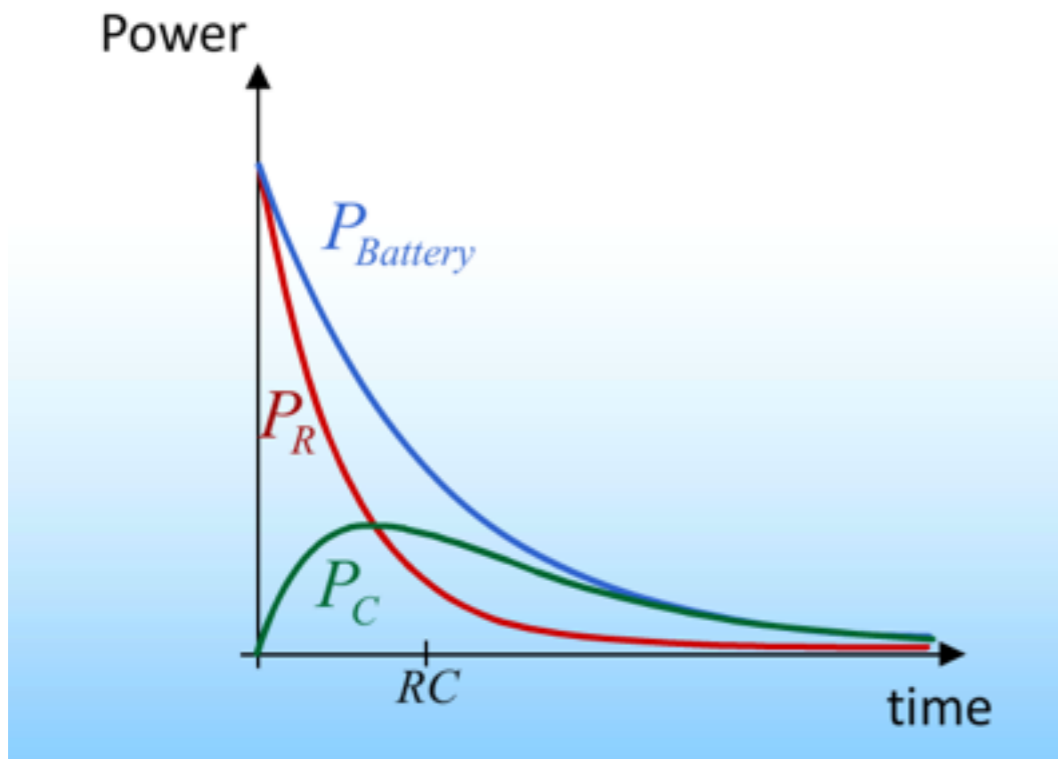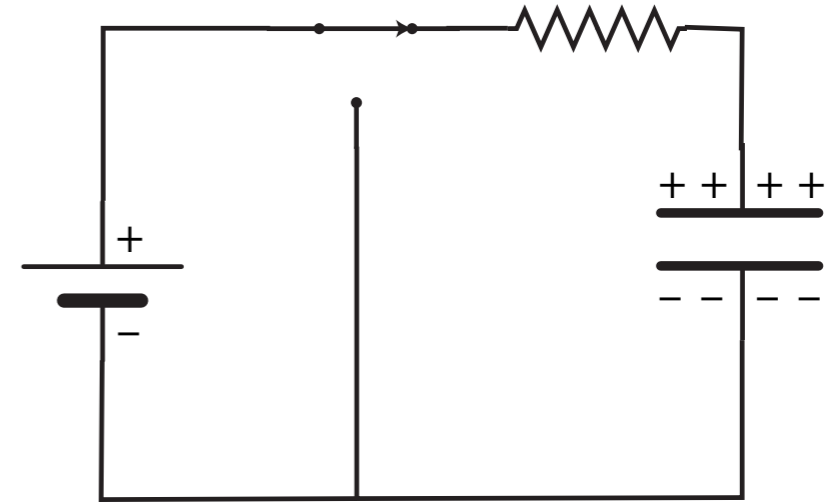- Power: $P = IV$
- Energy stored: $U = \frac{1}{2}CV^2$



$$P_{\text{Battery}}(t) = V_b I_o e^{-t/RC}$$

$$P_R(t) = R I_o^2 e^{-2t/RC}$$

$$P_C(t) = \left[\frac{q_o}{C} (1 - e^{-t/RC}) \right] \left[I_o e^{-t/RC} \right]$$