

9. (3 pts.) Which of the currents have changed in magnitude after the switch is closed?

- (A) Only I_3 has changed in magnitude.
- (B) Only I_2 and I_3 have changed in magnitude.
- (C) I_1 , I_2 , and I_3 have all changed in magnitude.
- (D) No currents have changed in magnitude.