

8. (4 pts.) What is the voltage across the 4 ohm resistor?

(A) 2 V

(B) 6 V

(C) 7 V

(D) 8 V

(E) 14 V