



7. (4 pts.) With the switch open as shown, what is the current  $I_1$ ?

- (A)  $I_1 = -7/2 \text{ A}$
- (B)  $I_1 = -1/2 \text{ A}$
- (C)  $I_1 = 1/2 \text{ A}$
- (D)  $I_1 = 3/2 \text{ A}$
- (E)  $I_1 = 7/2 \text{ A}$