

$$V_{AB} = V_B - V_A$$

$$V_{BC} = V_C - V_B$$

in parallel ~~branches~~ \Rightarrow same voltage drop.

$$I_2 = \frac{V_{AB}}{2R}$$

$$I_4 = \frac{V_{BC}}{2R}$$

$$I_3 = \frac{V_{AB}}{R}$$

$$I_5 = \frac{V_{BC}}{R}$$

ratio is set by R 's alone.

ratio is set by R 's along

"conductor"



$$\vec{E} = \frac{\lambda}{2\pi\epsilon_0 r} \hat{r} = \frac{Q_{\text{inside}}}{2\pi\epsilon_0 L r} \hat{r}$$

$$V = - \int_0^r d\vec{l} \cdot \vec{E} = - \int_0^r dr \frac{Q_{\text{inside}}}{2\pi\epsilon_0 L r}$$

$r < a$:

$$= 0$$

$r \geq a$:

$$= 0 - \int_a^r \frac{1}{r} () = - \log \frac{r}{a} \cdot \frac{Q}{L 2\pi\epsilon_0}$$



insulator :

$r < a$

$$V = - \int_0^r \left(\frac{\cancel{\pi} r^2}{\cancel{\pi} a^2} \right) \frac{Q}{L} \frac{1}{2\pi\epsilon_0} \frac{1}{r} = - \frac{r^2}{2 a^2} \cdot \frac{Q}{L} \frac{1}{2\pi\epsilon_0}$$
$$= - \frac{1}{4\pi\epsilon_0} \frac{Q}{L} \frac{r^2}{a^2}$$


$r \geq 0$

Same as conductor. |

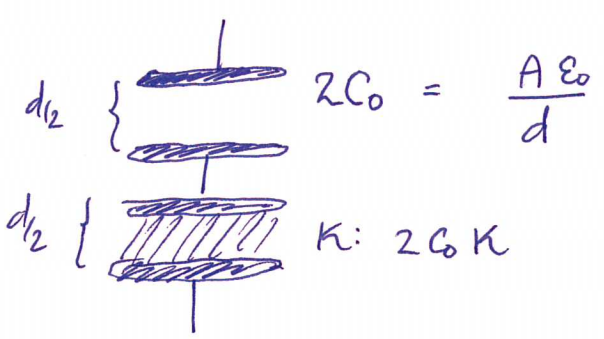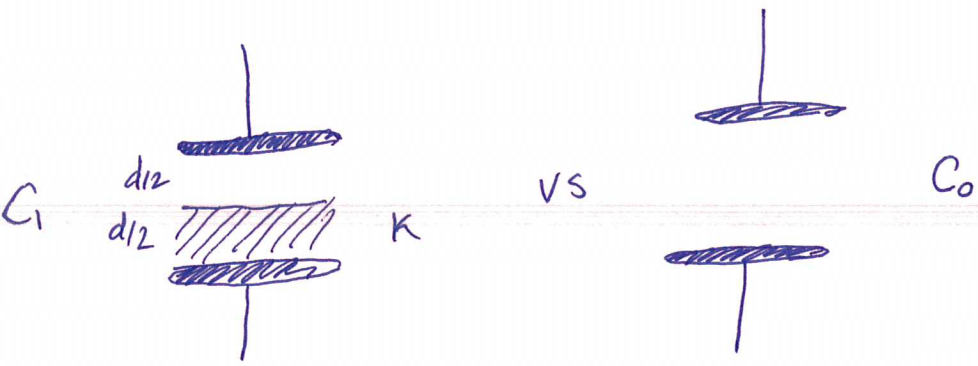


$$C_{\text{equiv}} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = C_0 \left(\frac{K}{2K} + \frac{1}{2K} \right)^{-1}$$

$$= C_0 \frac{2K}{(1+K)}$$

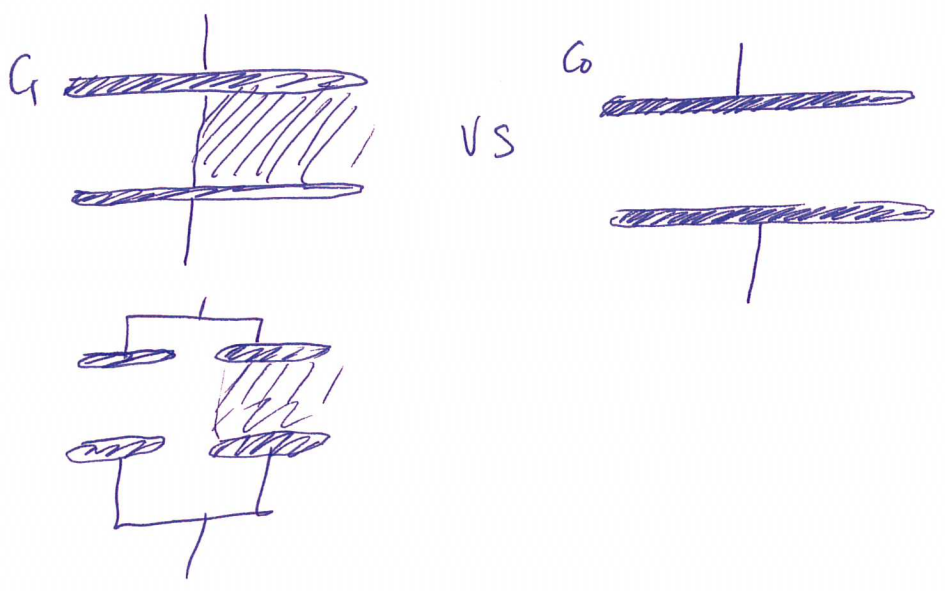

$$C_1 = C_A + K C_A$$

$$C_1 = (1+K) \frac{C_0}{2}$$

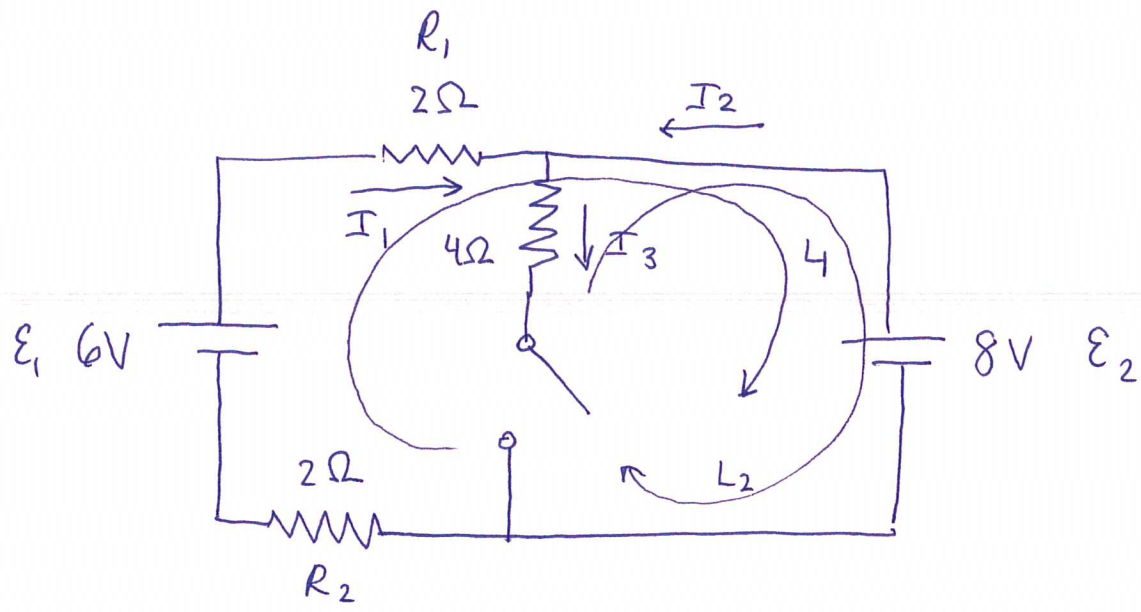

$$I_1 + I_2 = I_3$$

$$\begin{array}{l}
 L_1: \quad -\mathcal{E}_1 + I_1 R_1 + \mathcal{E}_2 + I_1 R_2 = 0 \\
 L_2: \quad -R_3 I_3 + \mathcal{E}_2 = 0
 \end{array}
 \left. \vphantom{\begin{array}{l} L_1 \\ L_2 \end{array}} \right\} \begin{array}{l} \text{Not coupled} = \Delta \\ \text{it is the same.} \end{array}$$