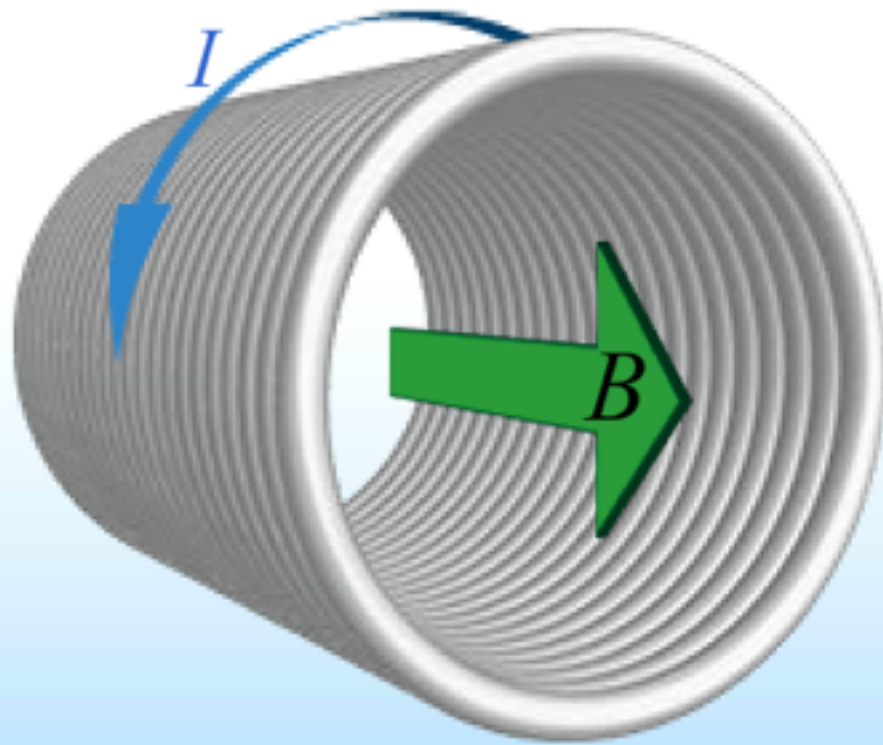


Inductance, inductors, RL circuits

Lecture 23


Induction/Inductors

Solenoids



$$L = \Phi_B / I$$


RL Circuit

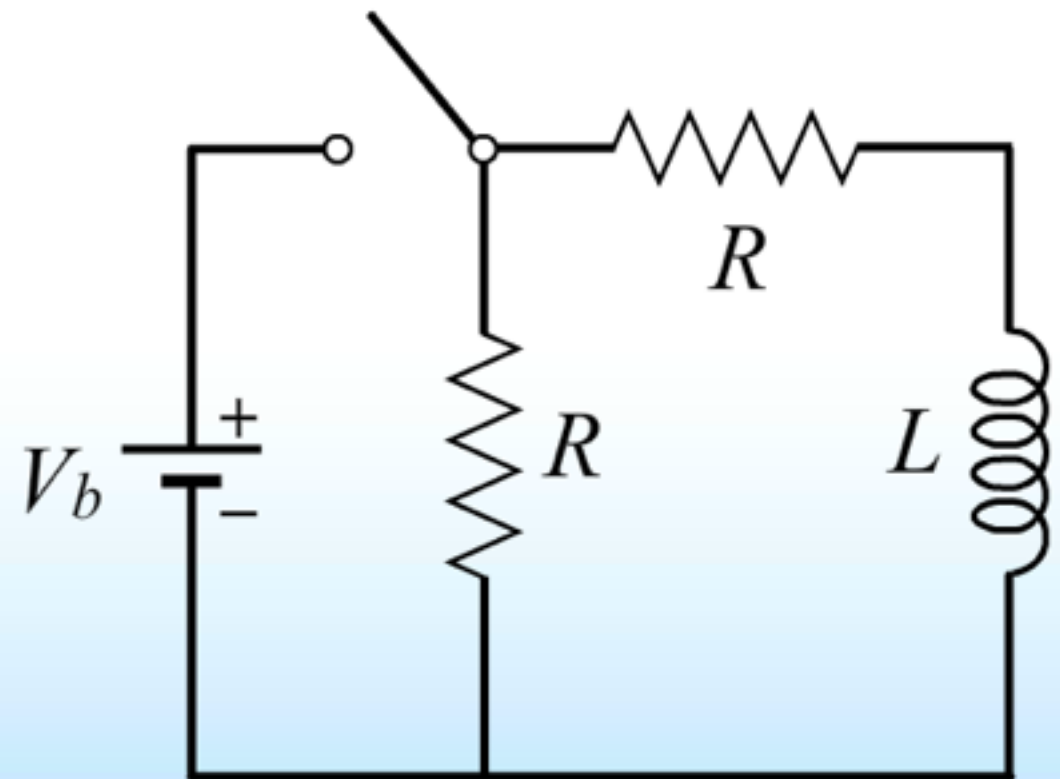

$$V_L = L \frac{dI}{dt}$$

$$\mathcal{E} = -\frac{d\Phi_B}{dt} = -L \frac{dI}{dt} = -V_L$$

Self-Inductance

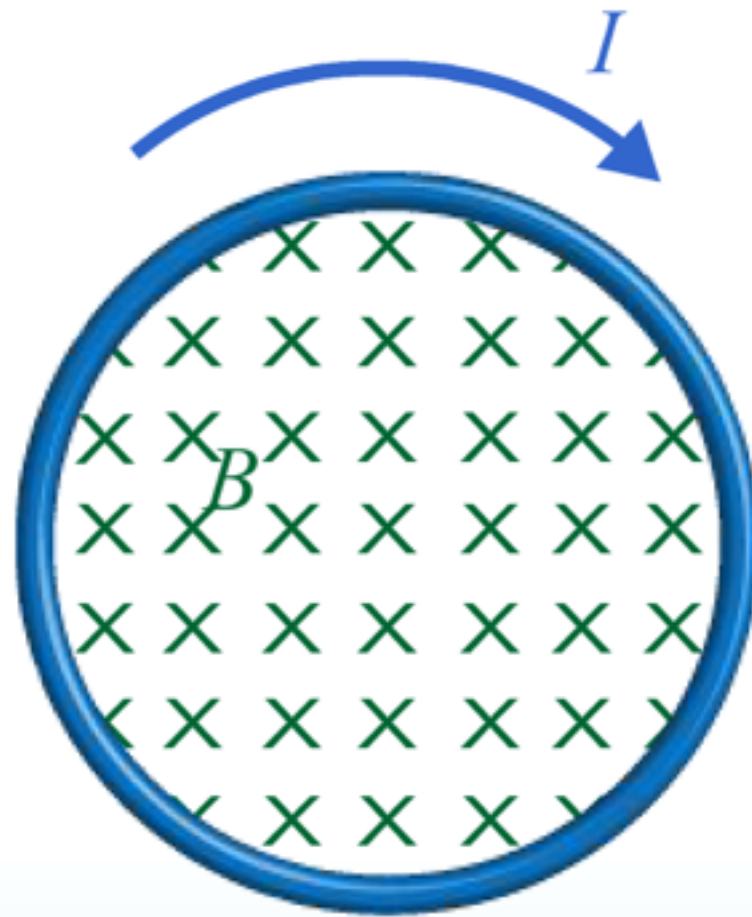

Self-Inductance

$$L \equiv \frac{\Phi_B}{I}$$


SI Unit

$$\text{H} = \text{T}\cdot\text{m}^2/\text{A}$$

Inductor Voltage

$$\mathcal{E} = -L \frac{dI}{dt}$$

Calculation of inductance:

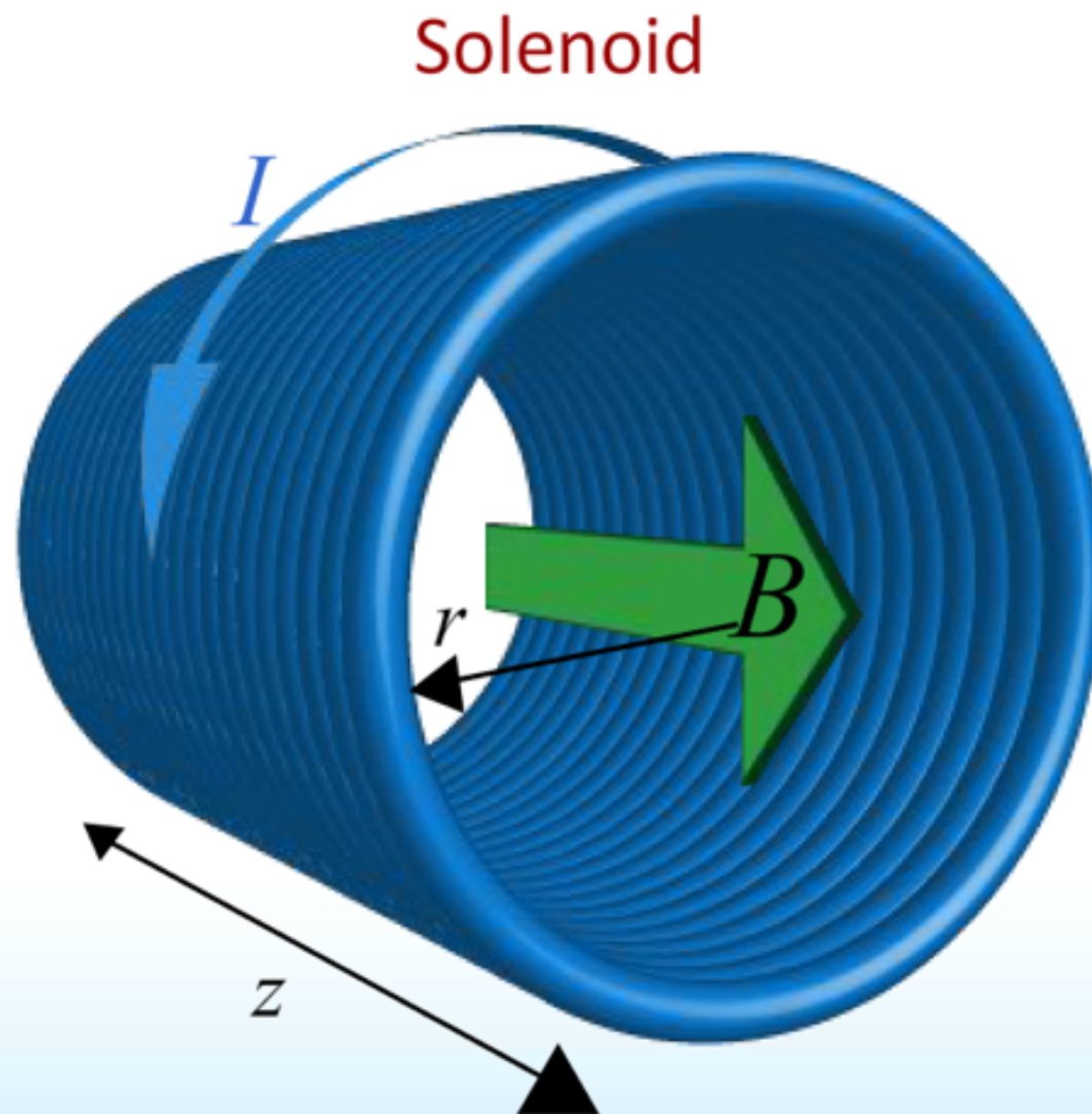

Magnetic Field

$$B = \mu_0 n I$$

Magnetic Flux


$$\Phi_B = \mu_0 n^2 z \pi r^2 I$$

Self-Inductance

$$L = \mu_0 n^2 z \pi r^2$$


New: RL circuits

Solenoids

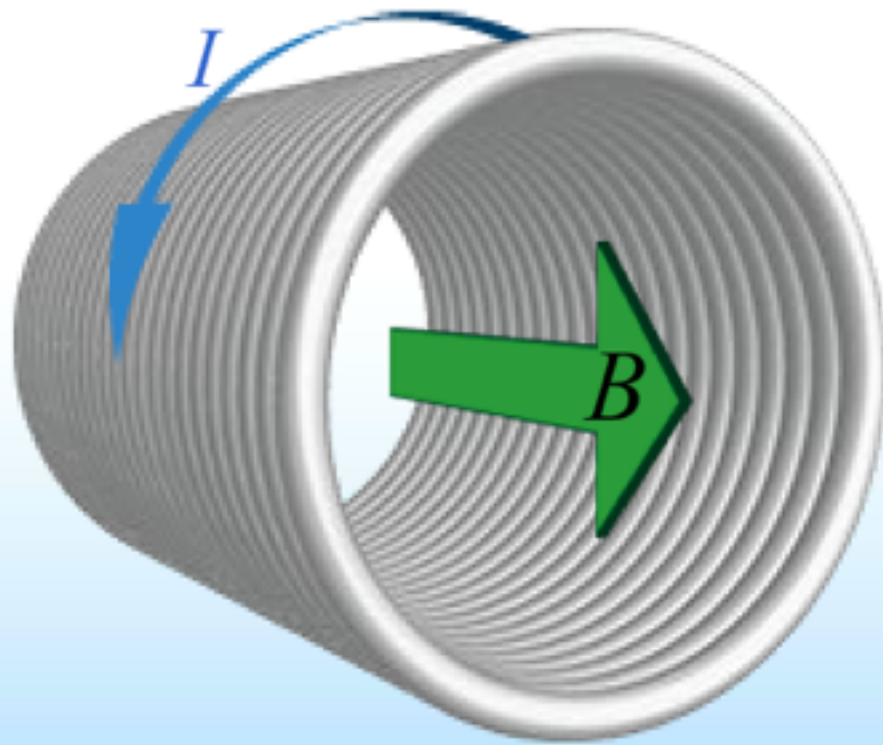

$$L = \Phi_B / I$$

RL Circuit

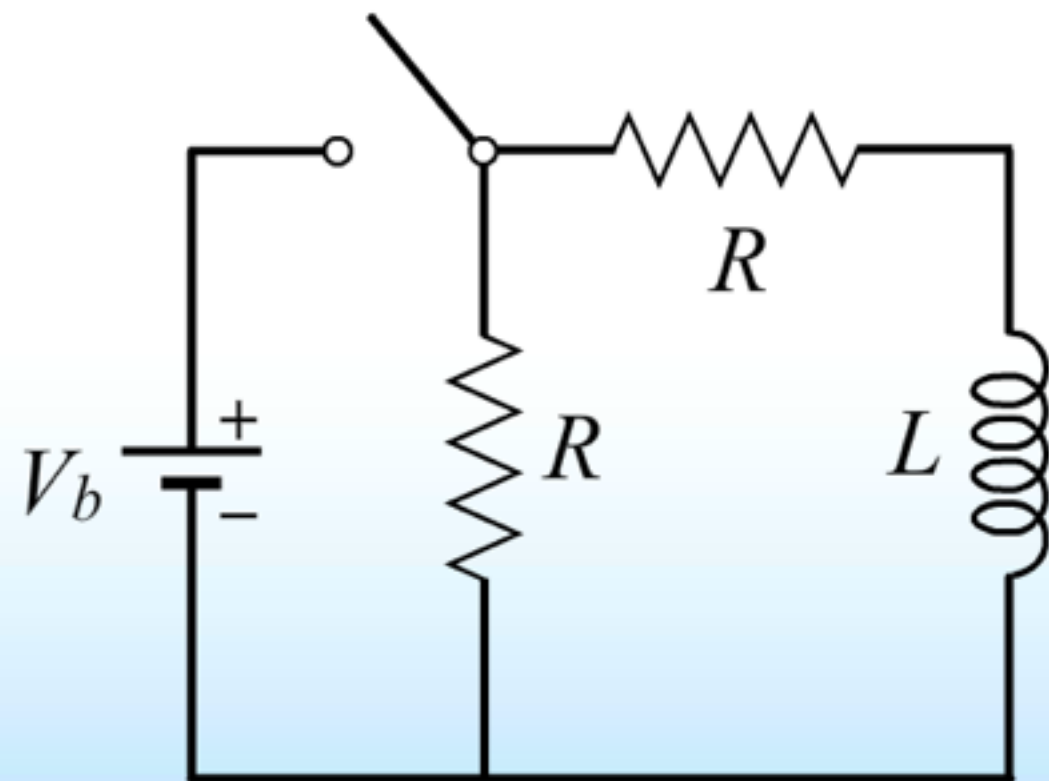


$$V_L = L \frac{dI}{dt}$$

(Reasoning) RL Circuits 1

Closing Switch

$t = 0$
$V_R(0) =$
$V_L(0) =$
$I_1(0) =$

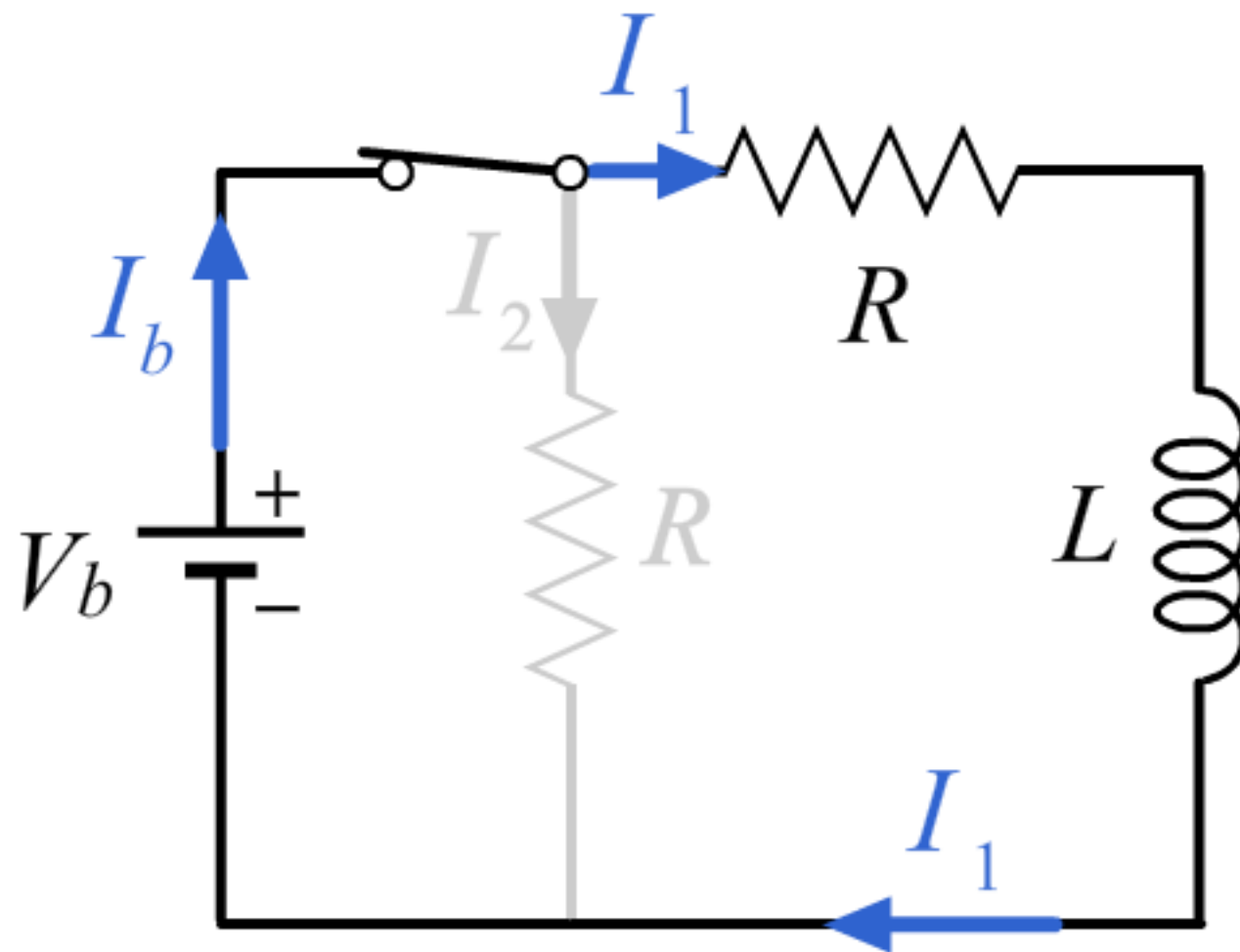$t \rightarrow \infty$
$V_R(\infty) =$
$V_L(\infty) =$
$I_1(\infty) =$



$$V_L = L \frac{dI}{dt}$$

(Reasoning) RL Circuits 1

Opening Switch

$$t = 0$$

$$V_R(0) =$$

$$V_L(0) =$$


$$I(0) =$$

$$t \rightarrow \infty$$

$$V_R(\infty) =$$

$$V_L(\infty) =$$

$$I(\infty) =$$

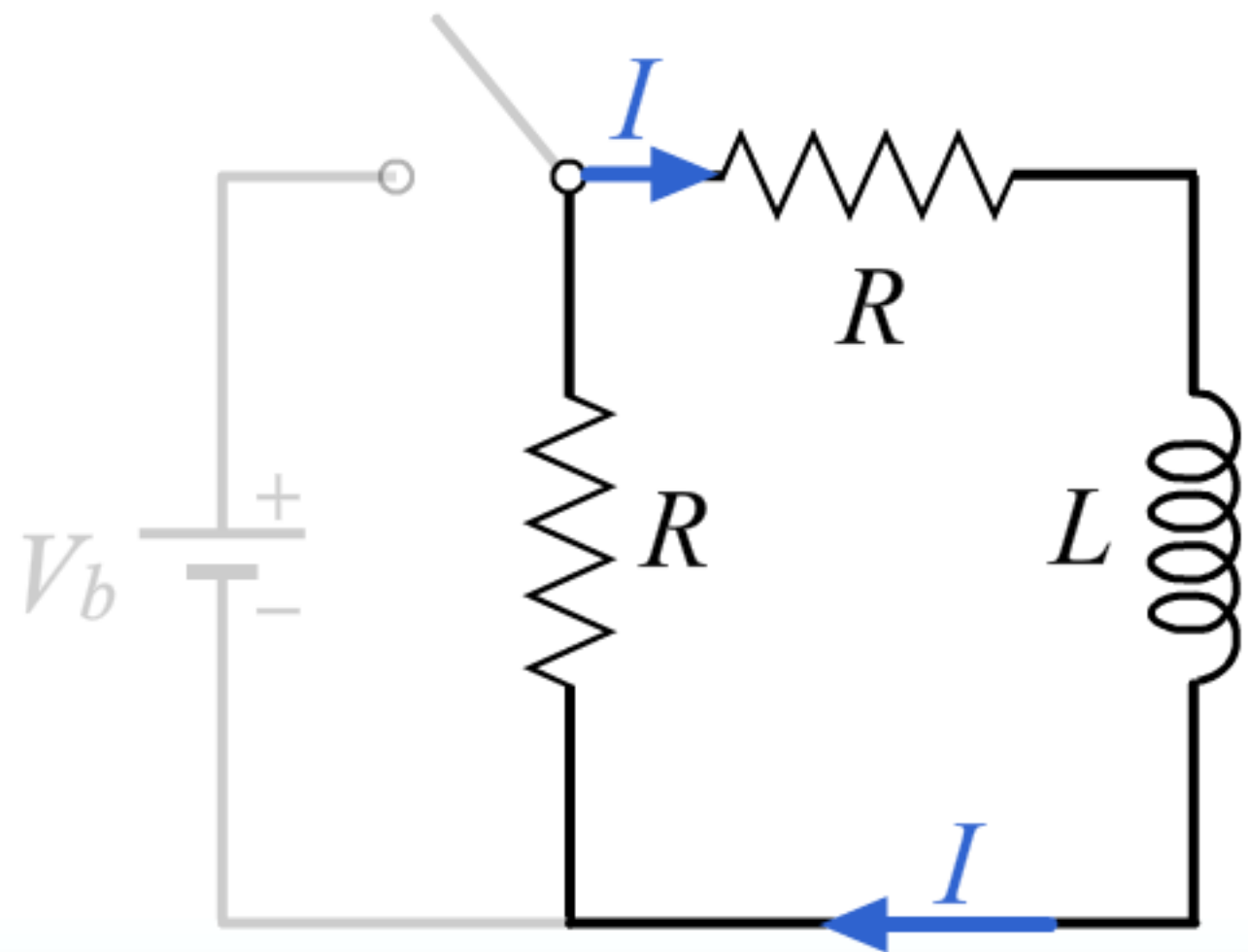

$$V_L = L \frac{dI}{dt}$$

RL Circuits: Detailed Analysis

Closing Switch

$$t = 0$$

$$V_R(0) = 0$$

$$V_L(0) = V_b$$


$$I_1(0) = 0$$

$$t \rightarrow \infty$$

$$V_R(\infty) = V_b$$


$$V_L(\infty) = 0$$

$$I_1(\infty) = \frac{V_b}{R}$$

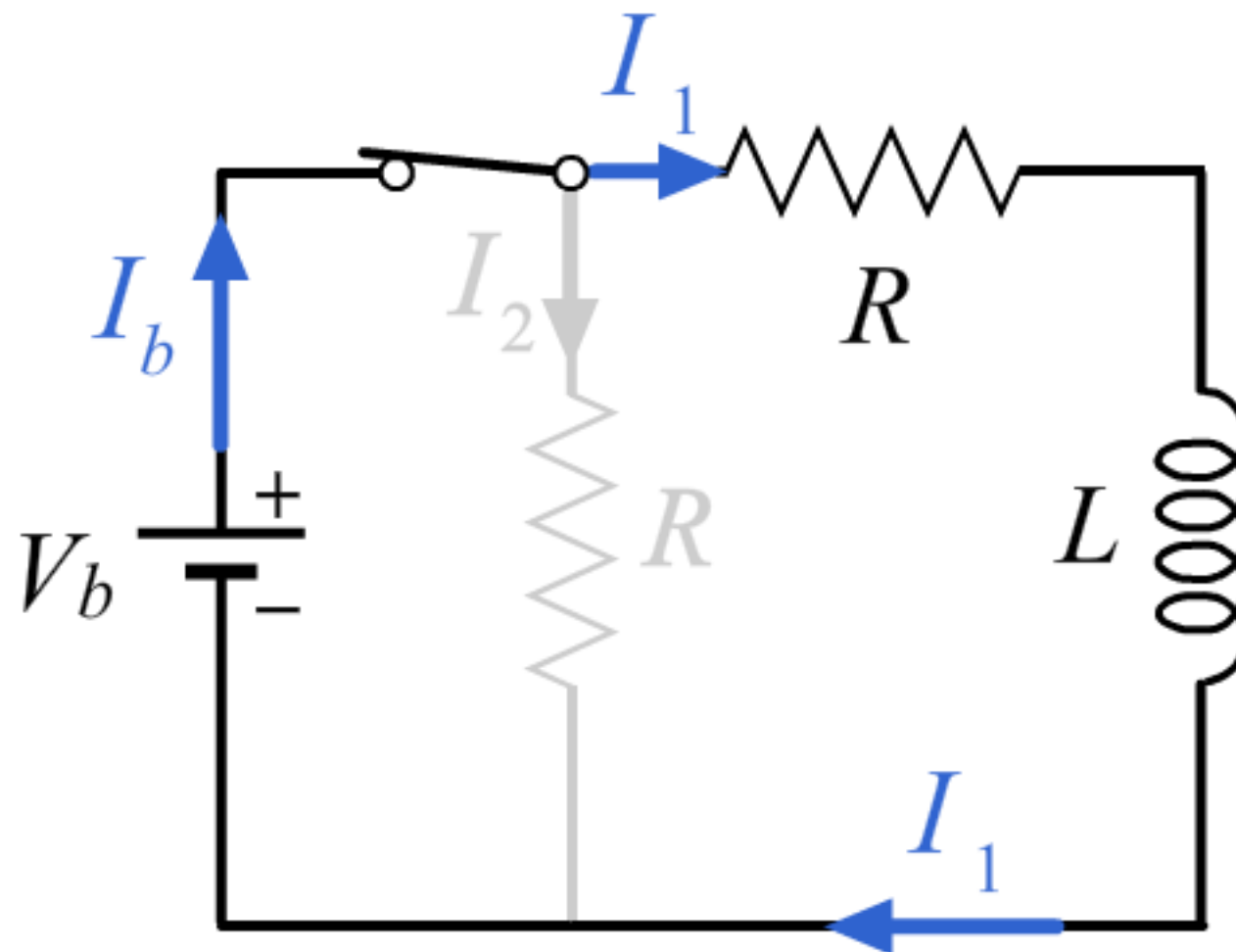

$$V_L = L \frac{dI}{dt}$$

RL Circuits: Detailed Analysis

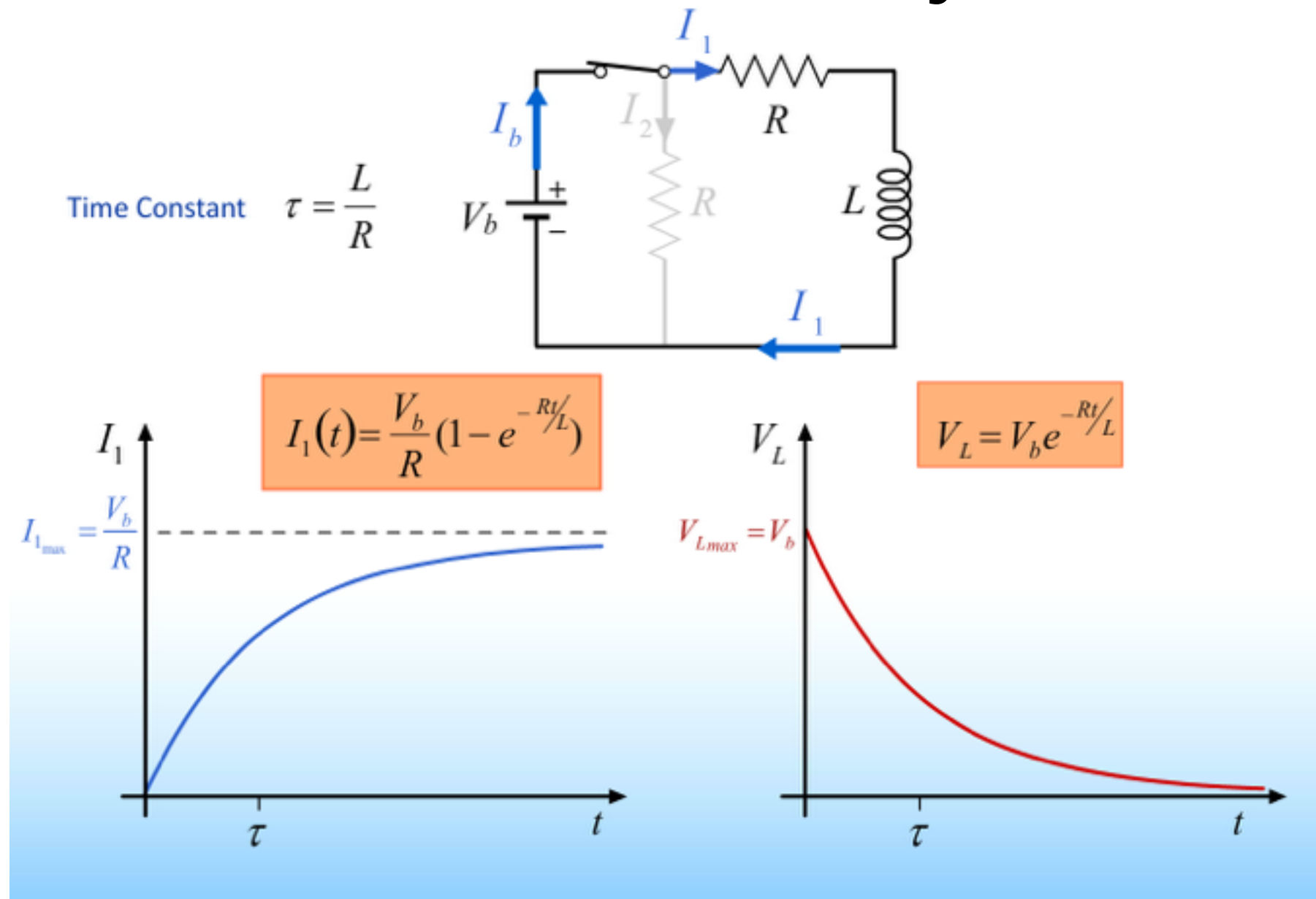

- Results

RL Circuits: Detailed Analysis

Opening Switch

$$t = 0$$

$$V_R(0) = V_b$$

$$V_L(0) = -2V_b$$


$$I(0) = \frac{V_b}{R}$$

$$t \rightarrow \infty$$

$$V_R(\infty) = 0$$


$$V_L(\infty) = 0$$

$$I(\infty) = 0$$

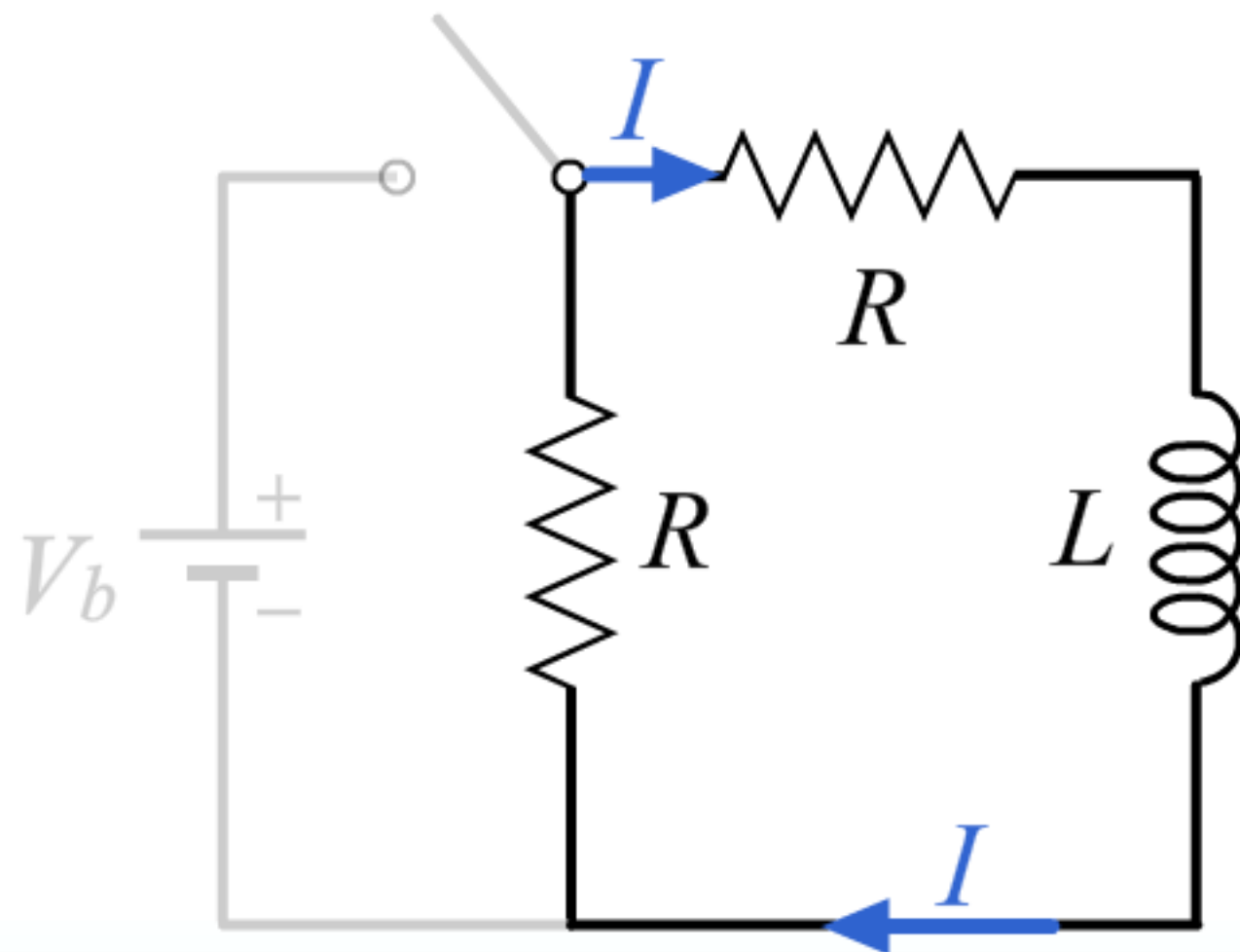


$$V_L = L \frac{dI}{dt}$$

RL Circuits: Detailed Analysis

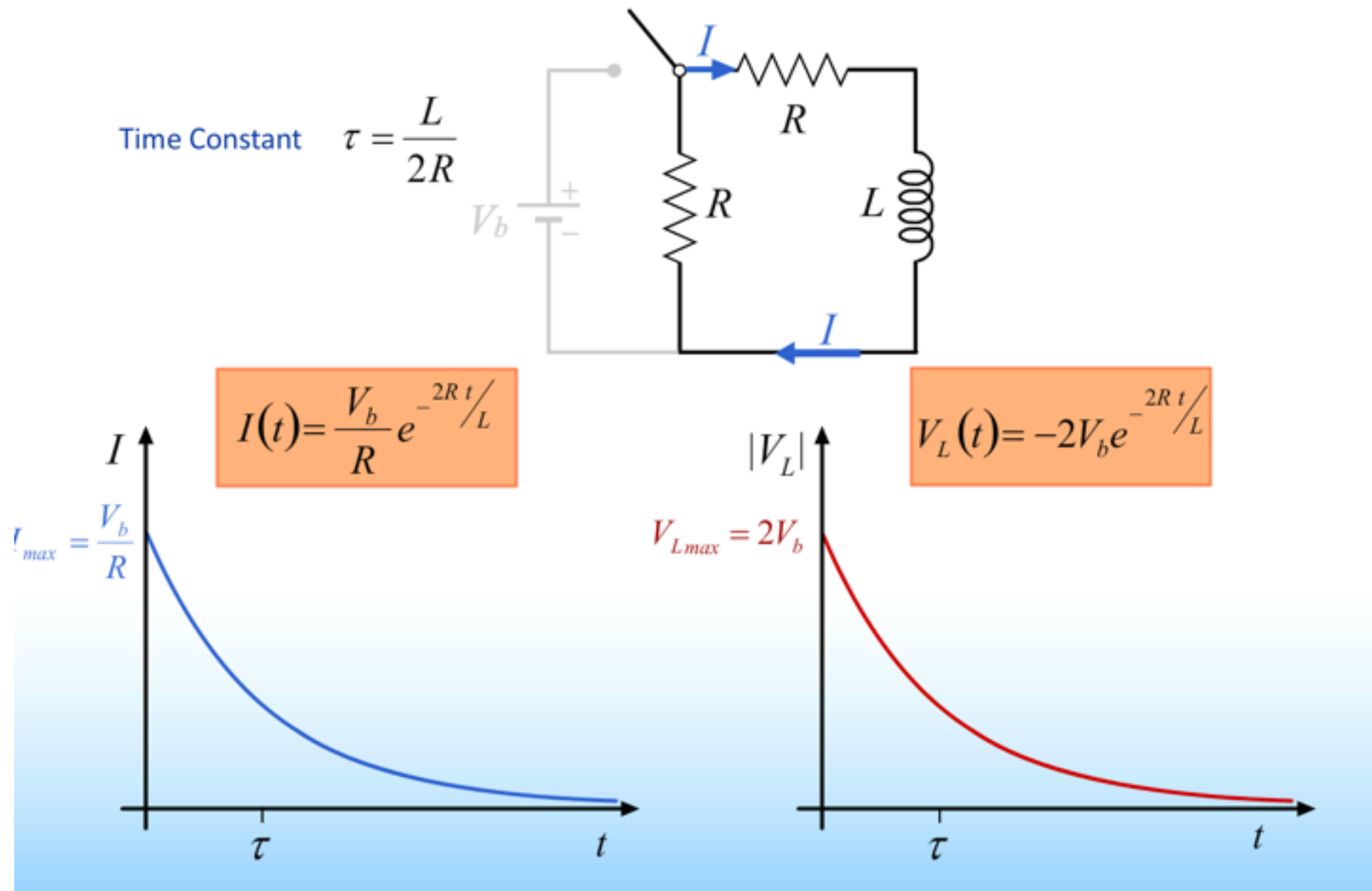


- Results


Where is the energy stored?

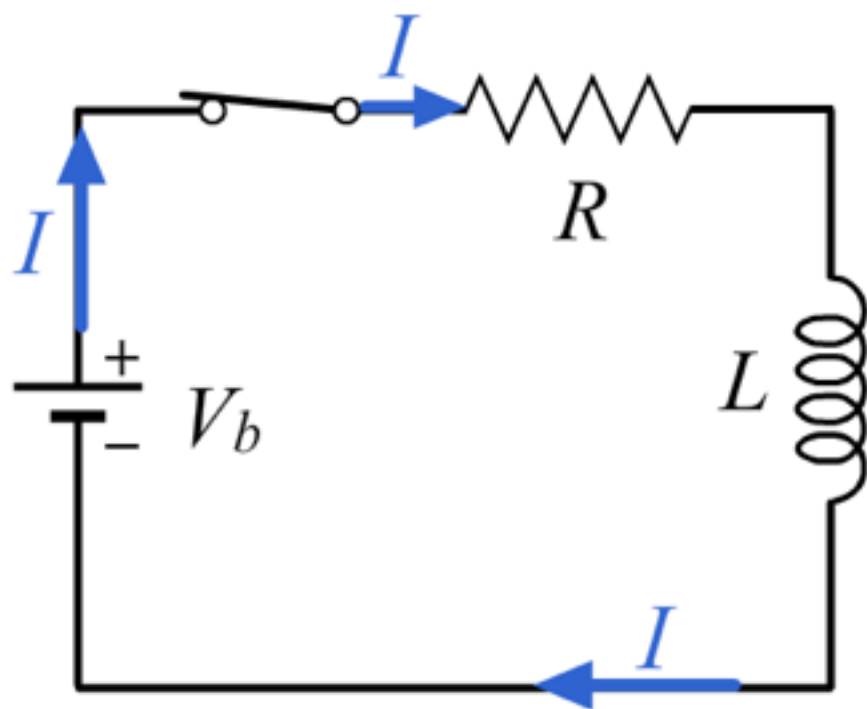

$$I(t) = \frac{V_b}{R} (1 - e^{-Rt/L})$$

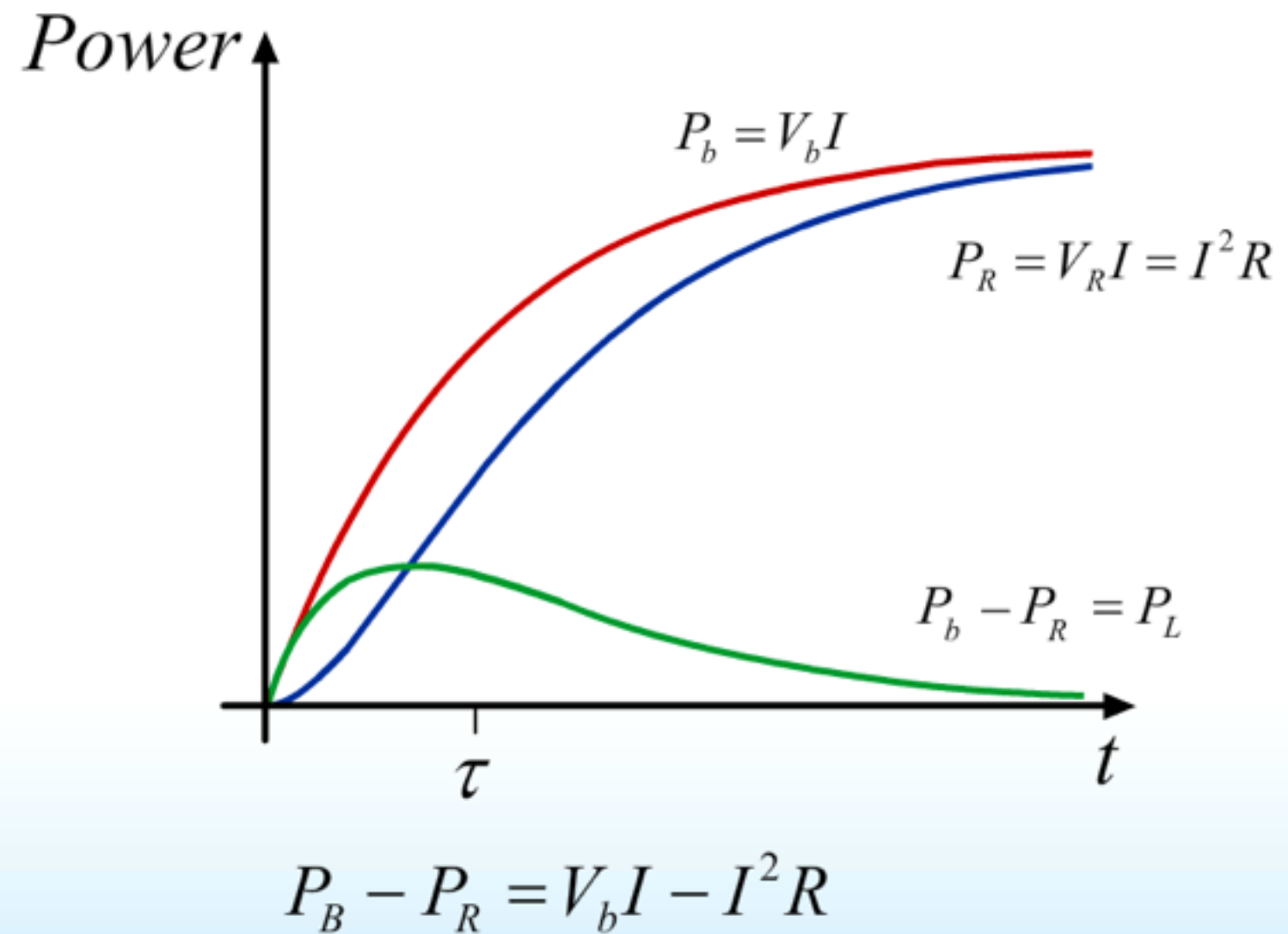


Where is the energy stored?

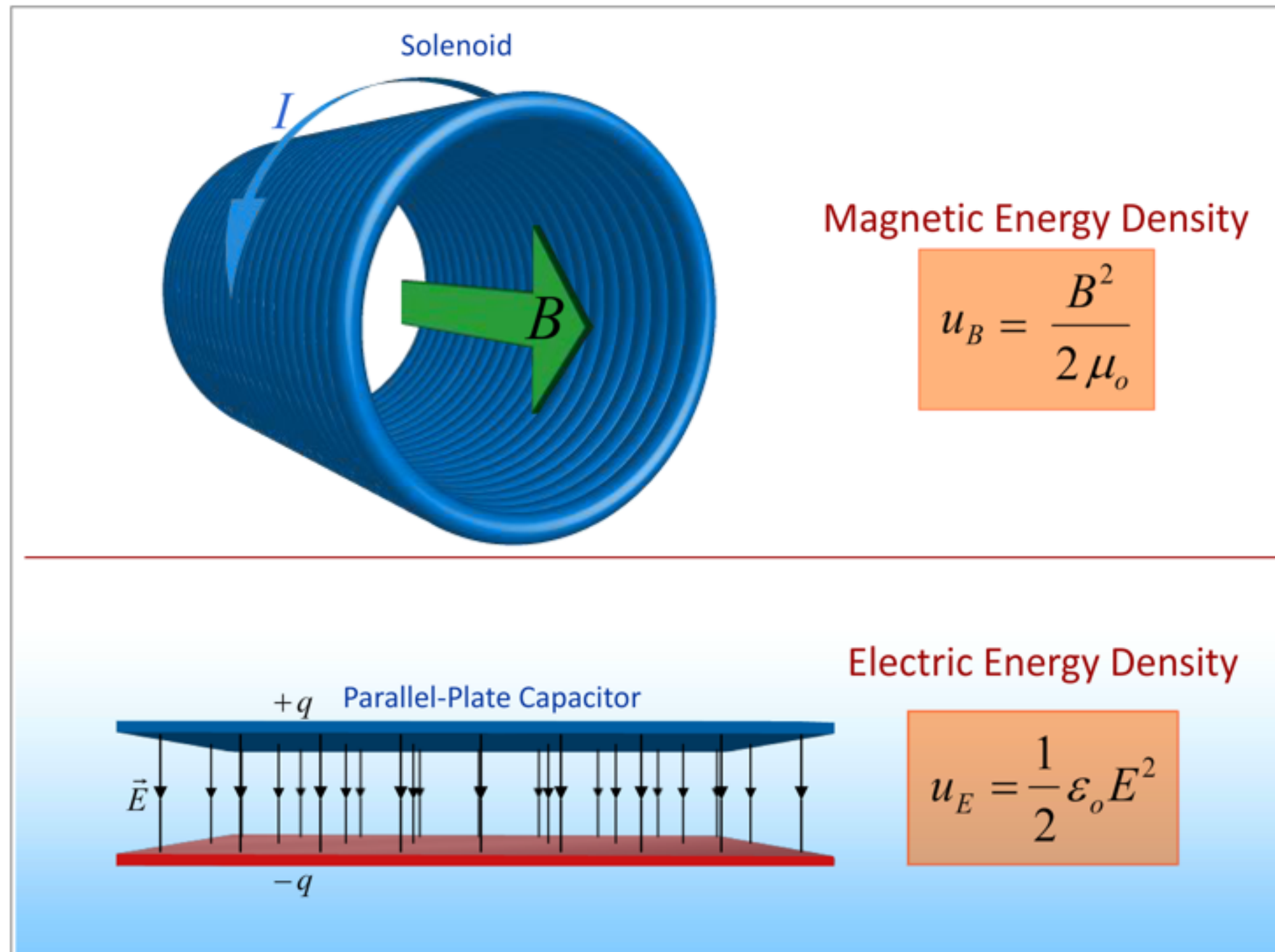


RLC circuits

Lecture 25

LC Circuits

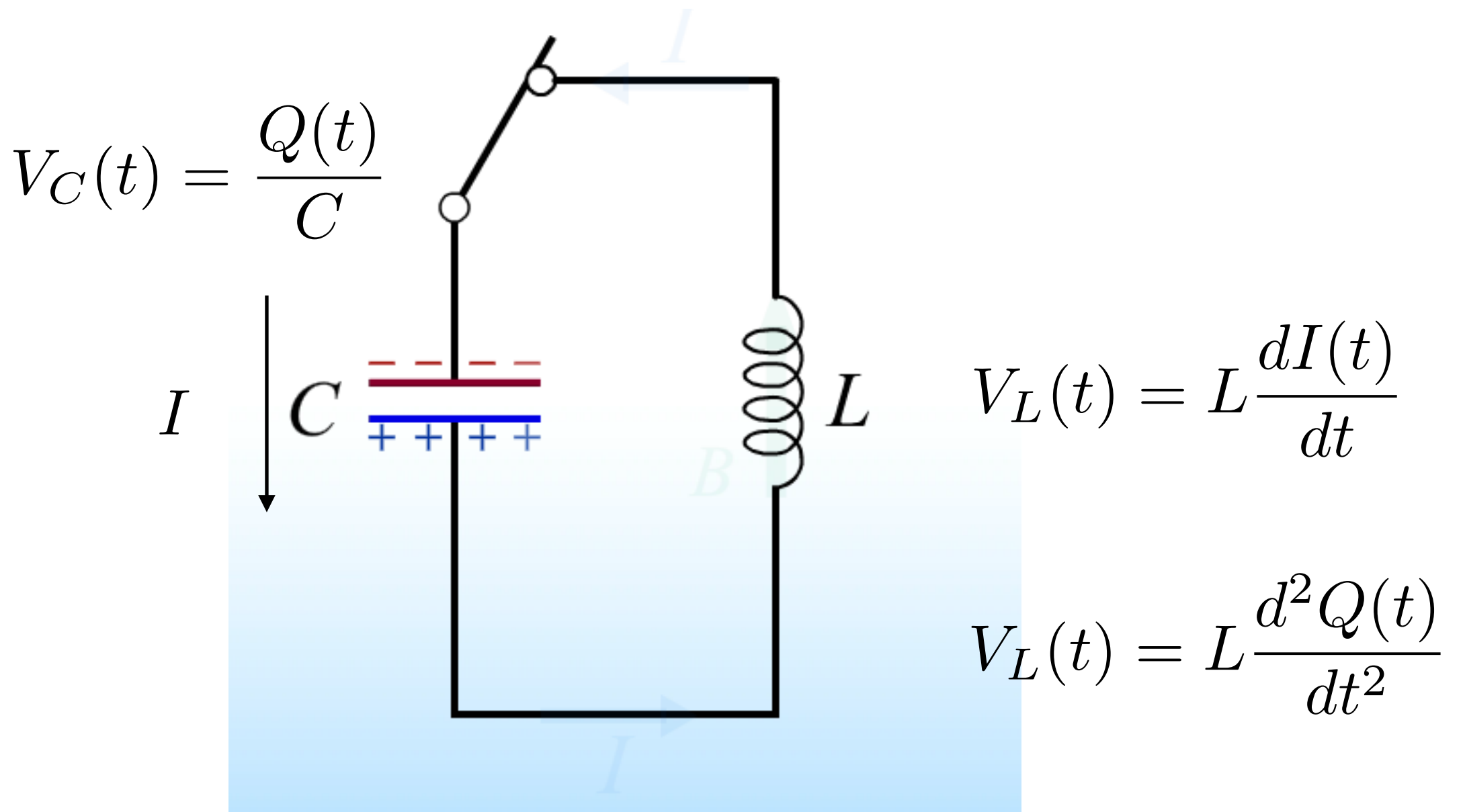


LC Circuits: Detailed Analysis

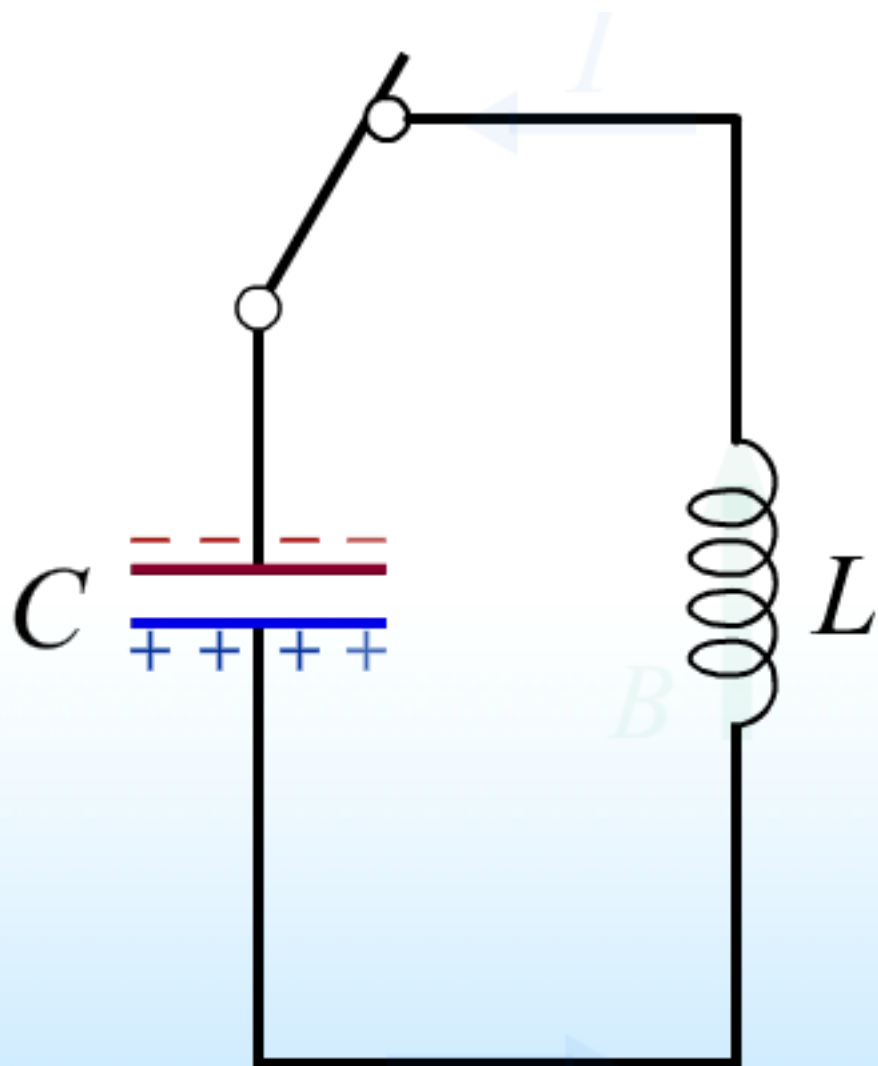

$$\text{KVL : } V_L(t) + V_C(t) = 0$$

$$0 = \frac{Q(t)}{C} + L \frac{d^2 Q(t)}{dt^2}$$


LC Circuits: Detailed Analysis

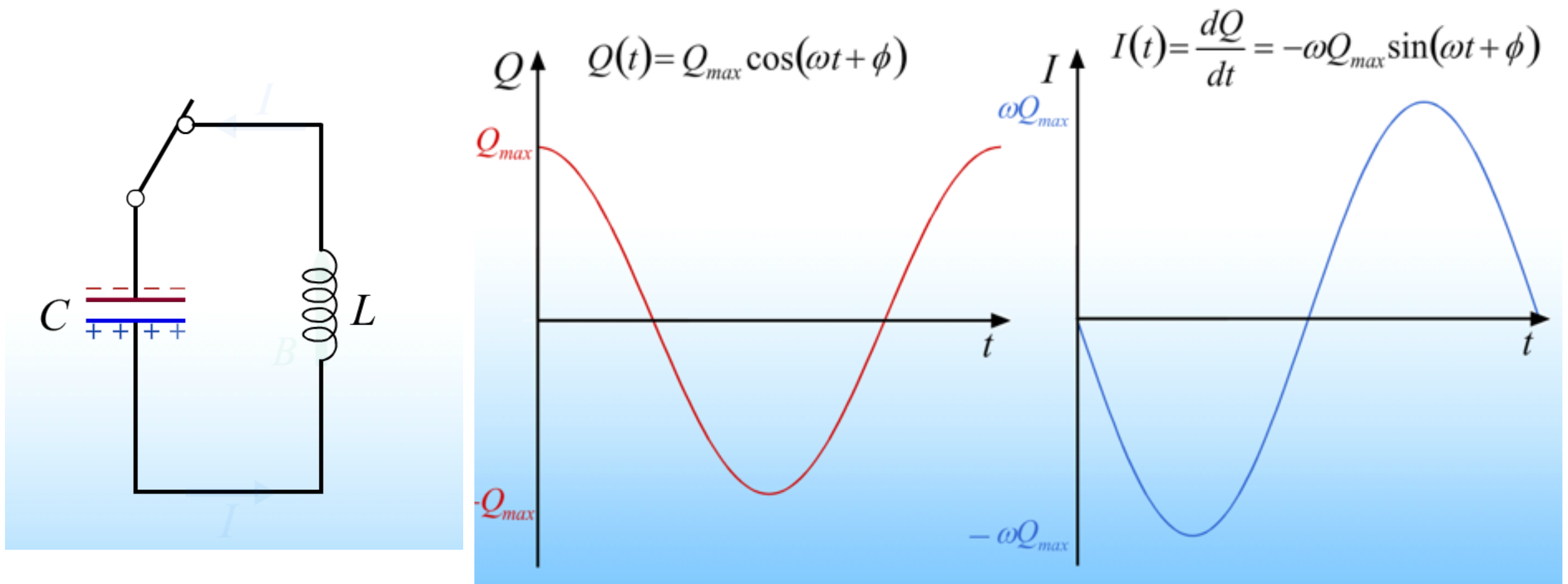

$$\omega = \sqrt{\frac{1}{LC}}$$

LC Circuits: Energy conservation

LR Circuit

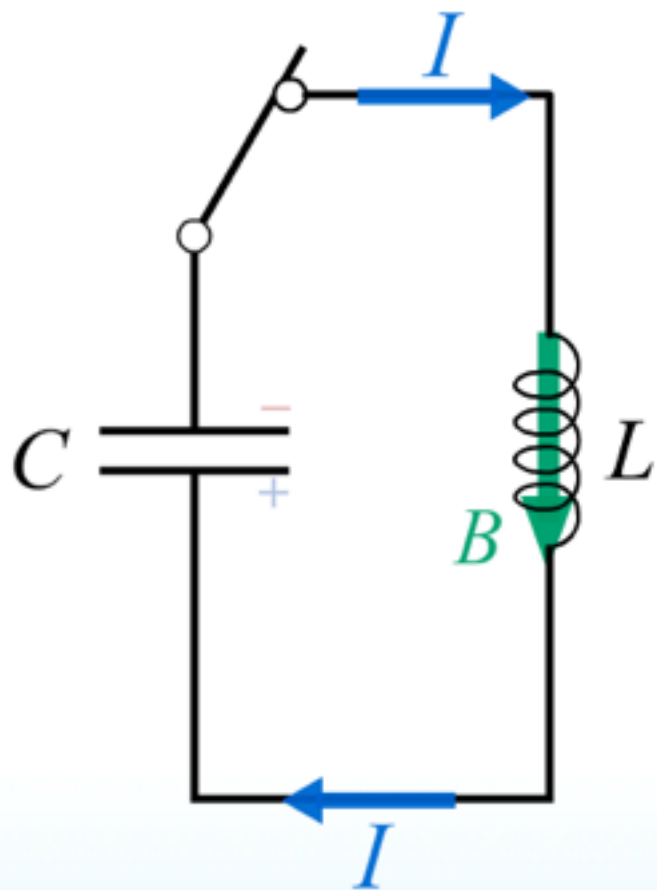

Inductor Energy

$$U_L = \frac{1}{2} LI^2$$



Kinetic Energy

$$K = \frac{1}{2} mv^2$$

Capacitor Energy


$$U_C = \frac{1}{2} \frac{Q^2}{C}$$



Spring Potential Energy

$$U_{spring} = \frac{1}{2} kx^2$$

Oscillating Block

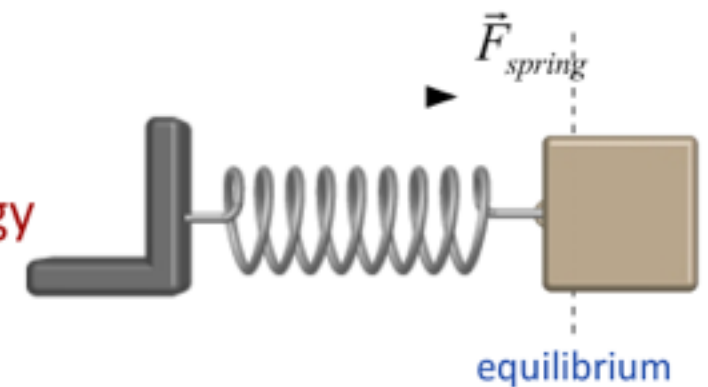


LRC Circuits

KVR

$$\frac{Q}{C} + R \frac{dQ}{dt} + L \frac{d^2 Q}{dt^2} = 0$$

Solution
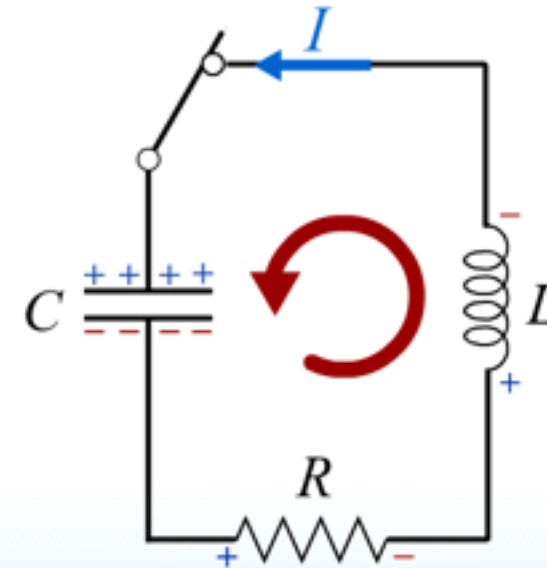
$$Q(t) = A e^{-\beta t} \cos(\omega' t + \phi)$$



Damping Factor $\beta = \frac{R}{2L}$

Oscillation Frequency $\omega'^2 = \omega_o^2 - \beta^2$

Natural Frequency $\omega_o = \frac{1}{\sqrt{LC}}$