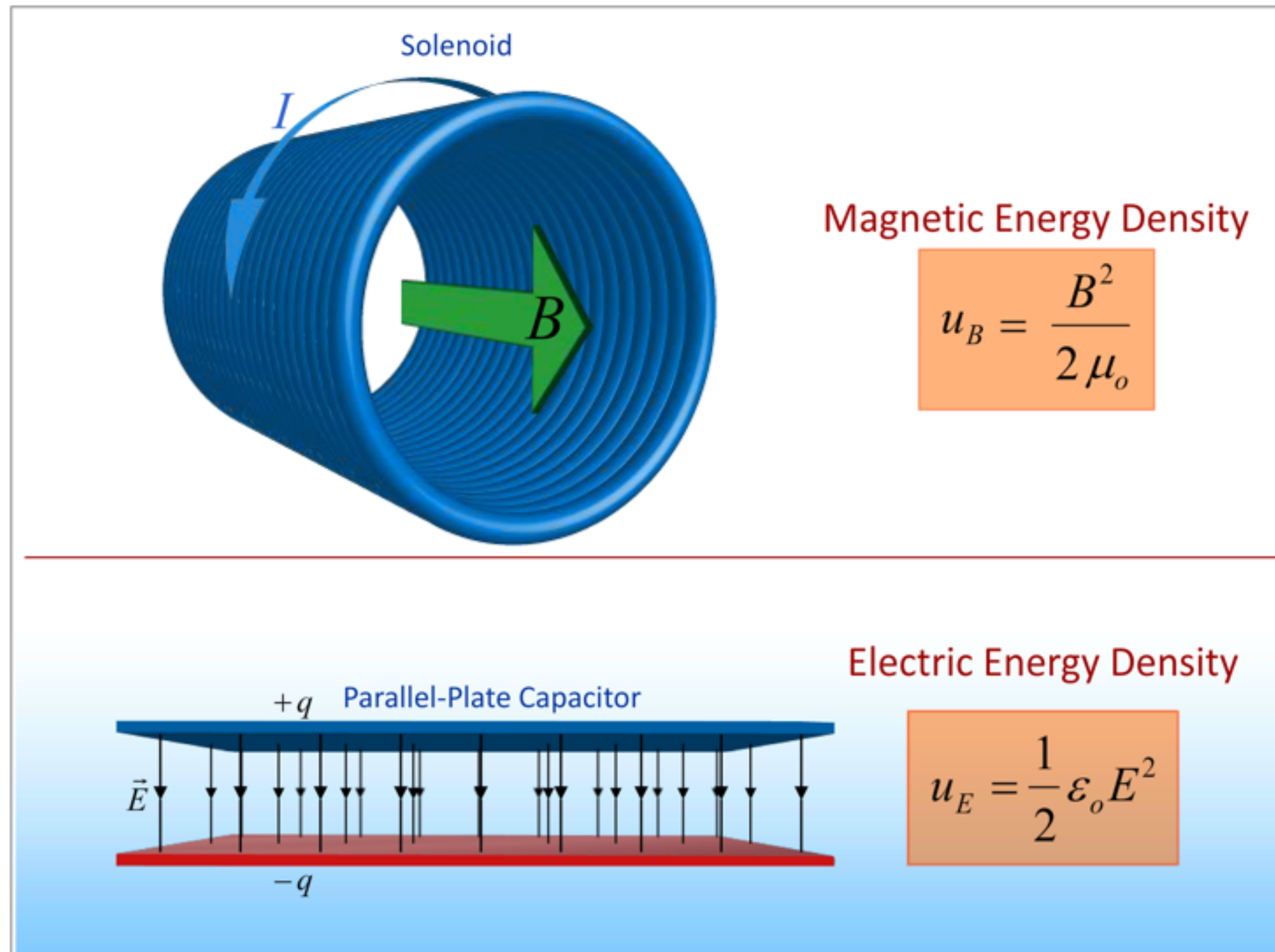



Where is the energy stored?




LC & RLC circuits

Lecture 23

LC Circuits

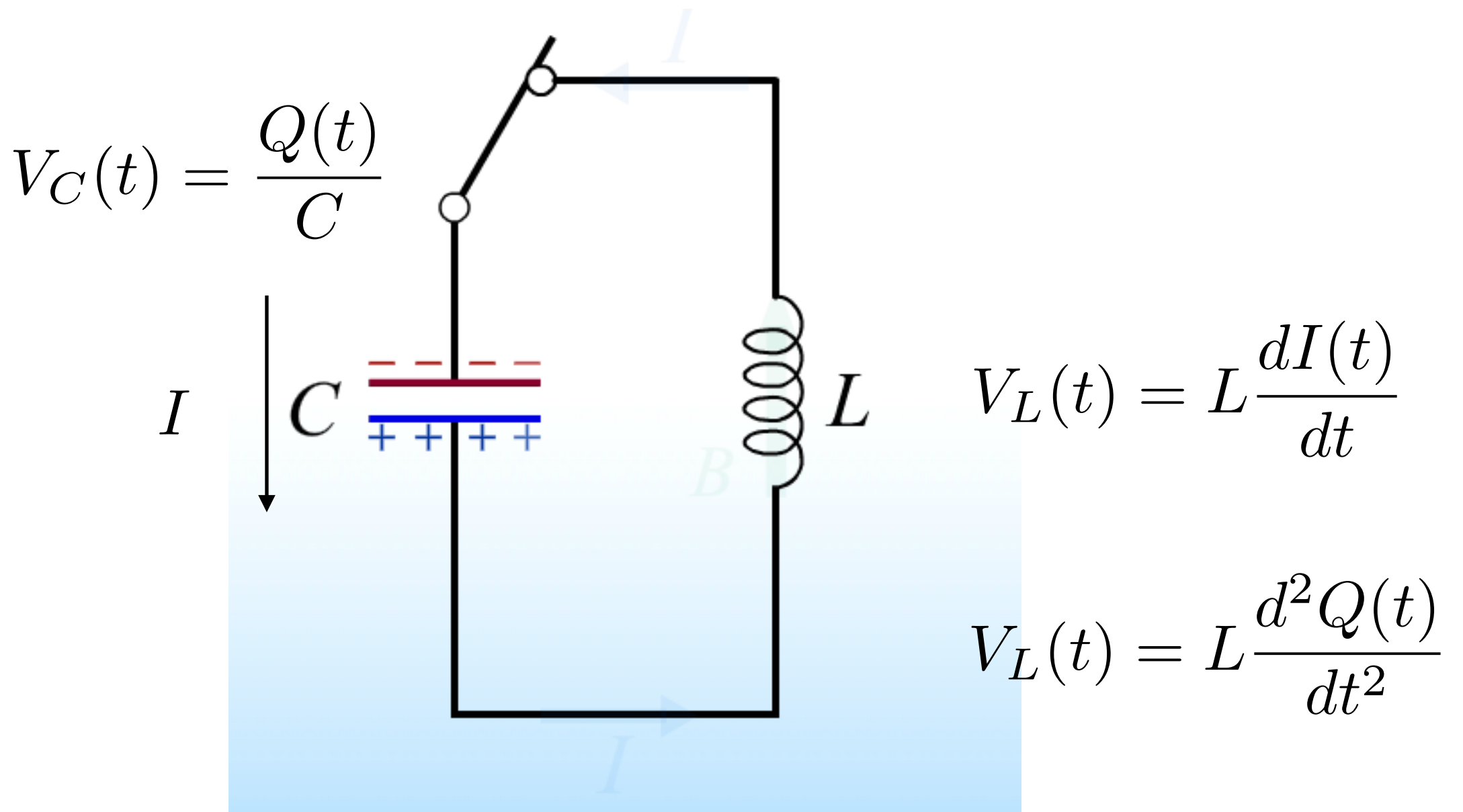


LC Circuits: Detailed Analysis

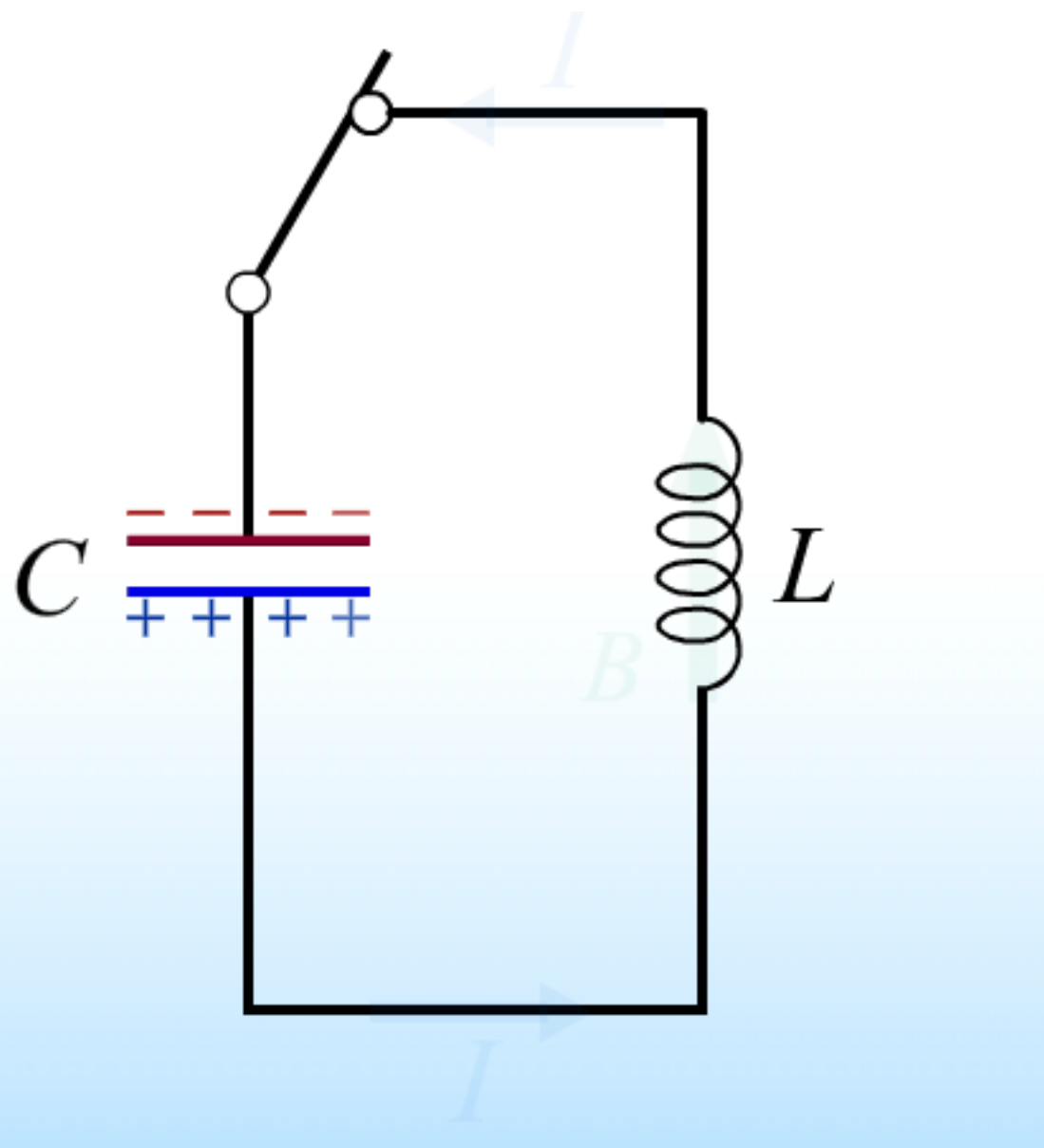

$$\text{KVL : } V_L(t) + V_C(t) = 0$$

$$0 = \frac{Q(t)}{C} + L \frac{d^2 Q(t)}{dt^2}$$


LC Circuits: Detailed Analysis

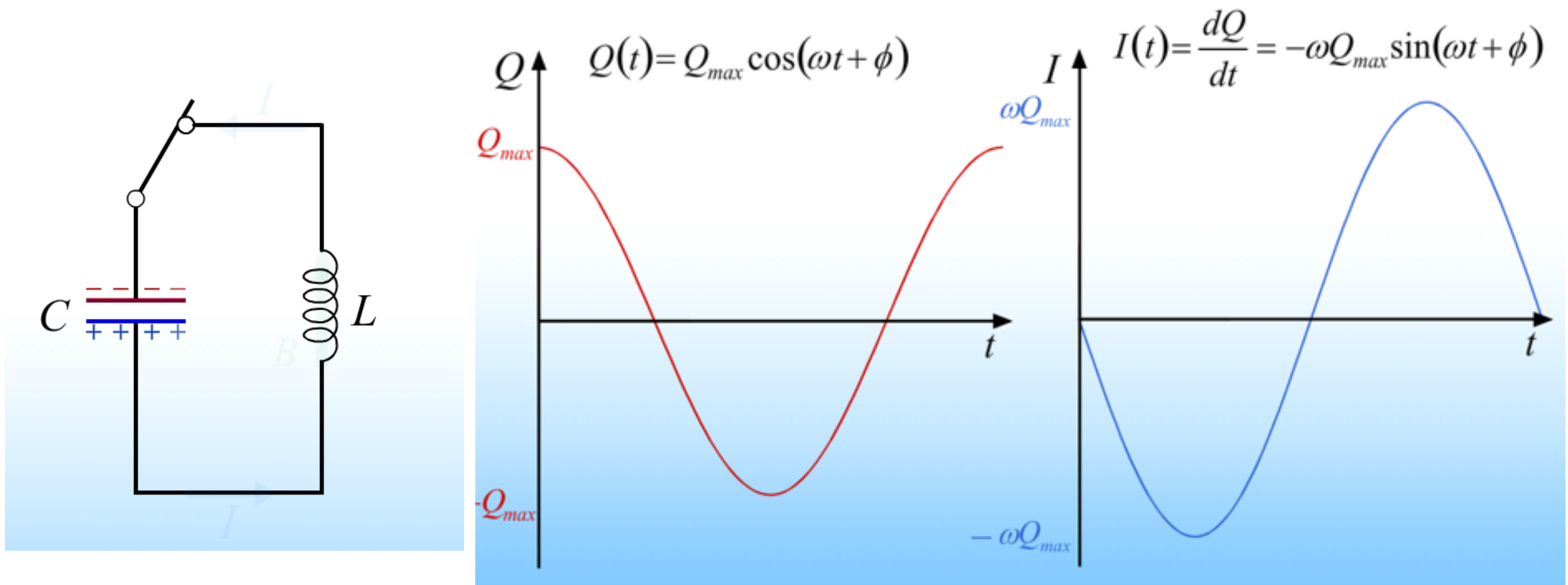

$$\omega = \sqrt{\frac{1}{LC}}$$

LC Circuits: Energy conservation

LR Circuit

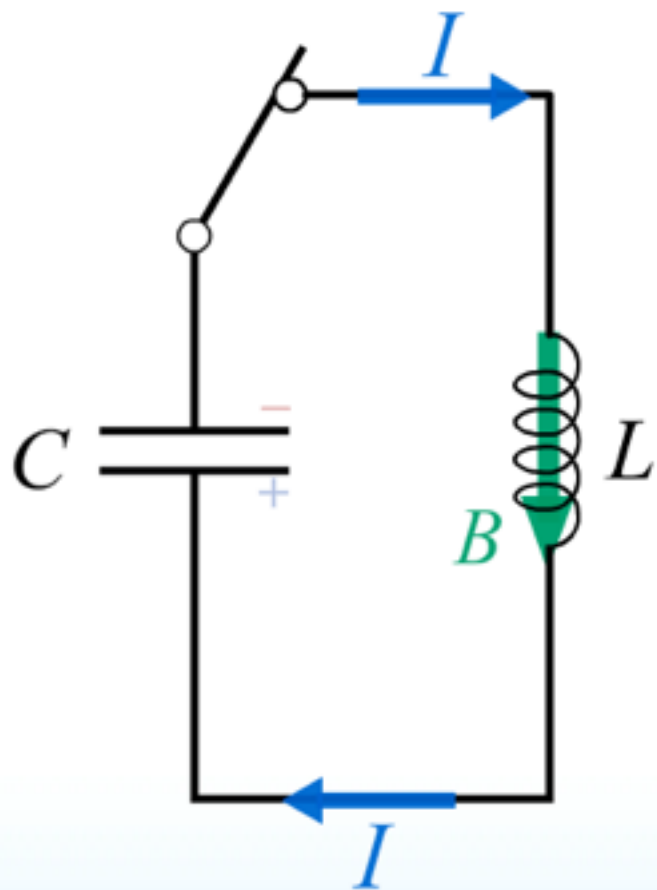

Inductor Energy

$$U_L = \frac{1}{2} LI^2$$



Kinetic Energy

$$K = \frac{1}{2} mv^2$$


Capacitor Energy

$$U_C = \frac{1}{2} \frac{Q^2}{C}$$



Spring Potential Energy

$$U_{spring} = \frac{1}{2} kx^2$$

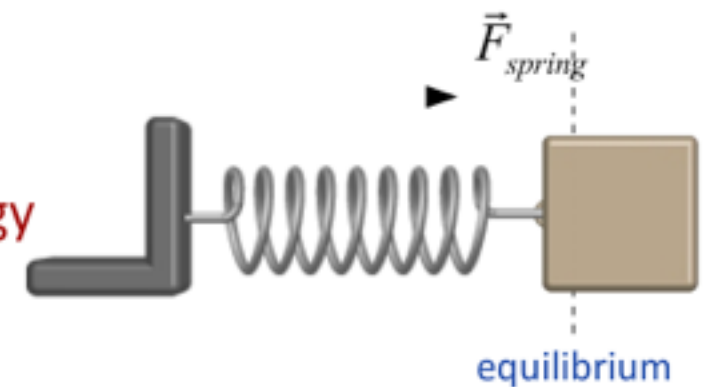


LRC Circuits

KVR

$$\frac{Q}{C} + R \frac{dQ}{dt} + L \frac{d^2 Q}{dt^2} = 0$$

Solution
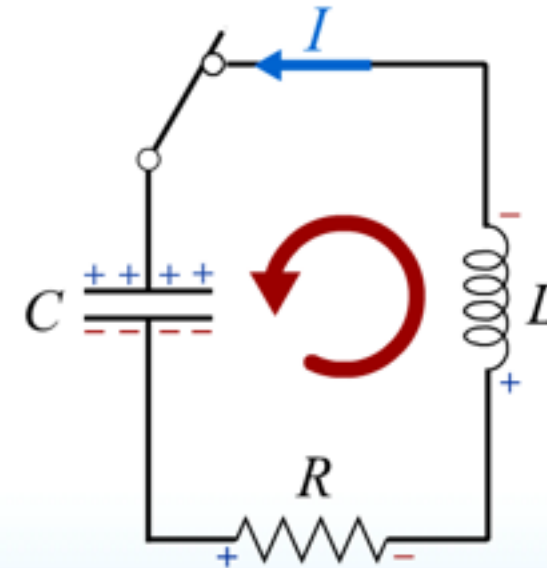
$$Q(t) = A e^{-\beta t} \cos(\omega' t + \phi)$$




Damping Factor $\beta = \frac{R}{2L}$

Oscillation Frequency $\omega'^2 = \omega_o^2 - \beta^2$

Natural Frequency $\omega_o = \frac{1}{\sqrt{LC}}$

LRC Circuits

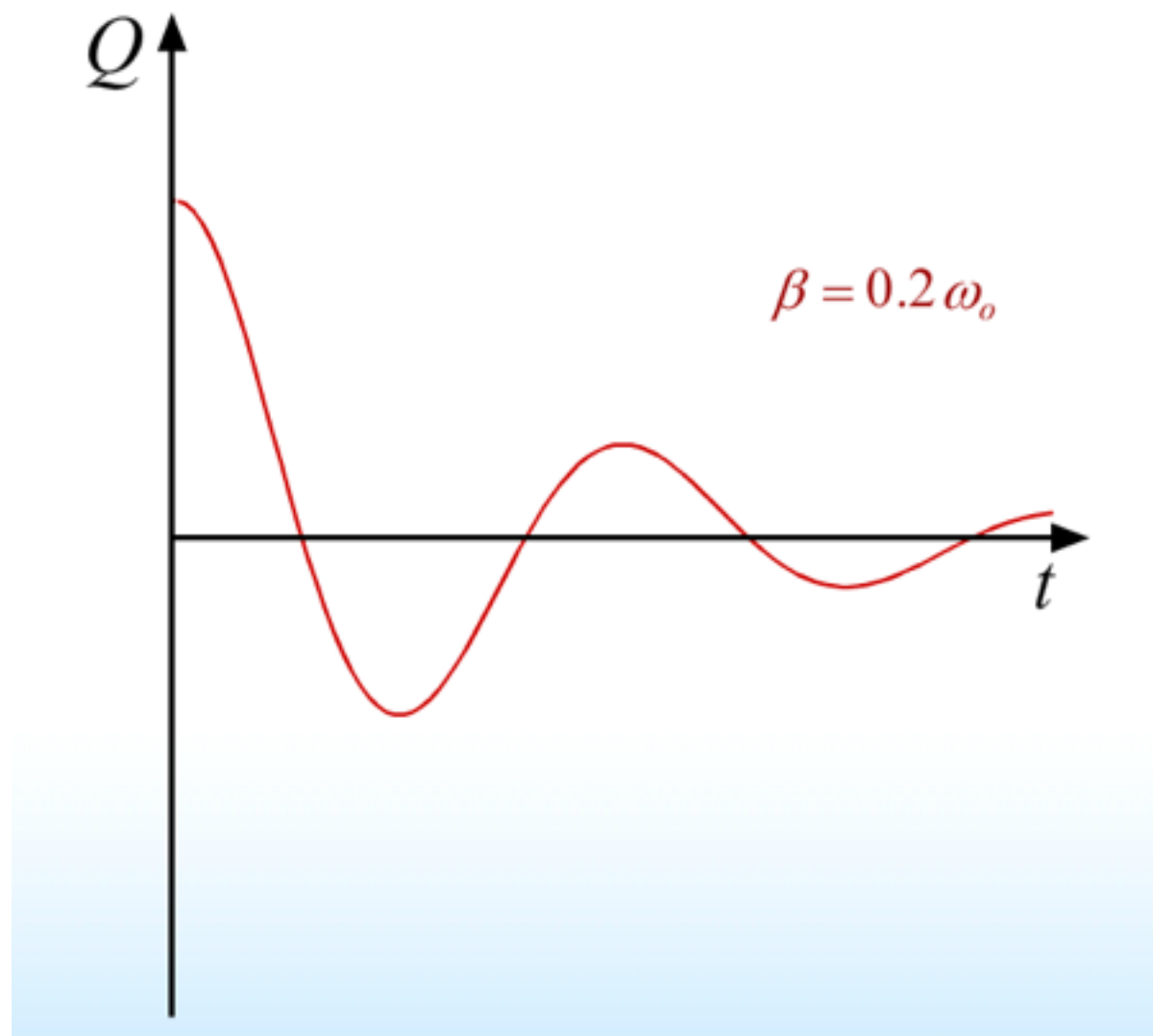

- Oscillations decay due to energy loss in the resistor!


MT2 Review

Lecture 24

Units Units Units


- Always Always Always convert to MKS
 - cm \rightarrow m
 - ms \rightarrow s
 - mA \rightarrow A
 - etc...

RC Circuits

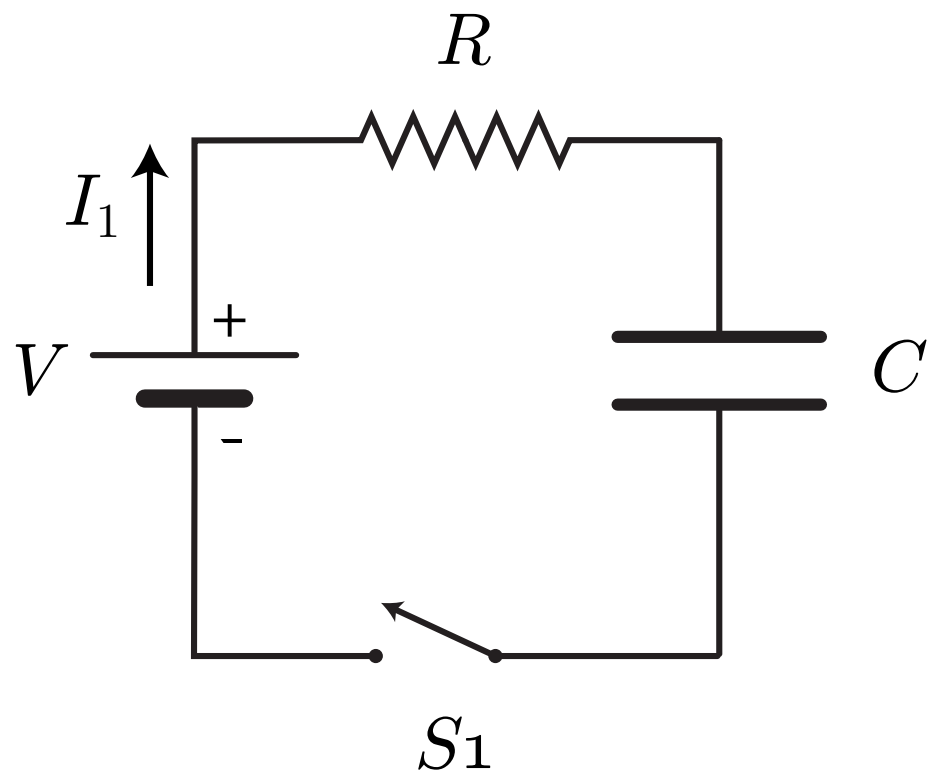


- C is uncharge at $t = 0$.
- What is the current the instant after S_1 is closed?
- Why?

RC Circuits

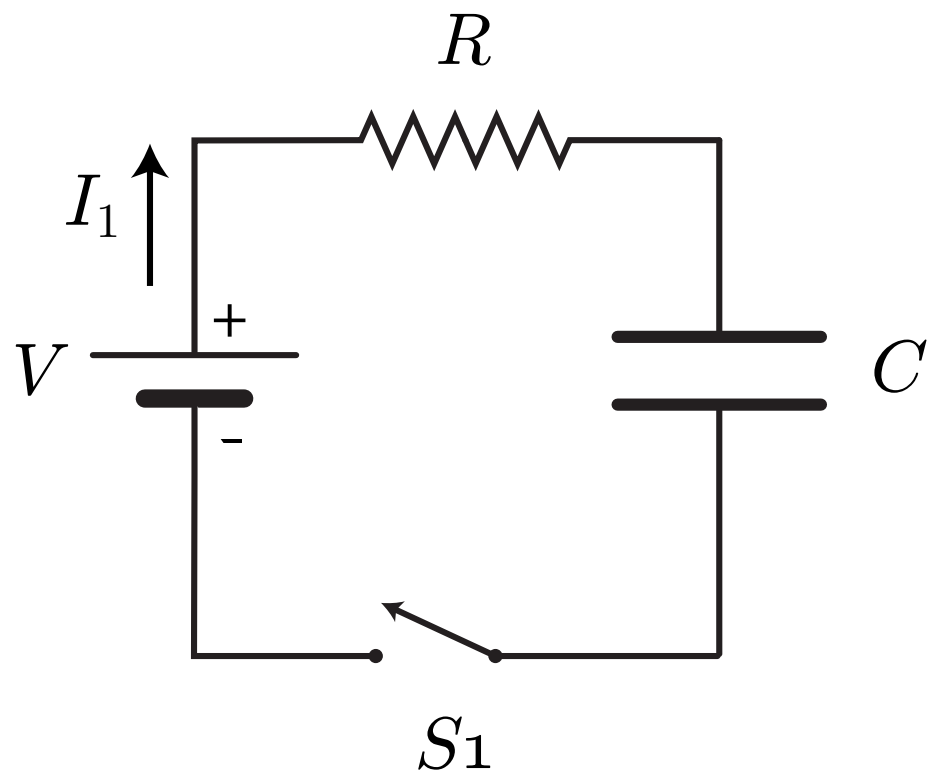


- C is uncharge at $t = 0$.
- What is the current at long times after S_1 is closed?
- Why?

RC Circuits

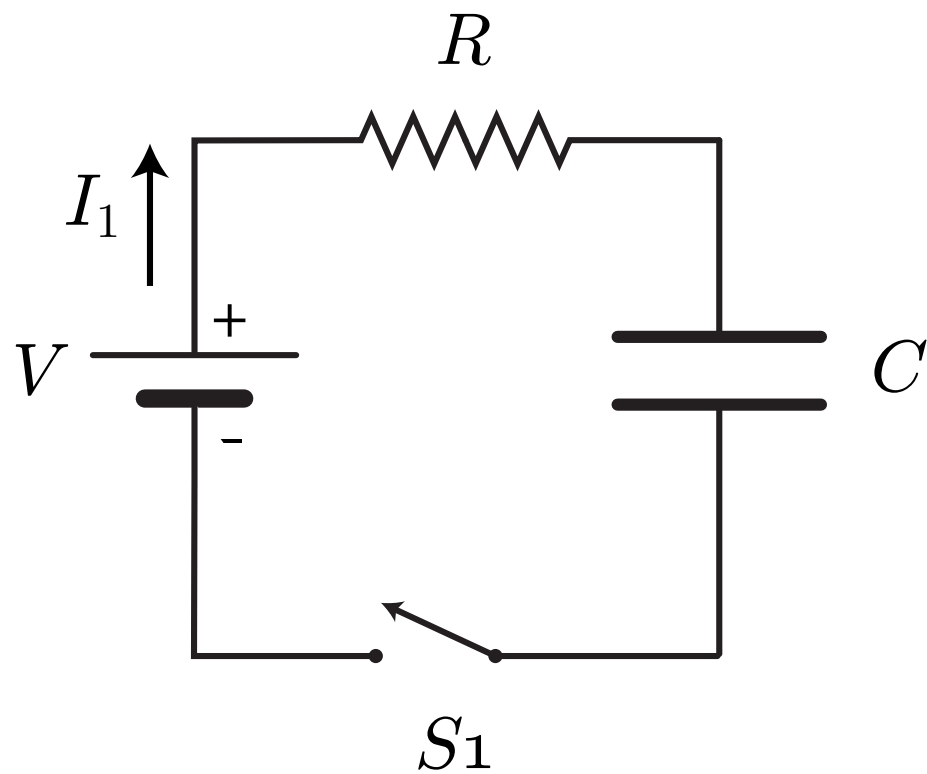


- C is uncharge at $t = 0$.
- What is the time constant?

RC Circuits

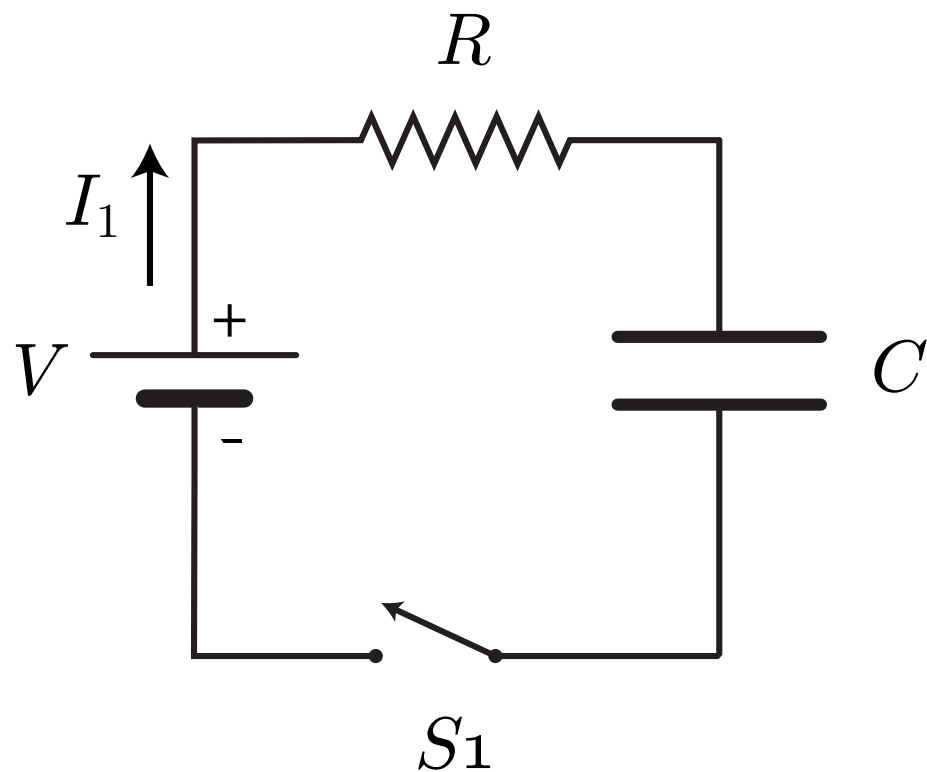


- C is uncharge at $t = 0$.
- Sketch the voltage across the capacitor as a function of time

RC Circuits

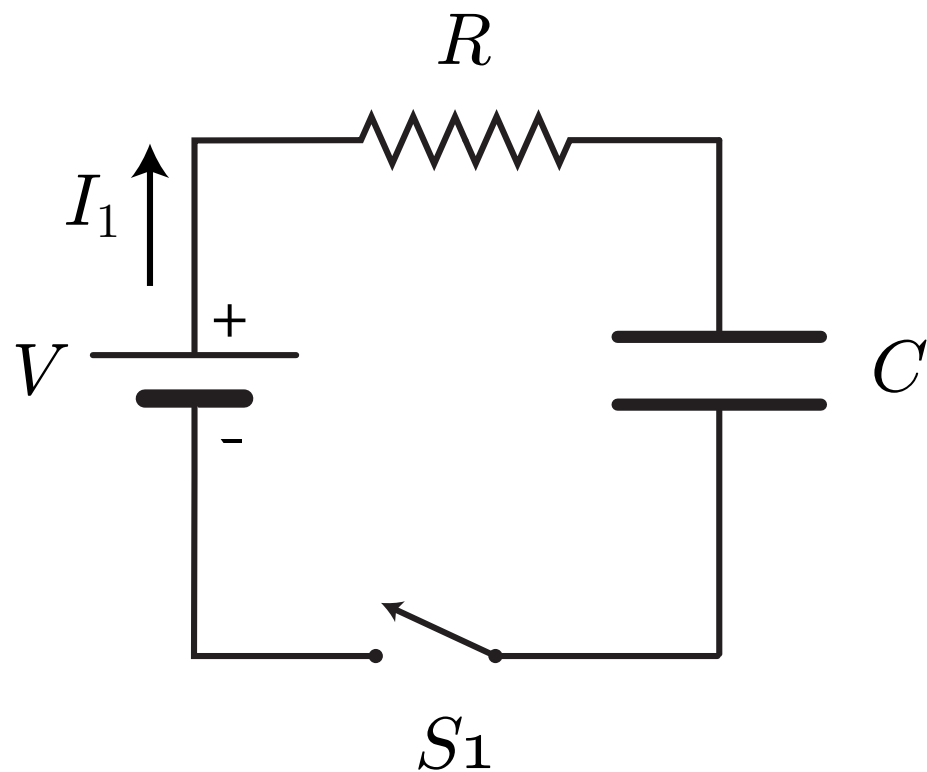

- If R is doubled, how should the components be changed to get the same $V_c(t)$ curve?
- Do $I(t)$ and $Q(t)$ change?

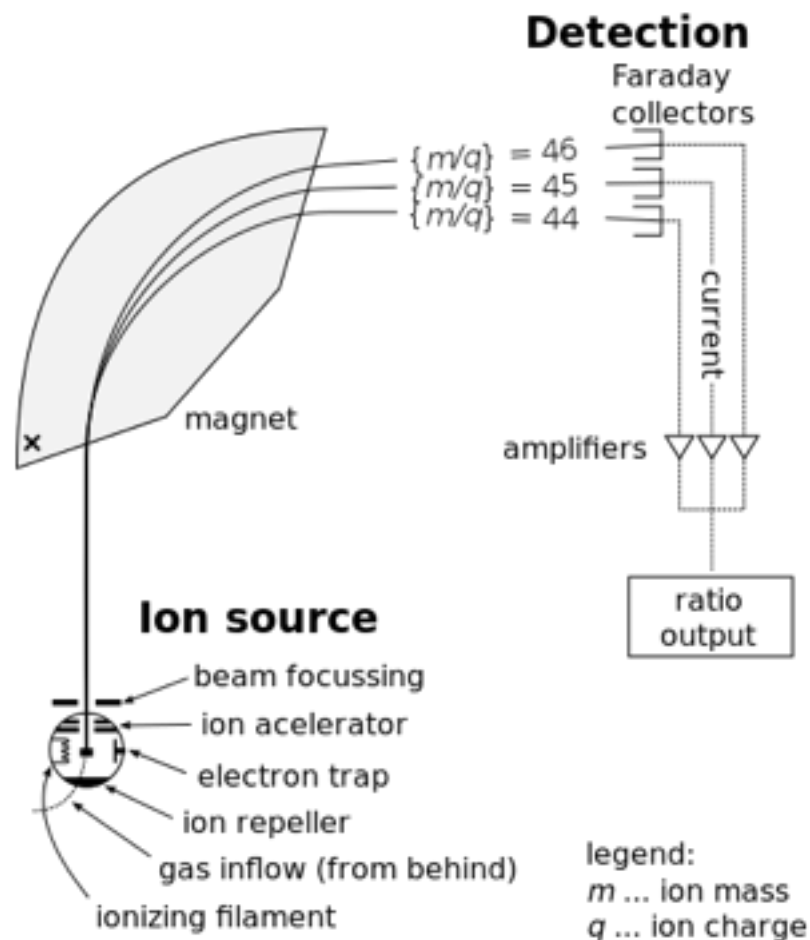
Charges Moving in a B Field: Mass Spectrometer



If the mass of the particle is doubled, how must the magnitude of the charge change such that the deflection of the particle is unchanged?


Charges Moving in a B Field: Velocity Selector

How does a velocity selector work?

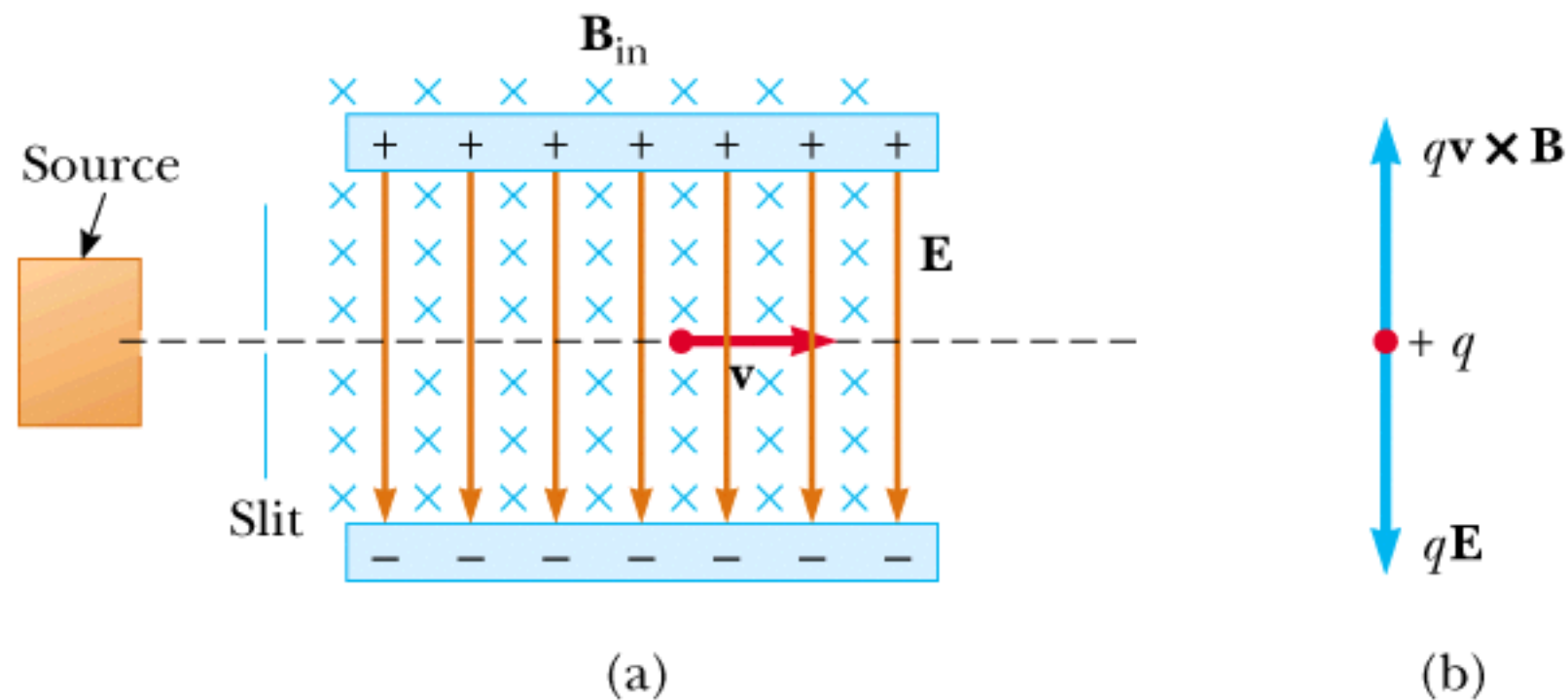

Charges Moving in a B Field

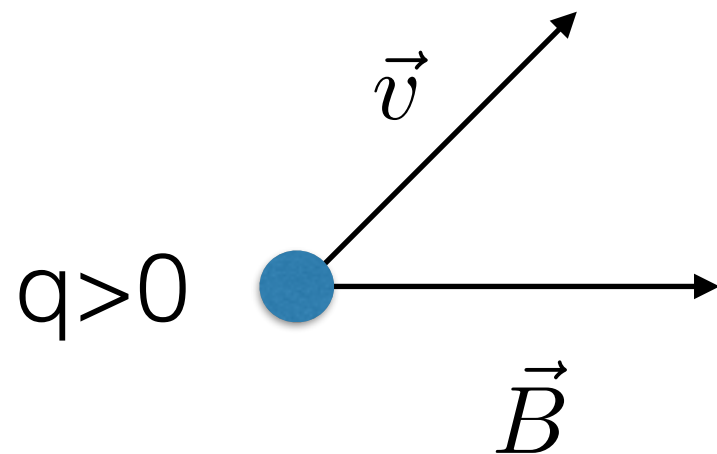
- What is the trajectory of this particle?



Ampère Law: Infinite Wire (1)

(Overhead)

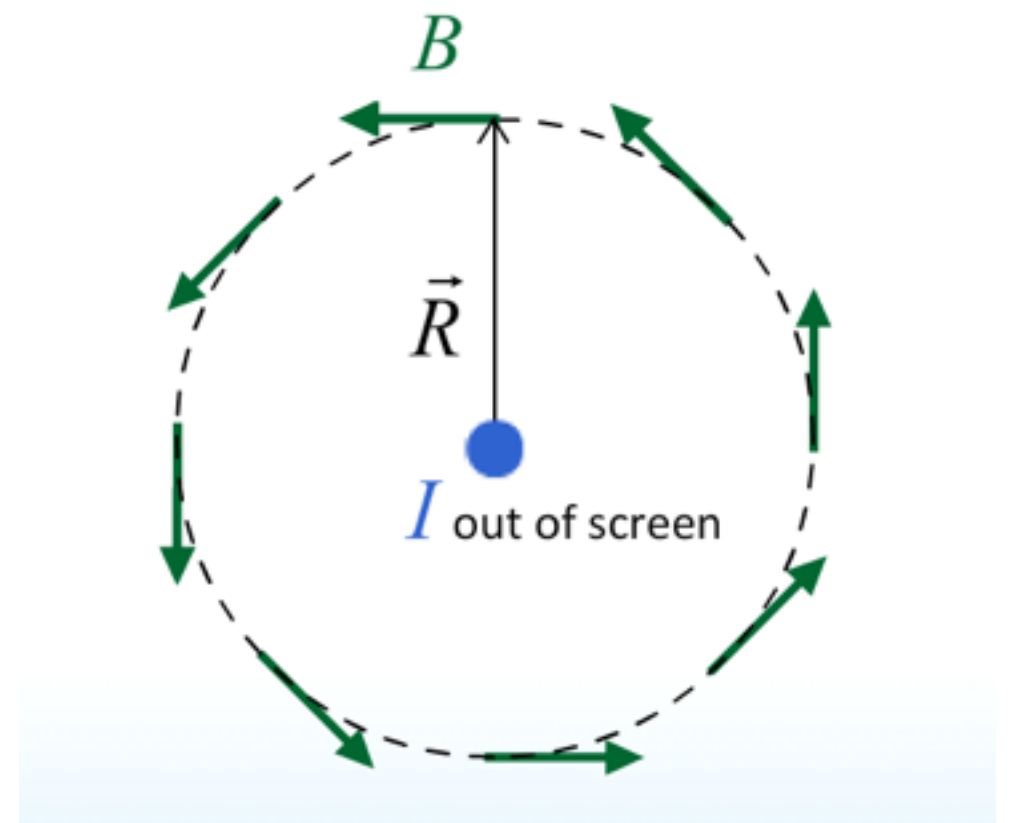
1. Identify **symmetry**
2. Draw B field/field lines
3. Choose a Ampère Loop
4. Compute B



$$B = \frac{\mu_0 I}{2\pi R}$$

Ampère Law: Weird Wires



I (out of the board)

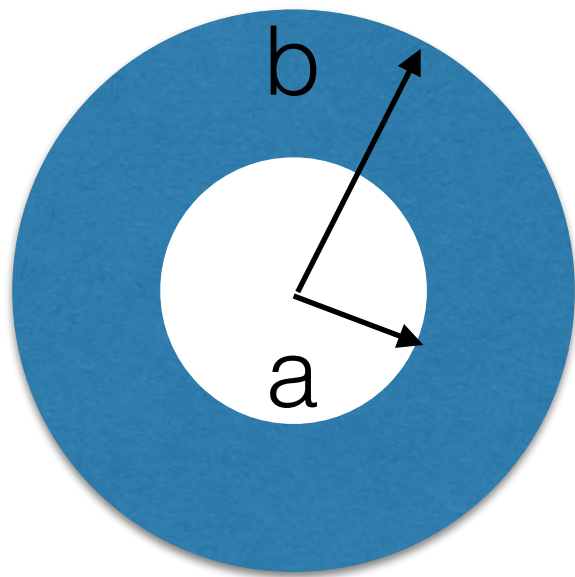


- A wire cross section is shown to the left. What is the B field as a function of the displacement r ?

Ampère Law: B field for an ∞ solenoid

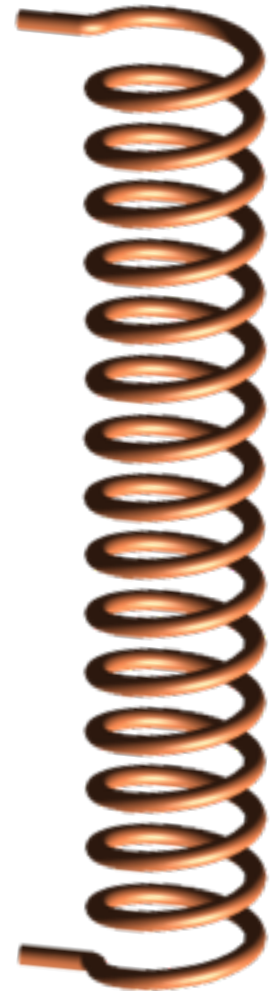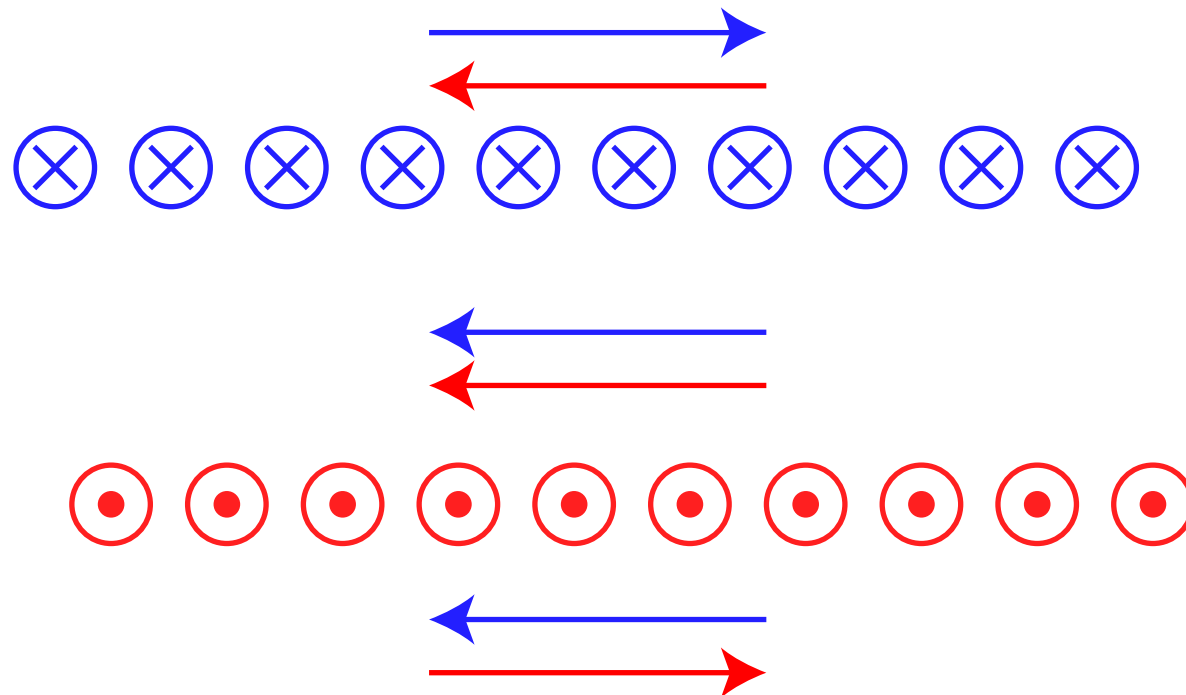
- Intuitive picture: \sim 2 infinite sheets



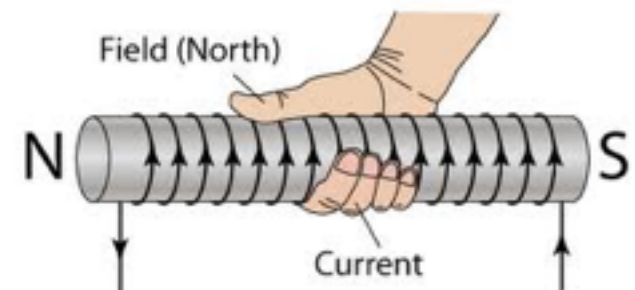- Field is \sim zero outside $B = \mu_0 n I$




AC circuits

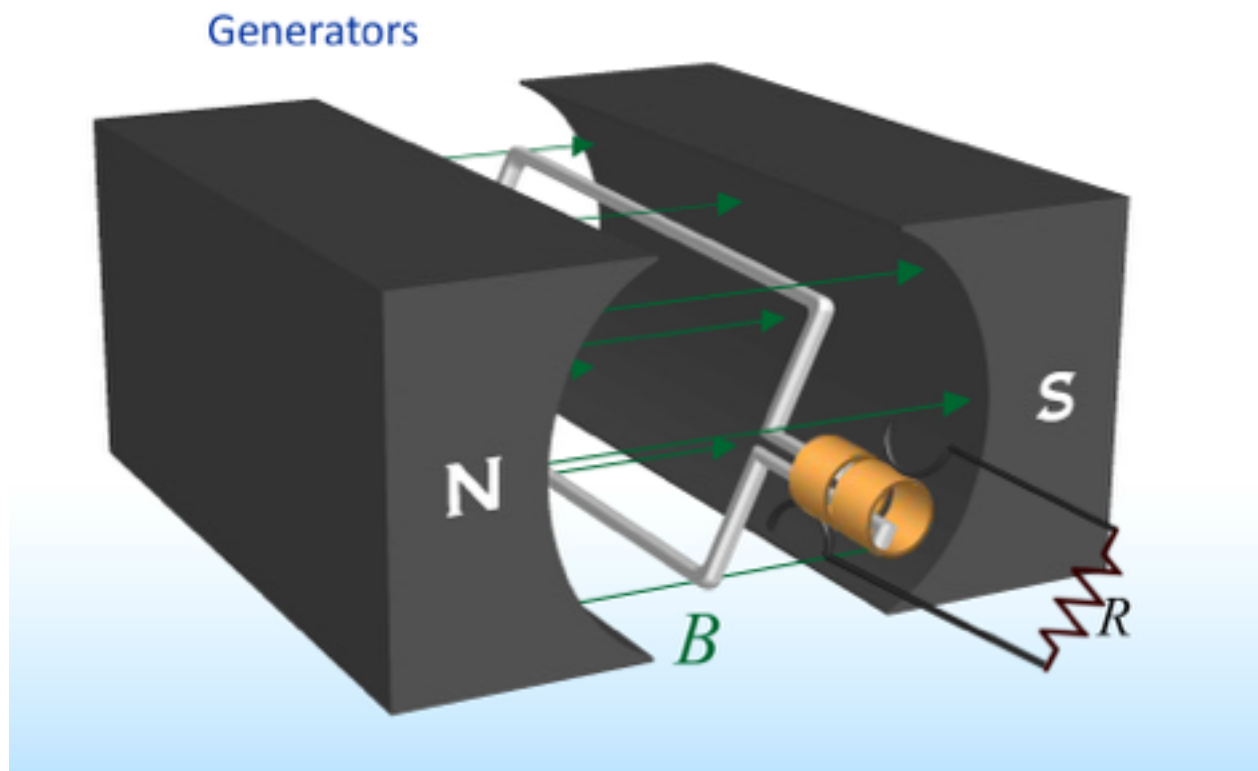

$$\mathcal{E}(t) = \mathcal{E}_{\max} \sin \omega t$$

Kircchoff Voltage Law (KVL):

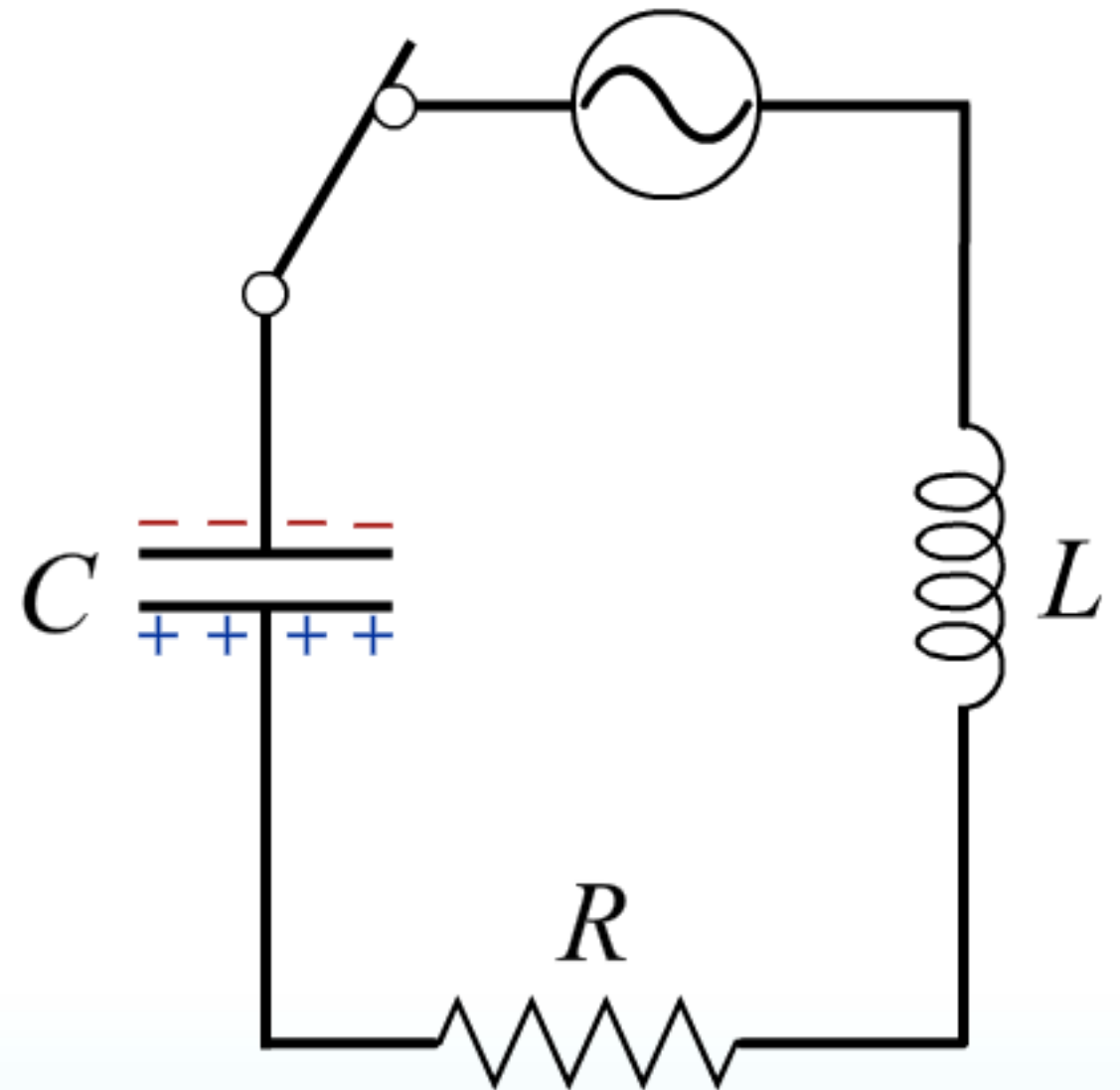

Phasors


- No one uses them...

$$V(t) = \mathcal{E}_{\max} \sin \omega t$$

- y-axis projection of the vector

$$\vec{V}(t) = \mathcal{E}_{\max} \cos \omega t \hat{i} + \mathcal{E}_{\max} \sin \omega t \hat{j}$$

Phasor Diagram

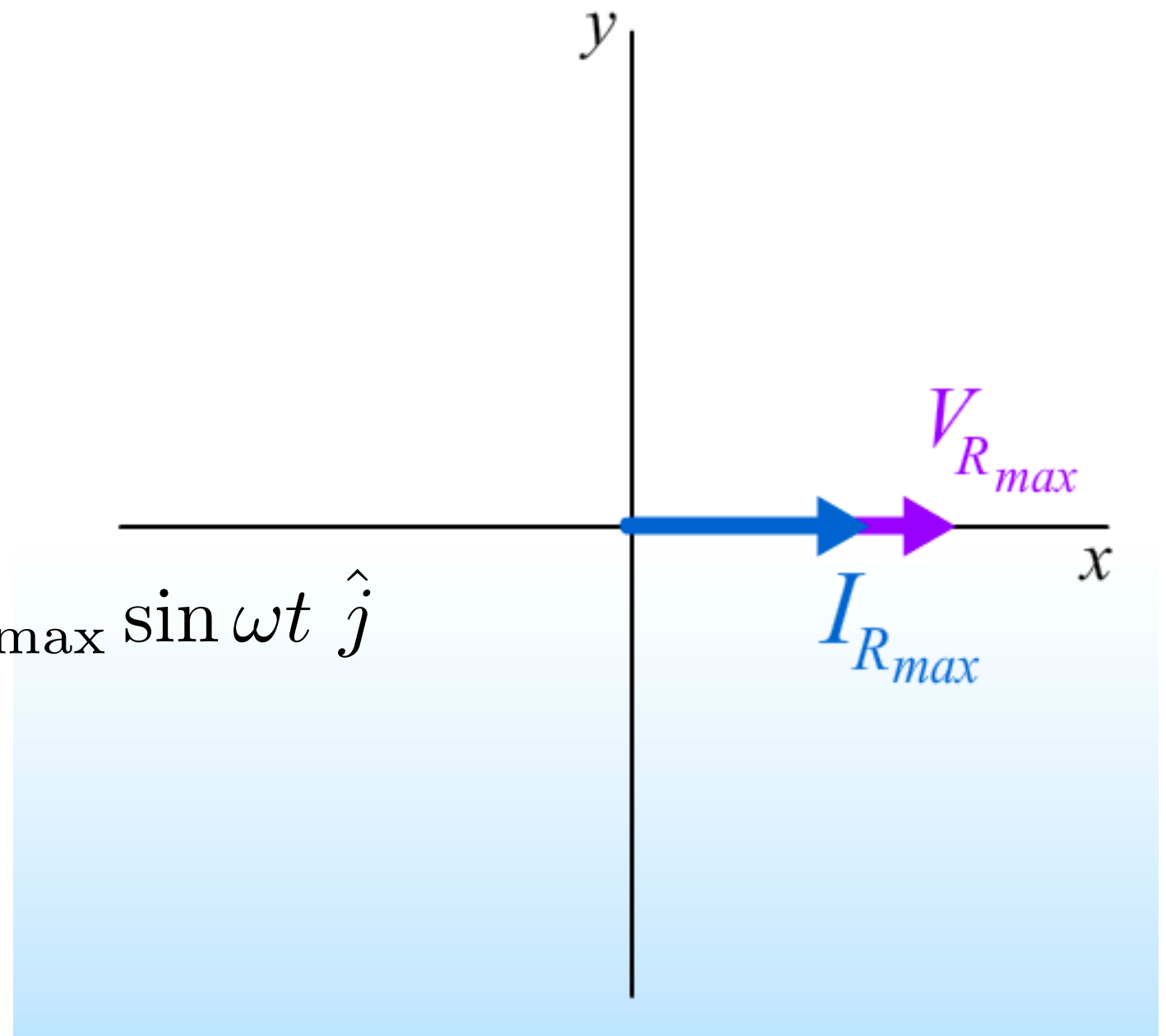


Phasors

- No one uses them...


$$V(t) = \mathcal{E}_{\max} \sin \omega t$$

- y-axis projection of the vector
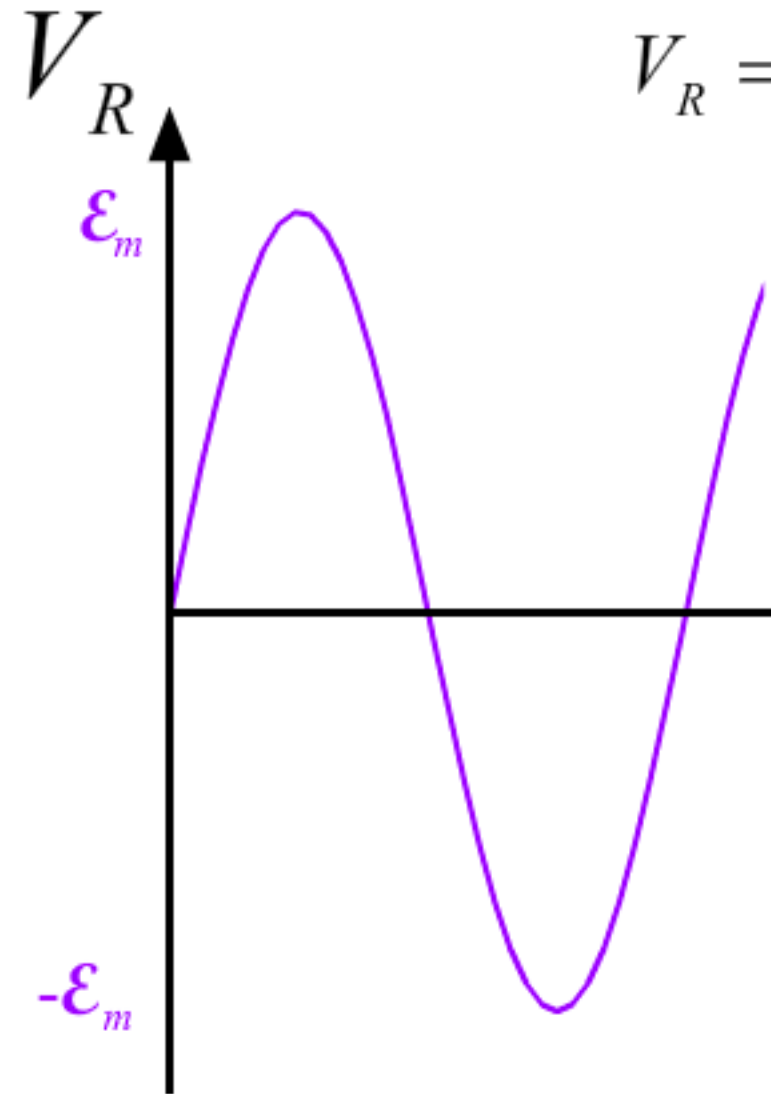
$$\vec{V}(t) = \mathcal{E}_{\max} \cos \omega t \hat{i} + \mathcal{E}_{\max} \sin \omega t \hat{j}$$



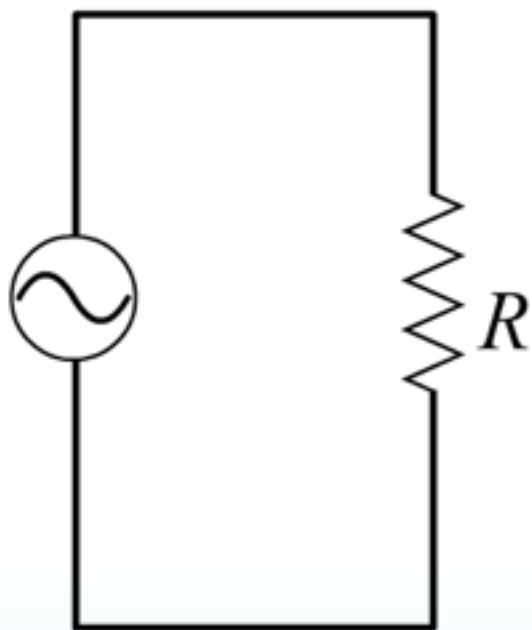
Overview of circuit components: Reactance



$$V = IR$$

$$I_R = \frac{\mathcal{E}_{\max}}{R} \sin \omega t$$


$$X_R = R$$

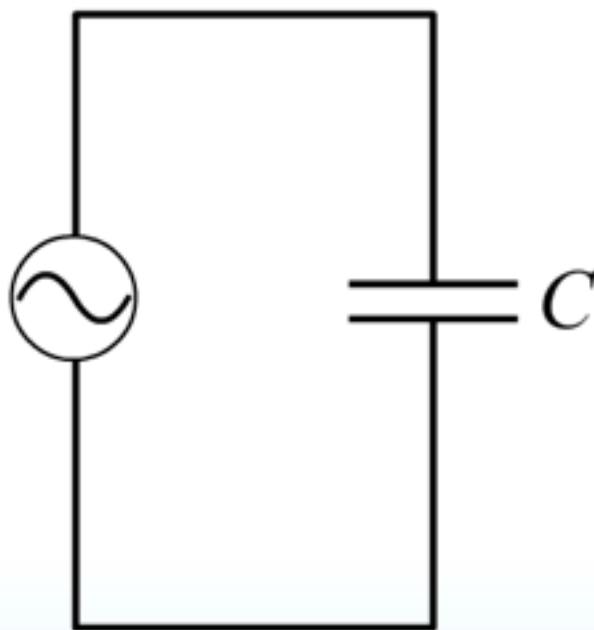

$$V = Q/C$$

$$I_C = \frac{\mathcal{E}_{\max}}{X_C} \cos \omega t$$

$$X_C = \frac{1}{\omega C}$$

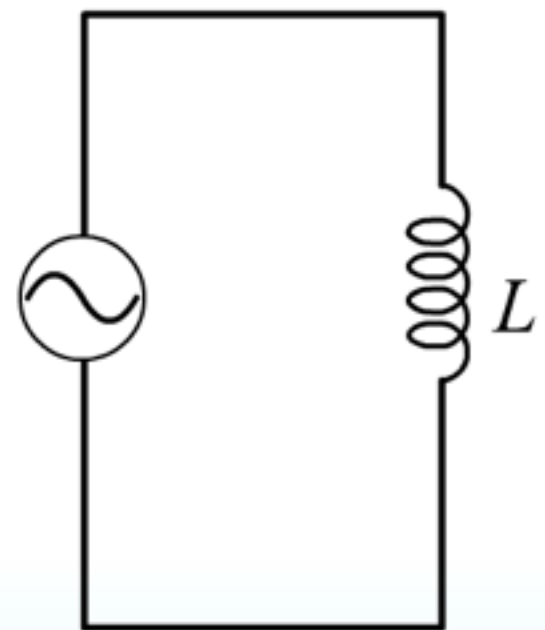


$$V = L \frac{dI}{dt}$$

$$I_L = -\frac{\mathcal{E}_{\max}}{X_L} \cos \omega t$$

$$X_L = \omega L$$

Resistor

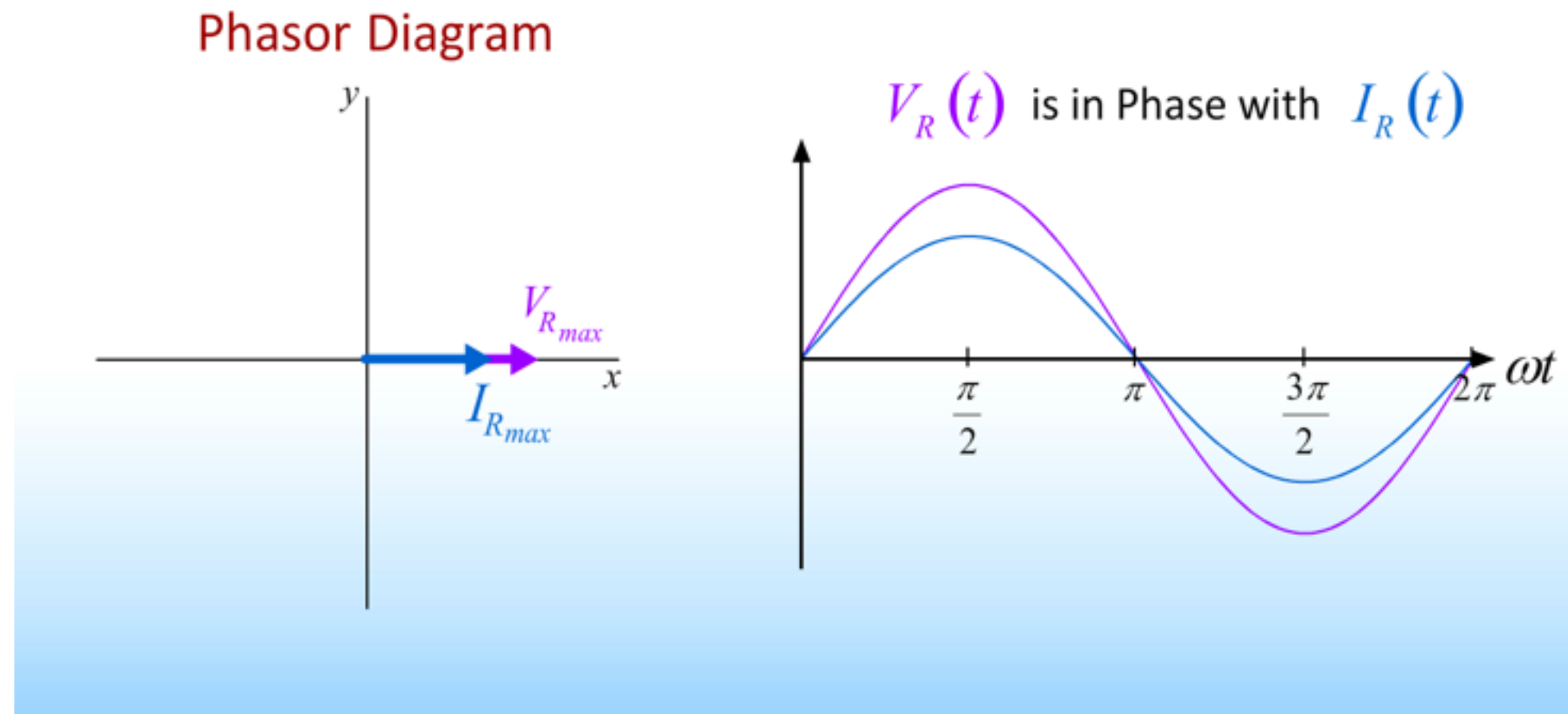


$$I_R = \frac{\mathcal{E}_{\max}}{R} \sin \omega t$$


$$\vec{I}_R(t) = \frac{\mathcal{E}_{\max}}{X_R} \left[\cos(\omega t) \hat{i} + \sin(\omega t) \hat{j} \right]$$

Capacitor

Phasor Diagram

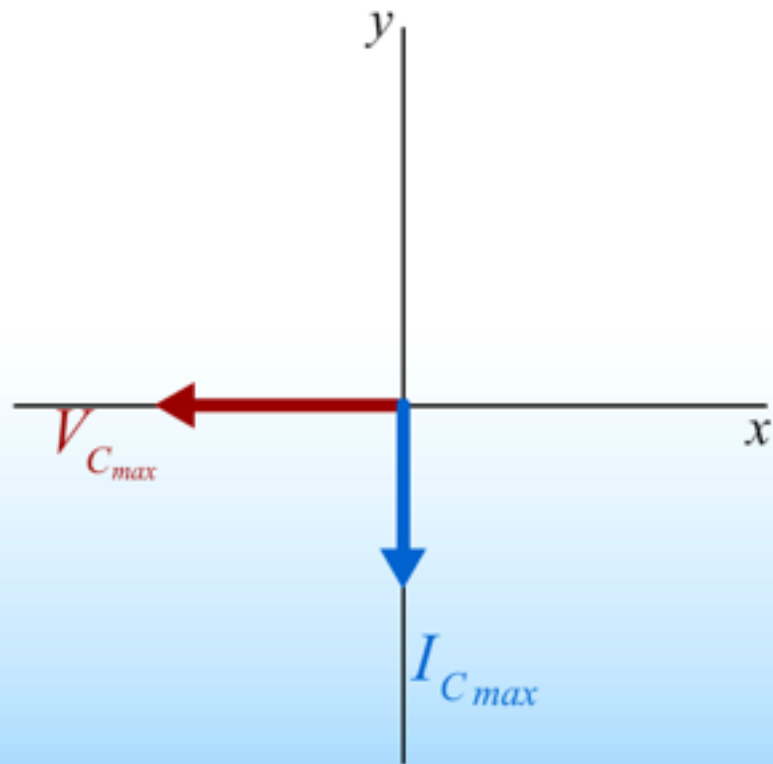

$V_C(t)$ lags $I_C(t)$ by 90°


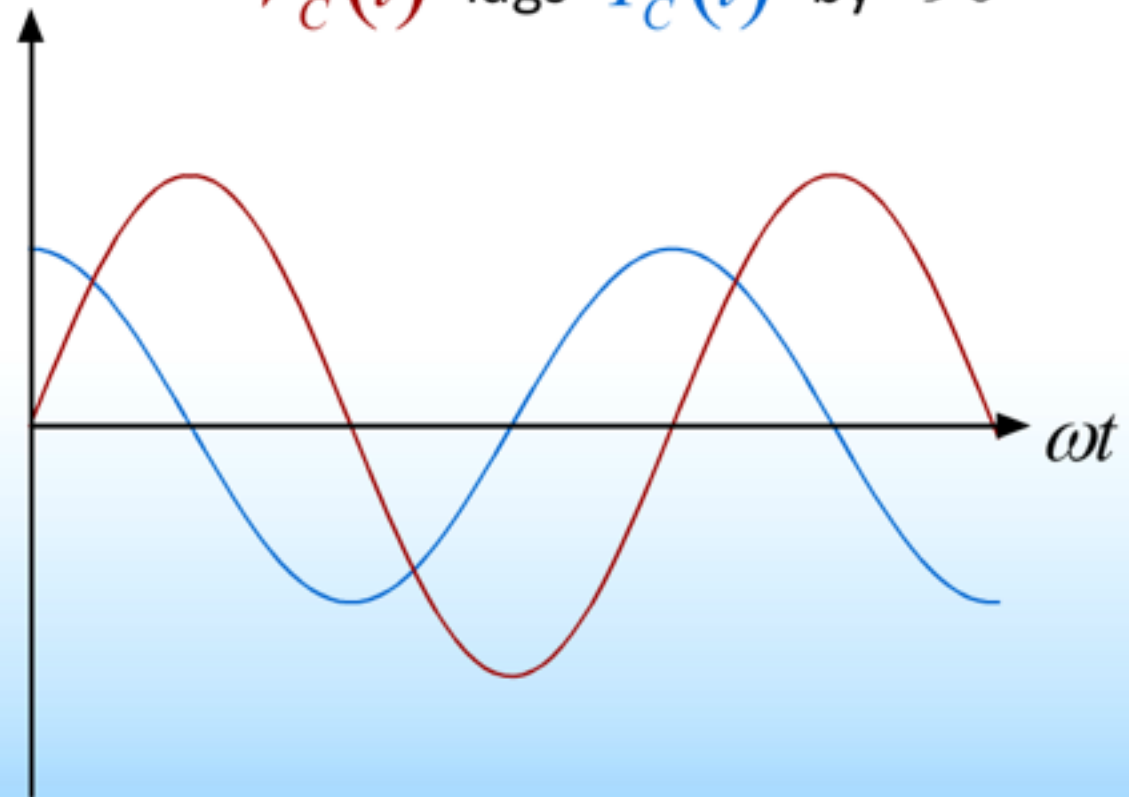


$$I_C = \frac{\mathcal{E}_{\max}}{X_C} \cos \omega t$$

$$\vec{I}_C(t) = \frac{\mathcal{E}_{\max}}{X_C} \left[\cos\left(\omega t + \frac{\pi}{2}\right) \hat{i} + \sin\left(\omega t + \frac{\pi}{2}\right) \hat{j} \right]$$

Inductor

Phasor Diagram

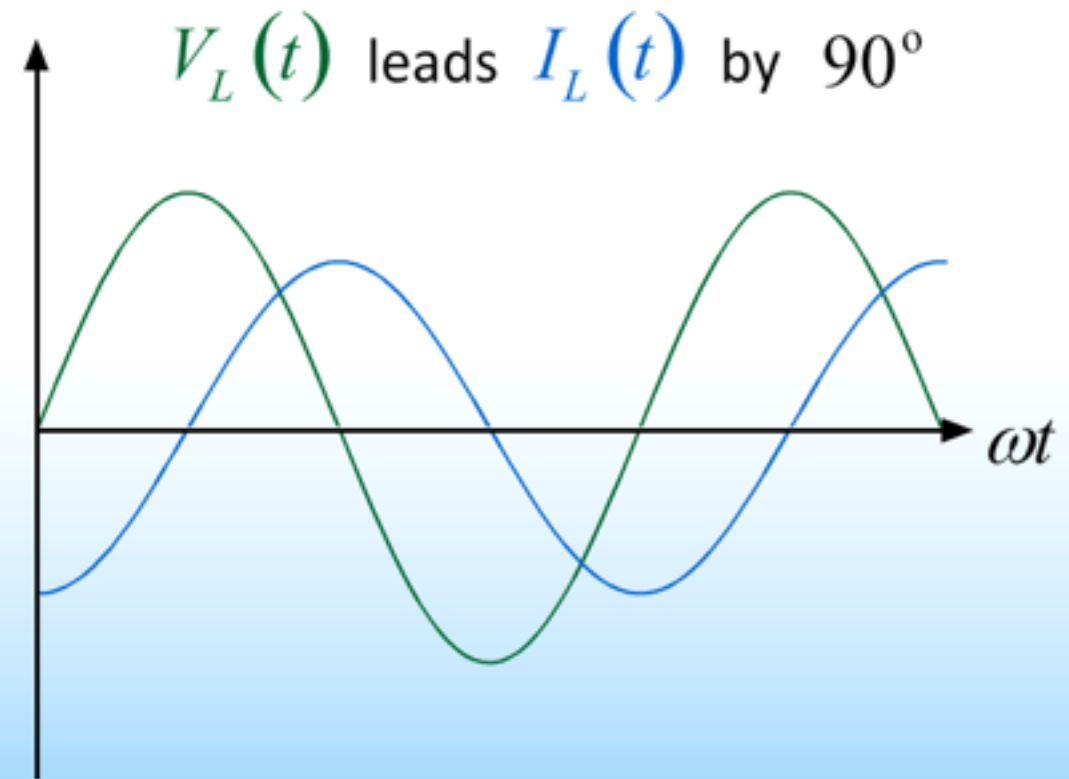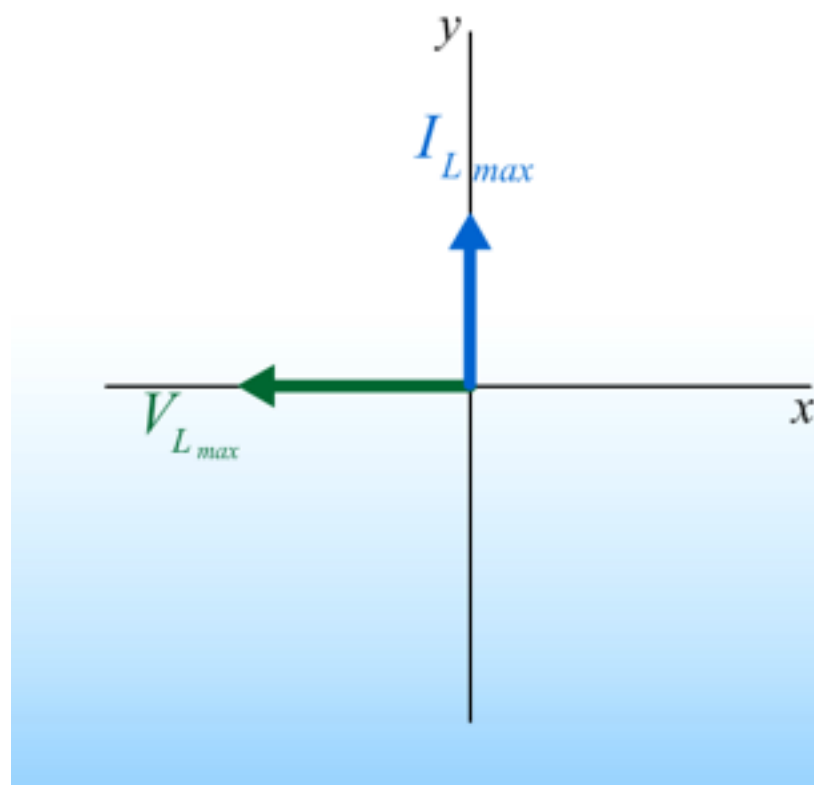

$$I_L = \frac{\mathcal{E}_{\max}}{X_L} \cos \omega t$$

$$\vec{I}_L(t) = \frac{\mathcal{E}_{\max}}{X_L} \left[\cos\left(\omega t - \frac{\pi}{2}\right) \hat{i} + \sin\left(\omega t - \frac{\pi}{2}\right) \hat{j} \right]$$

Putting it all together...

Current


$$I = I_m \sin(\omega t - \phi)$$

KVR

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} - \mathcal{E}_m \sin(\omega t) = 0$$

- Unknowns:

$$I_{\max}, \quad \phi$$

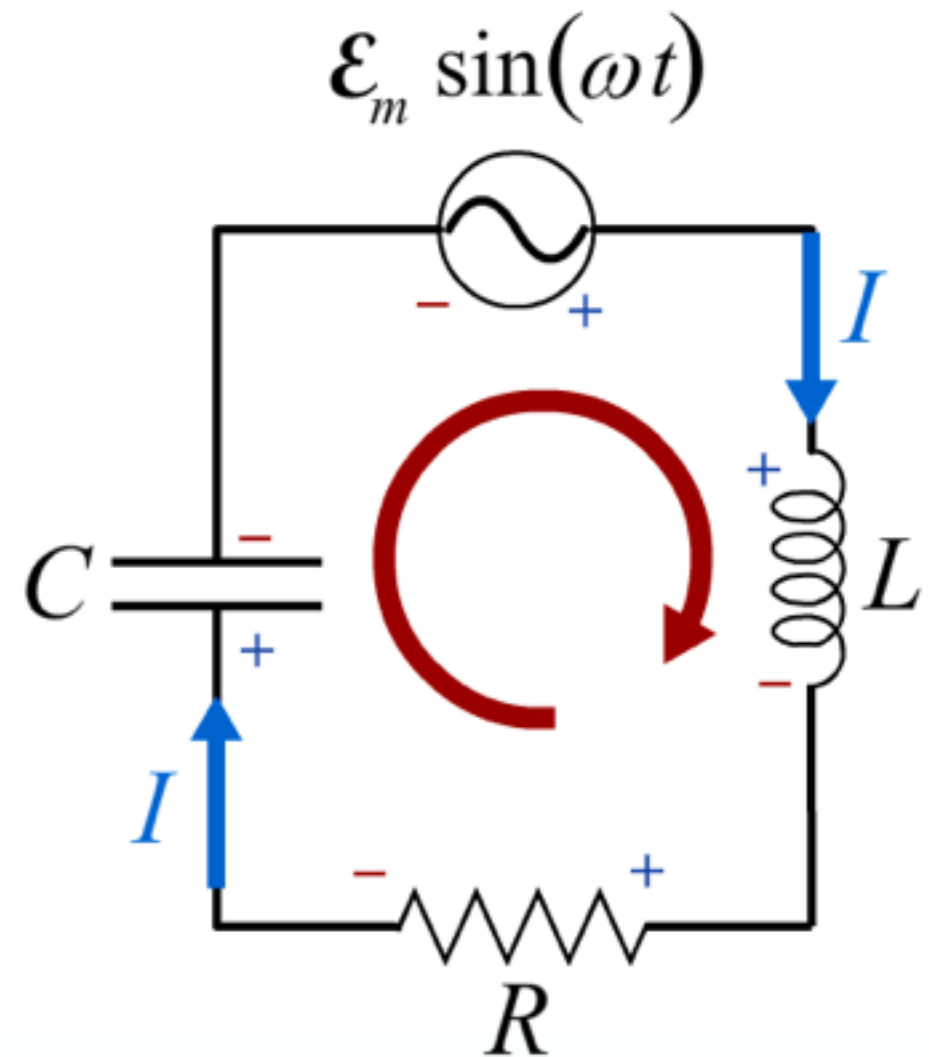

Putting it all together...

- Unknowns:

$$I_{\max}, \phi$$

- Choose unknowns such that:

$$\vec{V}_R + \vec{V}_C + \vec{V}_L = \vec{\mathcal{E}}$$

- Result:

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$I_{\max} = \frac{\mathcal{E}_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Phasor Diagram

