


RLC & AC circuits

Lecture 26


Announcements

- Reading for Wednesday: 29-5 to 29-6
- Exam pickup: Wednesday

LC Circuits

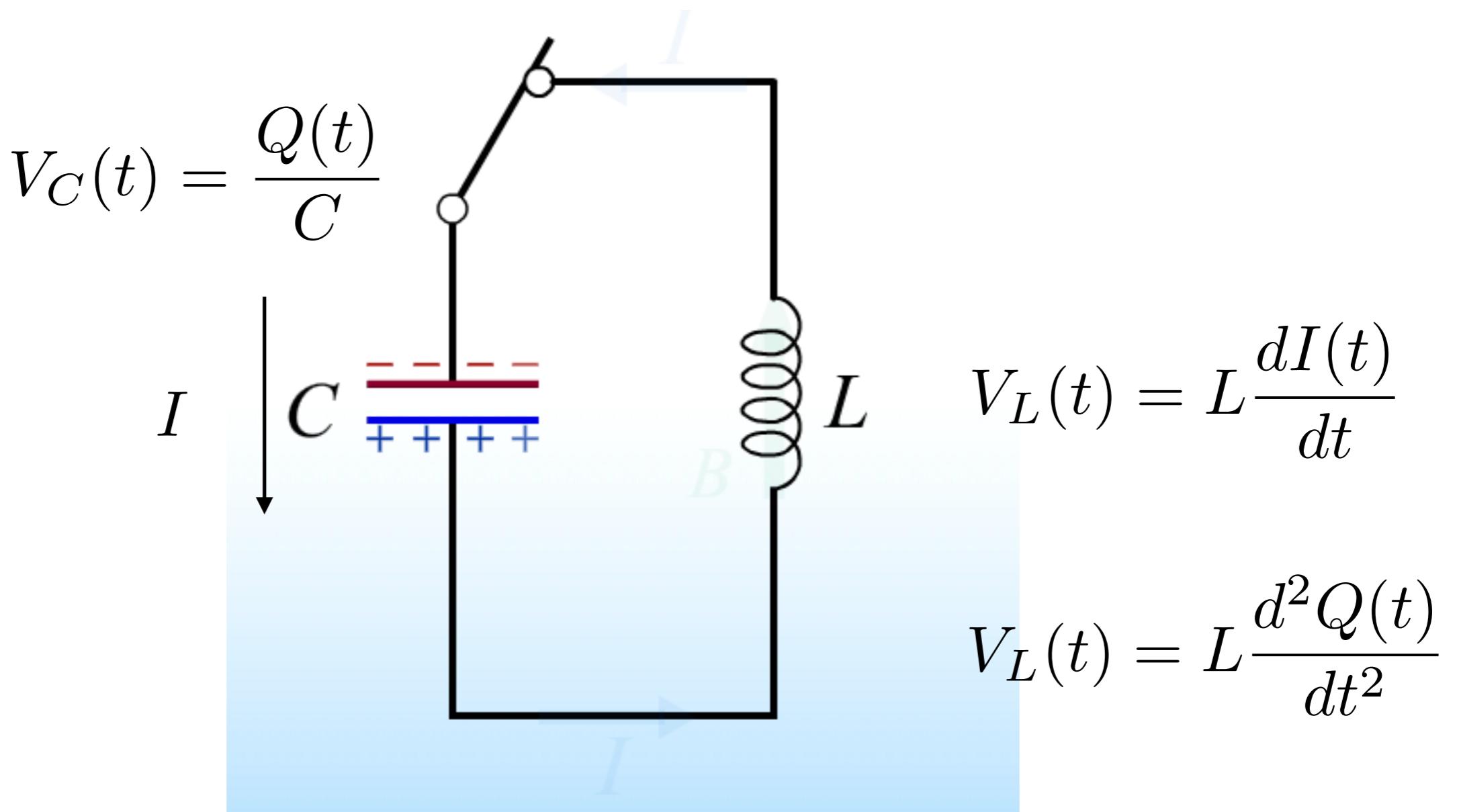



LC Circuits: Detailed Analysis

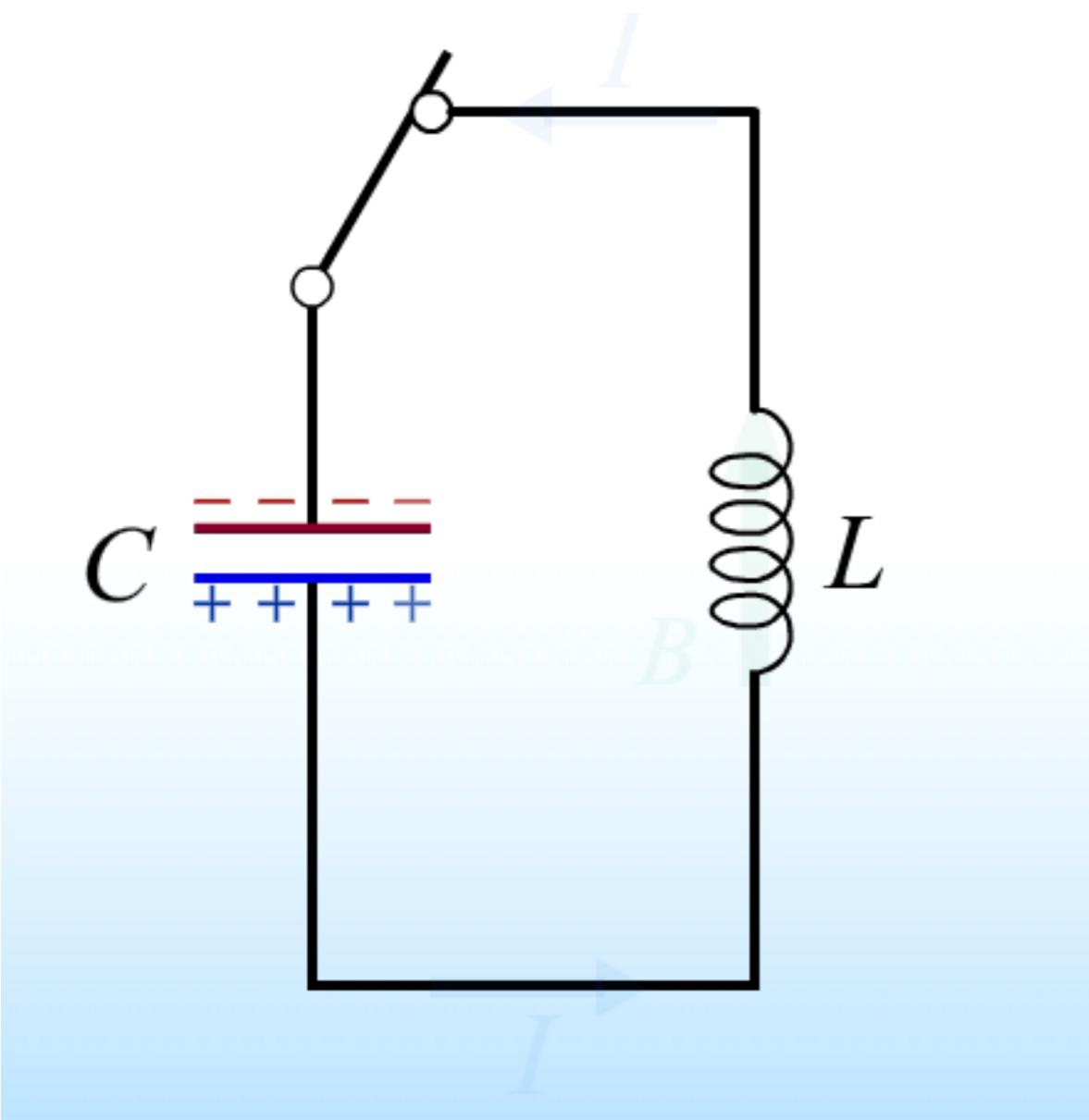

$$\text{KVL : } V_L(t) + V_C(t) = 0$$

$$0 = \frac{Q(t)}{C} + L \frac{d^2 Q(t)}{dt^2}$$


LC Circuits: Detailed Analysis

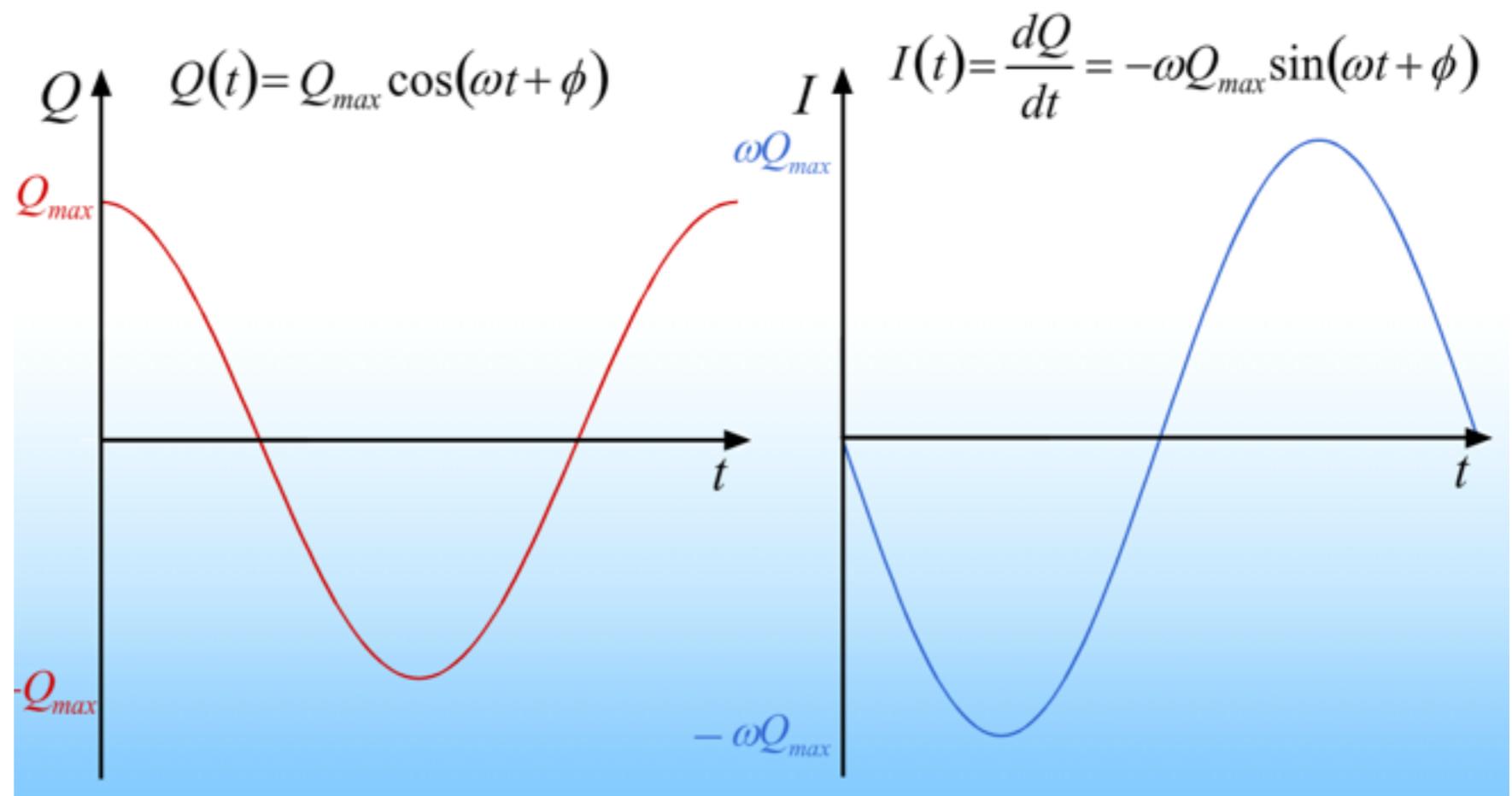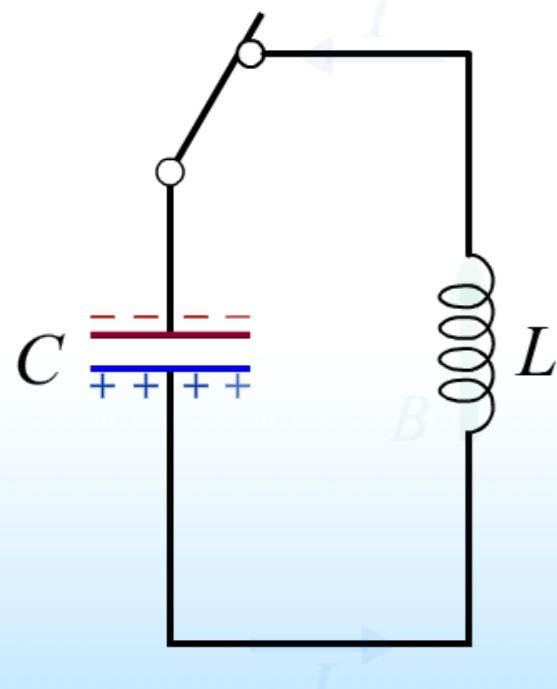

$$\omega = \sqrt{\frac{1}{LC}}$$

LC Circuits: Energy conservation

LR Circuit

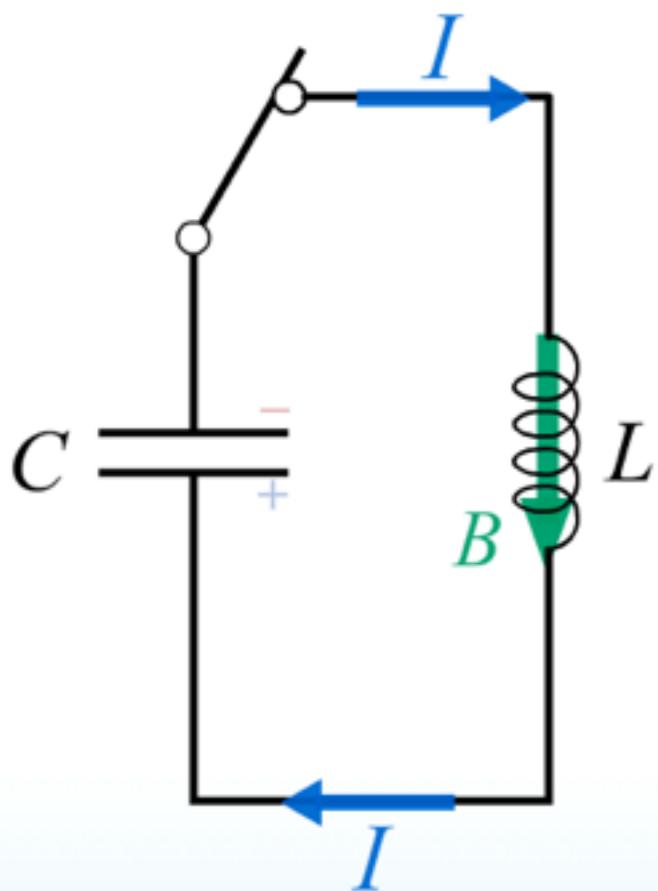


Inductor Energy

$$U_L = \frac{1}{2} LI^2 \longrightarrow K = \frac{1}{2} mv^2$$

Capacitor Energy

$$U_C = \frac{1}{2} \frac{Q^2}{C} \longrightarrow U_{spring} = \frac{1}{2} kx^2$$

Oscillating Block

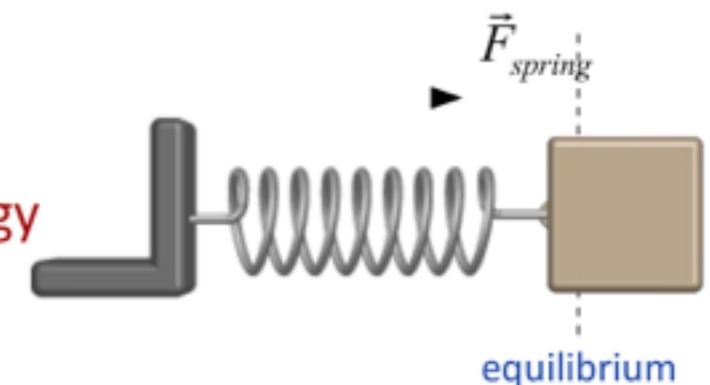


LRC Circuits

KVR

$$\frac{Q}{C} + R \frac{dQ}{dt} + L \frac{d^2Q}{dt^2} = 0$$

Solution
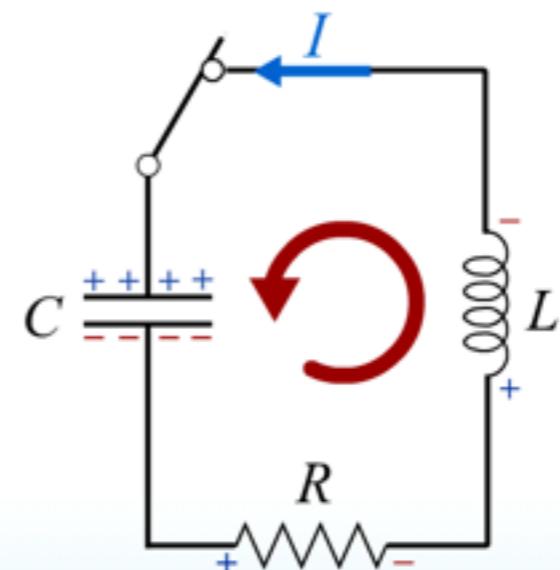
$$Q(t) = A e^{-\beta t} \cos(\omega' t + \phi)$$




Damping Factor $\beta = \frac{R}{2L}$

Oscillation Frequency $\omega'^2 = \omega_o^2 - \beta^2$

Natural Frequency $\omega_o = \frac{1}{\sqrt{LC}}$


LRC Circuits

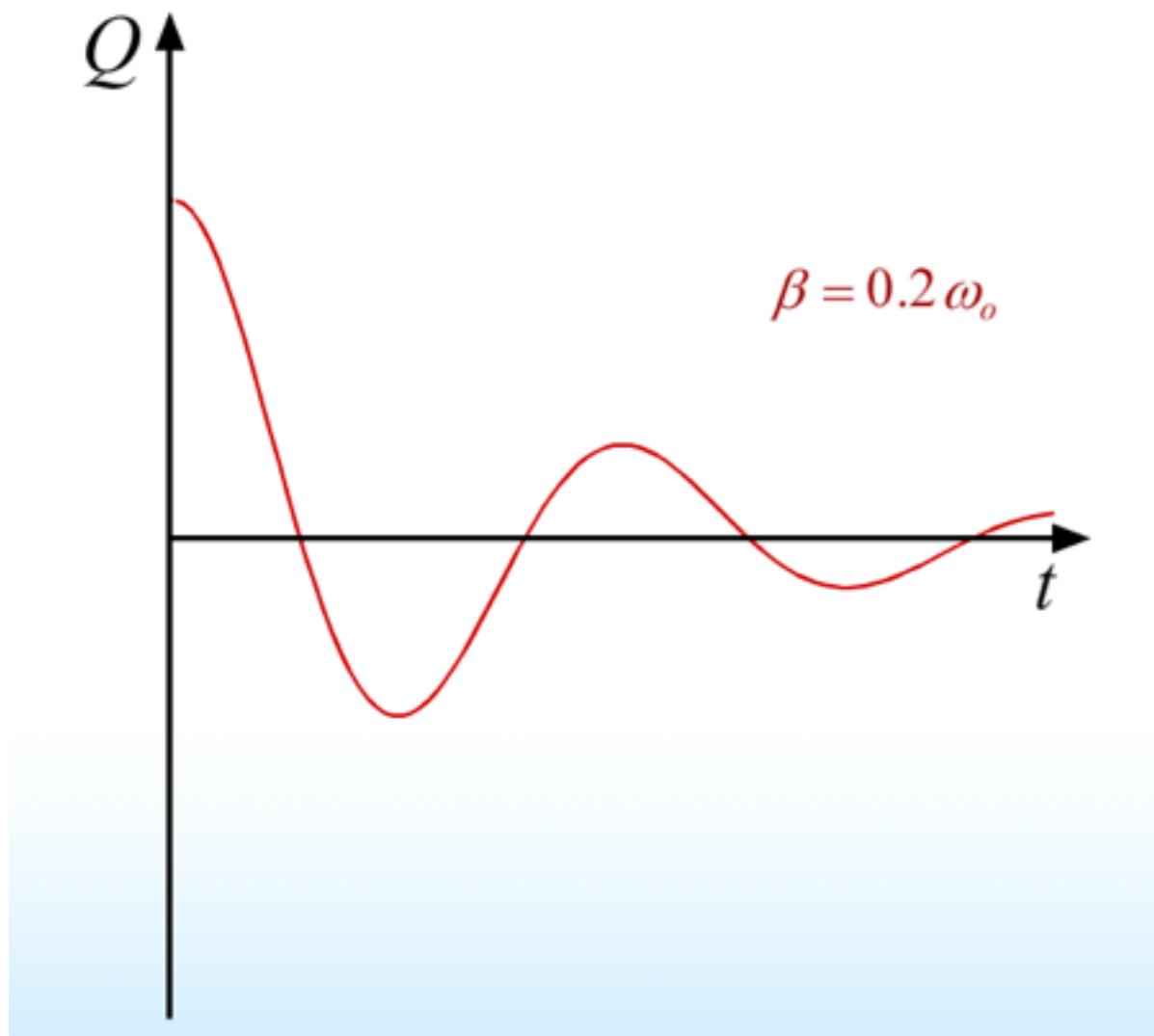


- Oscillations decay due to energy loss in the resistor!

AC circuits

Generators

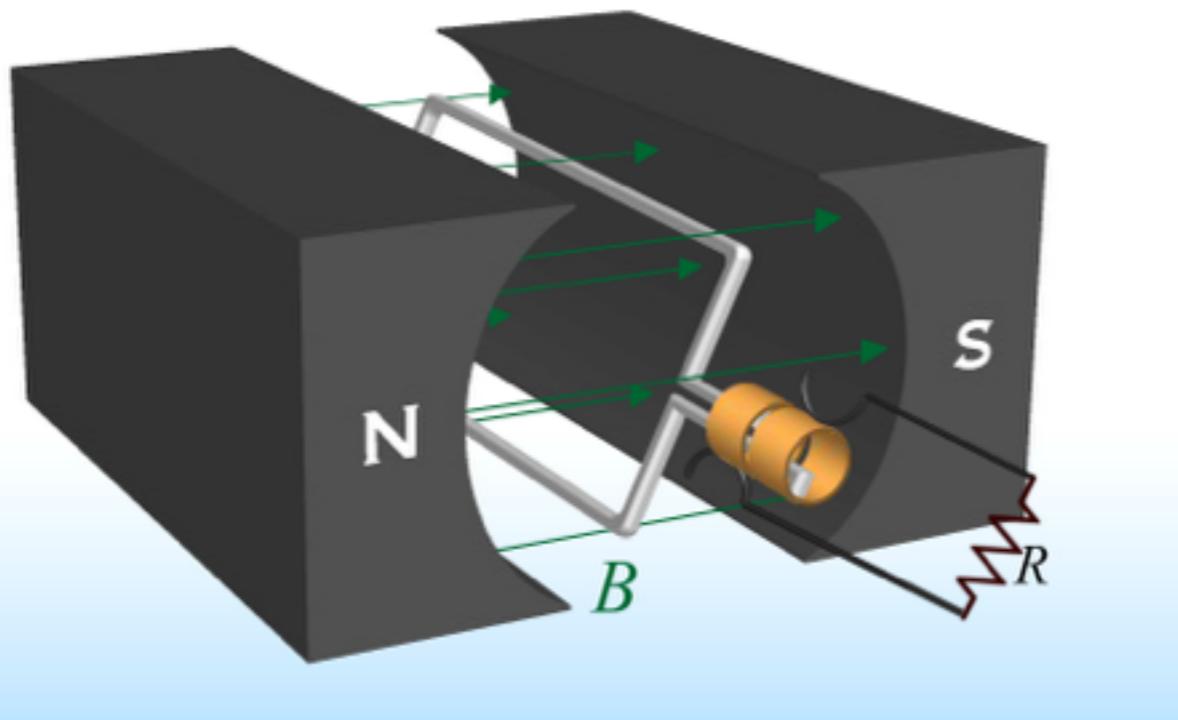
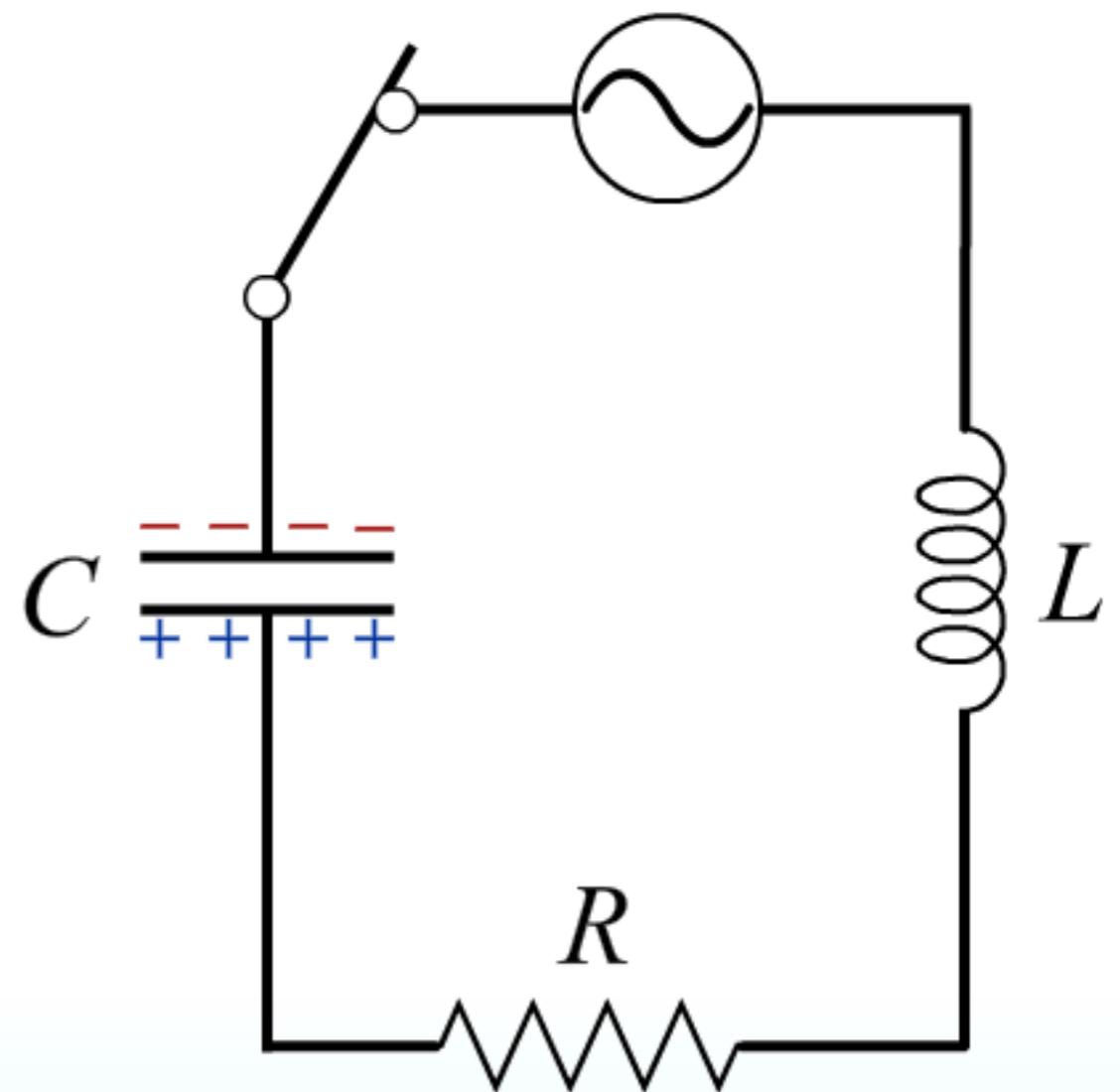
$$\mathcal{E}(t) = \mathcal{E}_{\max} \sin \omega t$$



Kircchoff Voltage Law (KVL):

Phasors


- No one uses them...

$$V(t) = \mathcal{E}_{\max} \sin \omega t$$

- y-axis projection of the vector

$$\vec{V}(t) = \mathcal{E}_{\max} \cos \omega t \hat{i} + \mathcal{E}_{\max} \sin \omega t \hat{j}$$

Phasor Diagram

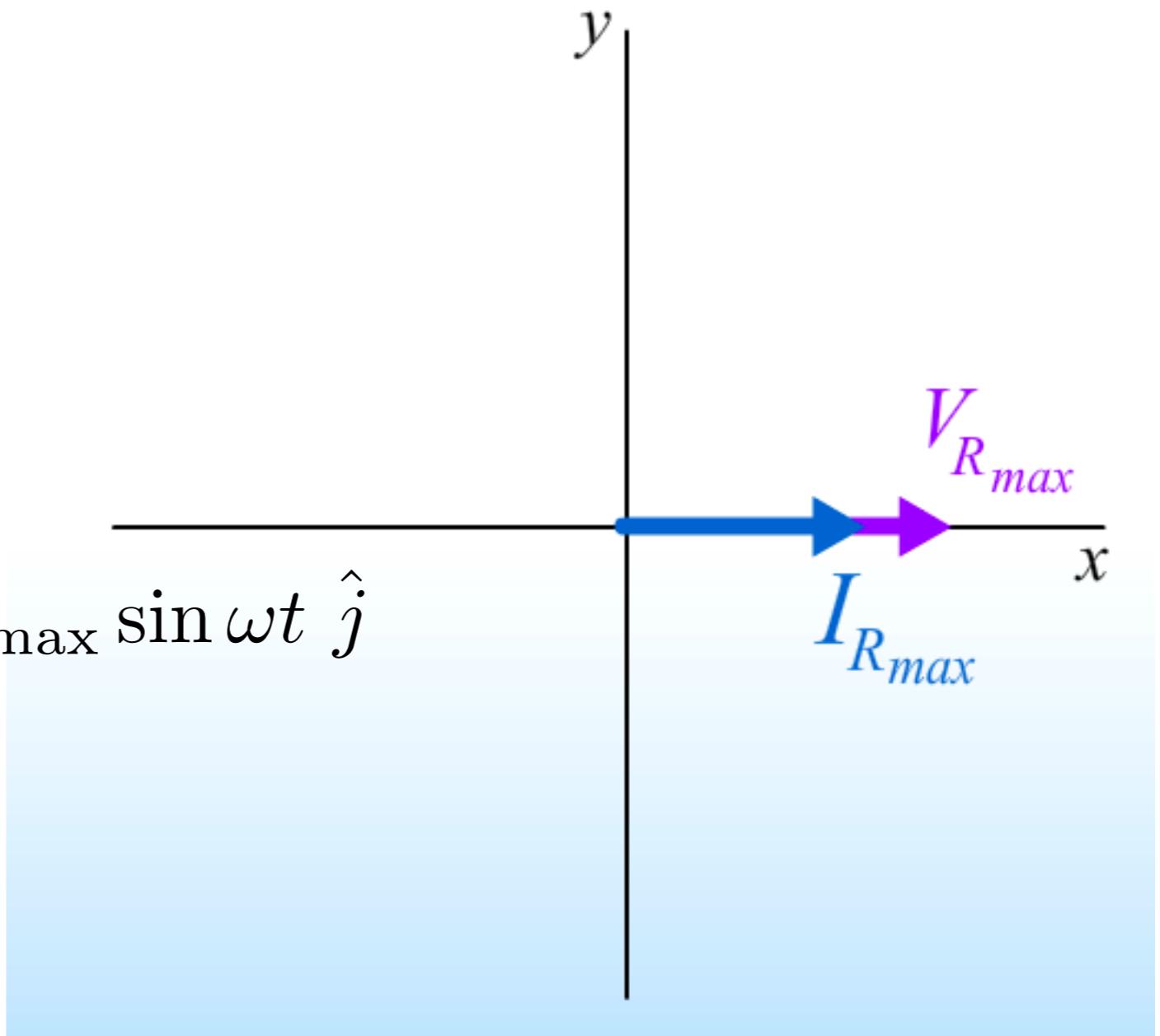


Phasors

- No one uses them...




$$V(t) = \mathcal{E}_{\max} \sin \omega t$$

- y-axis projection of the vector
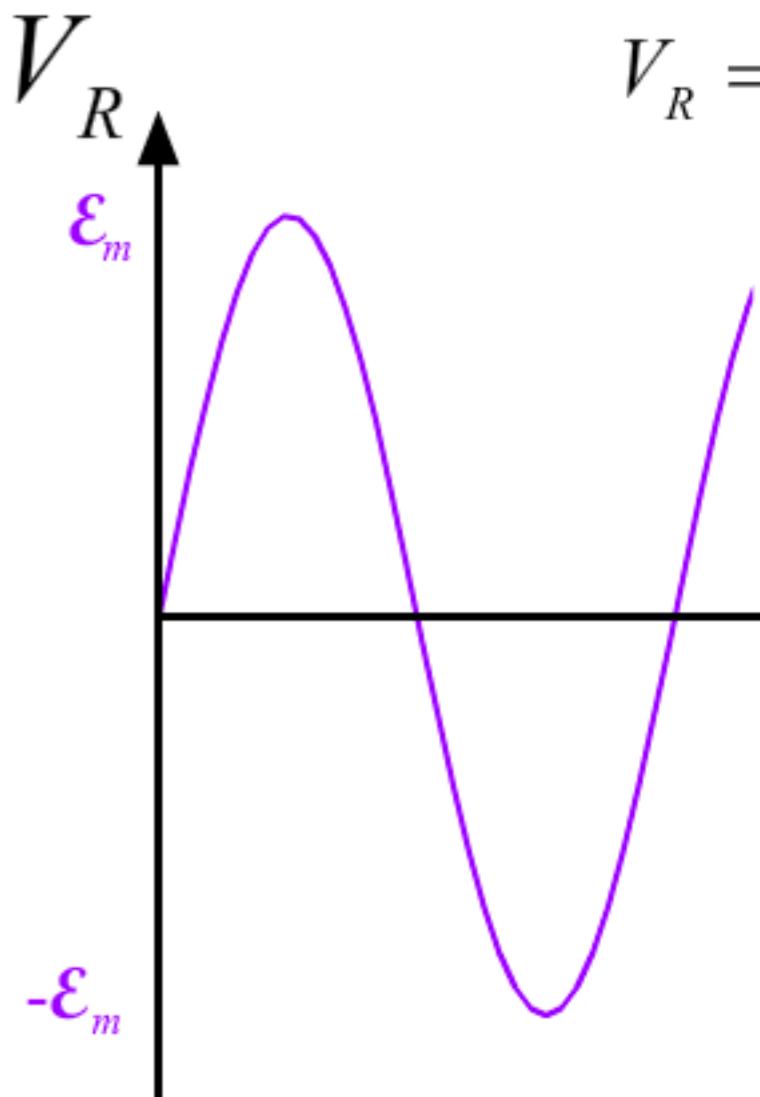
$$\vec{V}(t) = \mathcal{E}_{\max} \cos \omega t \hat{i} + \mathcal{E}_{\max} \sin \omega t \hat{j}$$



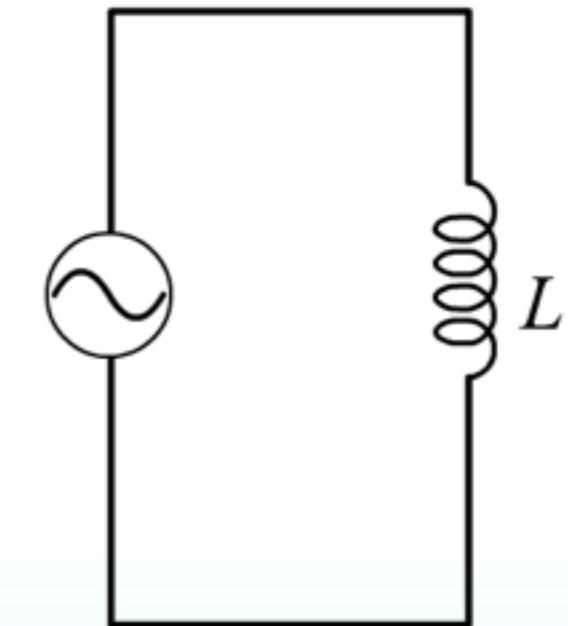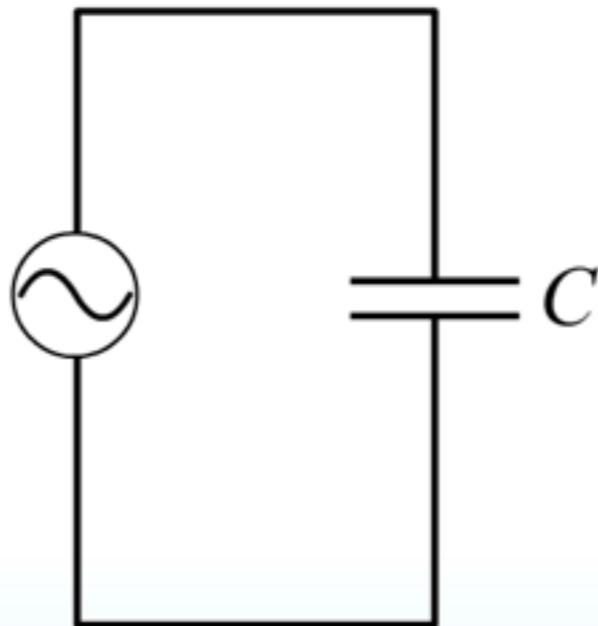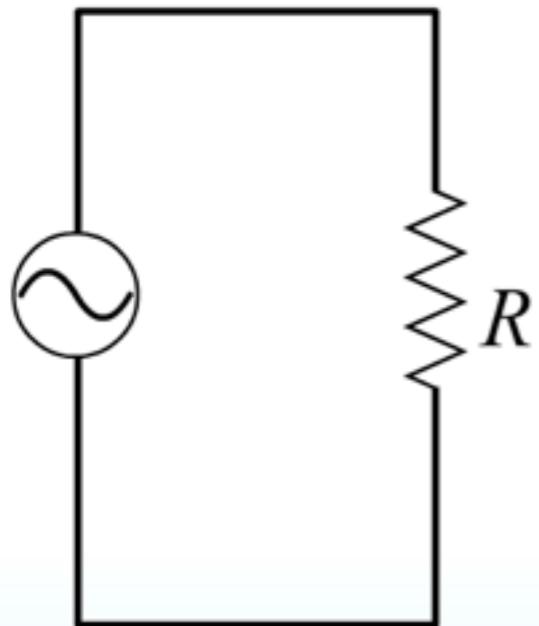Overview of circuit components: Reactance



$$V = IR$$

$$I_R = \frac{\mathcal{E}_{\max}}{R} \sin \omega t$$

$$X_R = R$$

$$V = Q/C$$

$$I_C = \frac{\mathcal{E}_{\max}}{X_C} \cos \omega t$$

$$X_C = \frac{1}{\omega C}$$


$$V = L \frac{dI}{dt}$$

$$I_L = -\frac{\mathcal{E}_{\max}}{X_L} \cos \omega t$$


$$X_L = \omega L$$

Resistor

Phasor Diagram

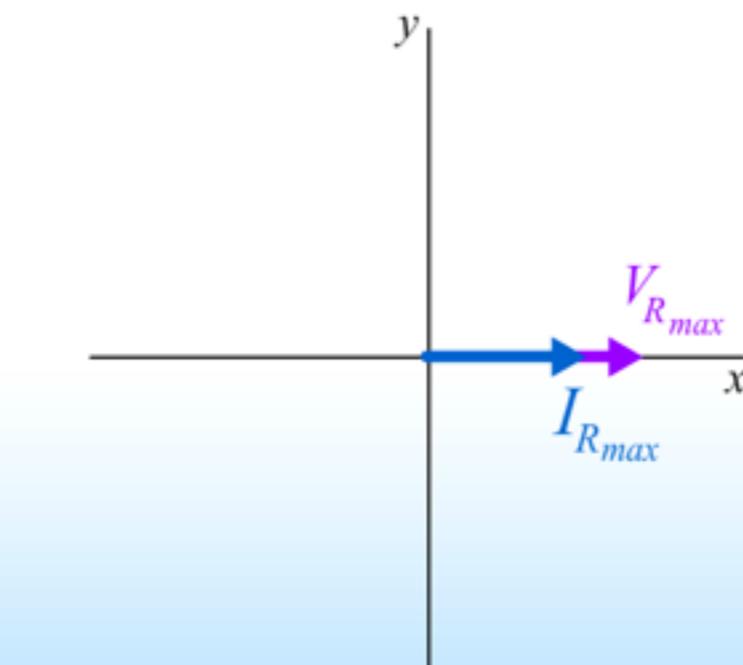

$V_R(t)$ is in Phase with $I_R(t)$

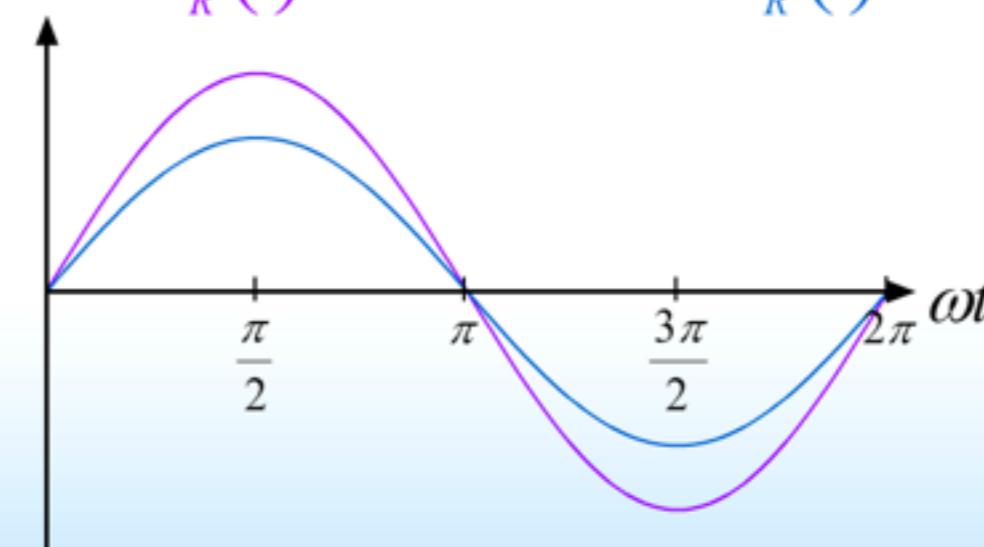


$$I_R = \frac{\mathcal{E}_{\max}}{R} \sin \omega t$$


$$\vec{I}_R(t) = \frac{\mathcal{E}_{\max}}{X_R} \left[\cos(\omega t) \hat{i} + \sin(\omega t) \hat{j} \right]$$

Capacitor

Phasor Diagram

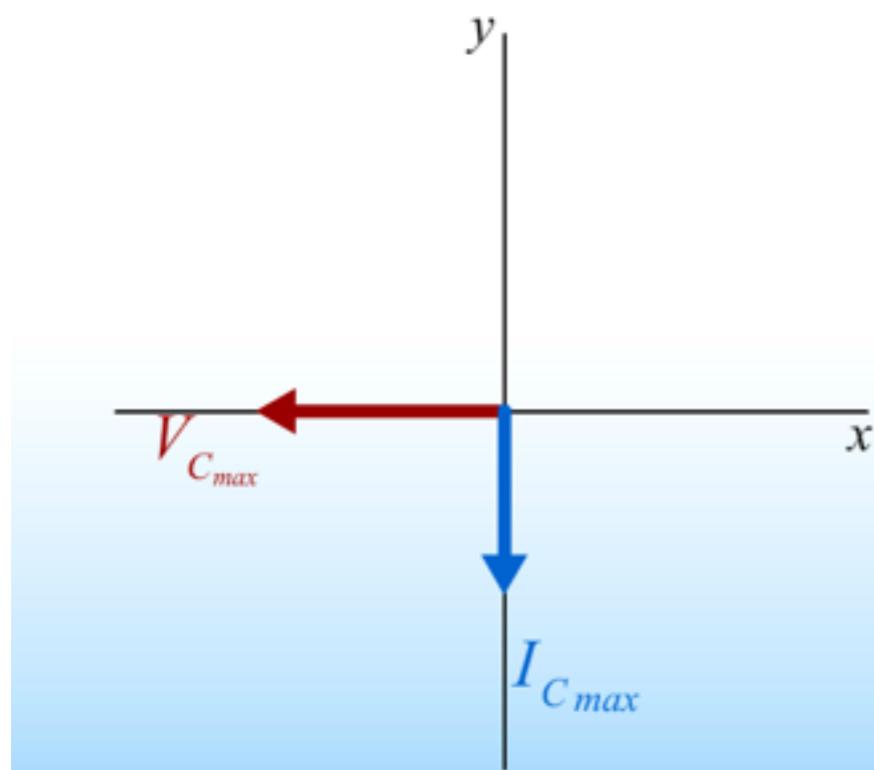

$V_C(t)$ lags $I_C(t)$ by 90°


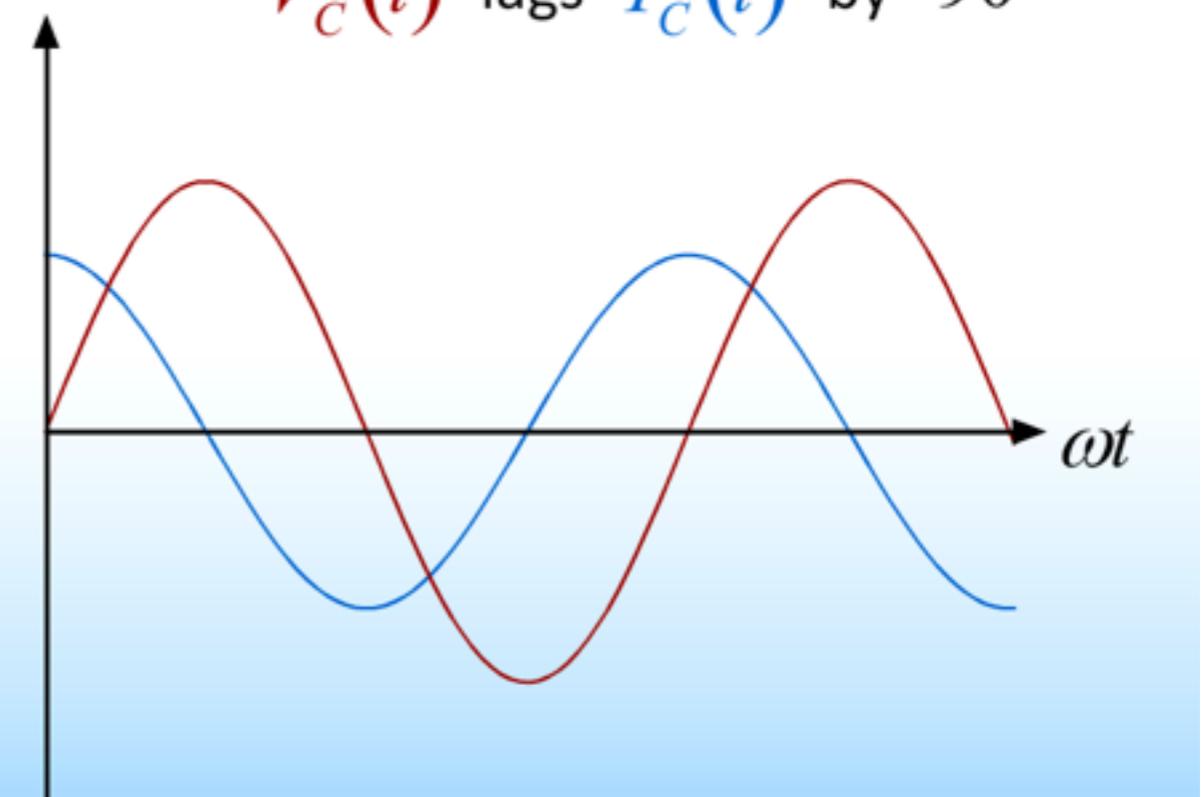


$$I_C = \frac{\mathcal{E}_{\max}}{X_C} \cos \omega t$$

$$\vec{I}_C(t) = \frac{\mathcal{E}_{\max}}{X_C} \left[\cos\left(\omega t + \frac{\pi}{2}\right) \hat{i} + \sin\left(\omega t + \frac{\pi}{2}\right) \hat{j} \right]$$

Inductor

Phasor Diagram

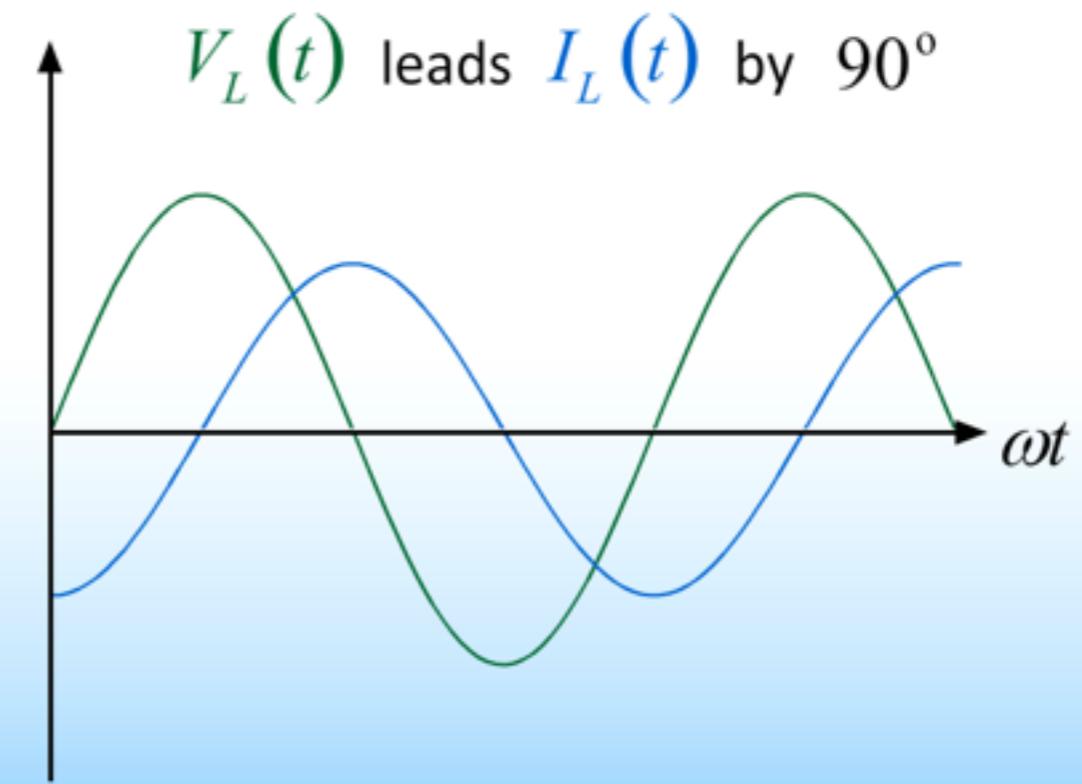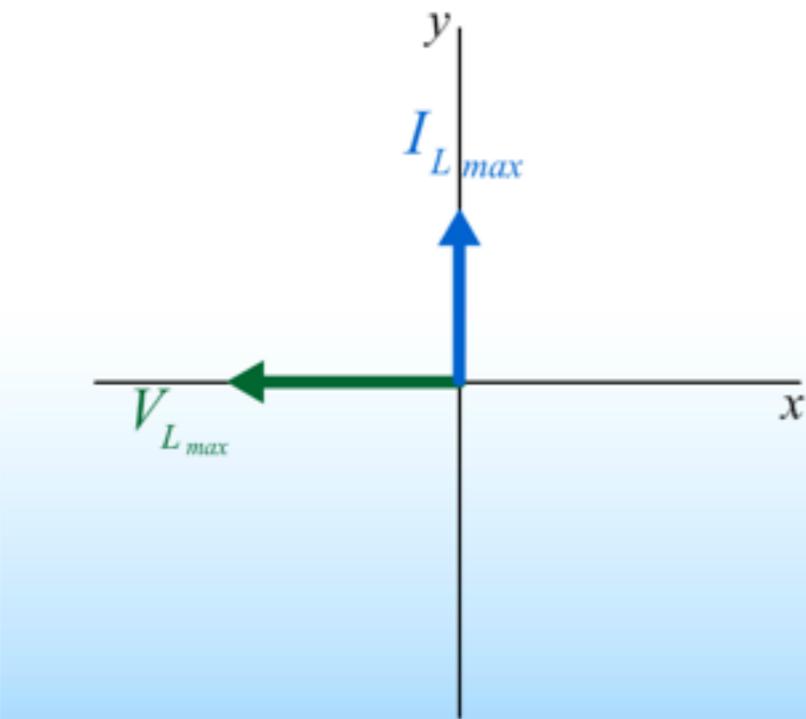

$$I_L = \frac{\mathcal{E}_{\max}}{X_L} \cos \omega t$$

$$\vec{I}_L(t) = \frac{\mathcal{E}_{\max}}{X_L} \left[\cos\left(\omega t - \frac{\pi}{2}\right) \hat{i} + \sin\left(\omega t - \frac{\pi}{2}\right) \hat{j} \right]$$

Putting it all together...

Current

$$I = I_m \sin(\omega t - \phi)$$


KVR

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} - \mathcal{E}_m \sin(\omega t) = 0$$

- Unknowns:

$$I_{\max}, \quad \phi$$

$$\mathcal{E}_m \sin(\omega t)$$

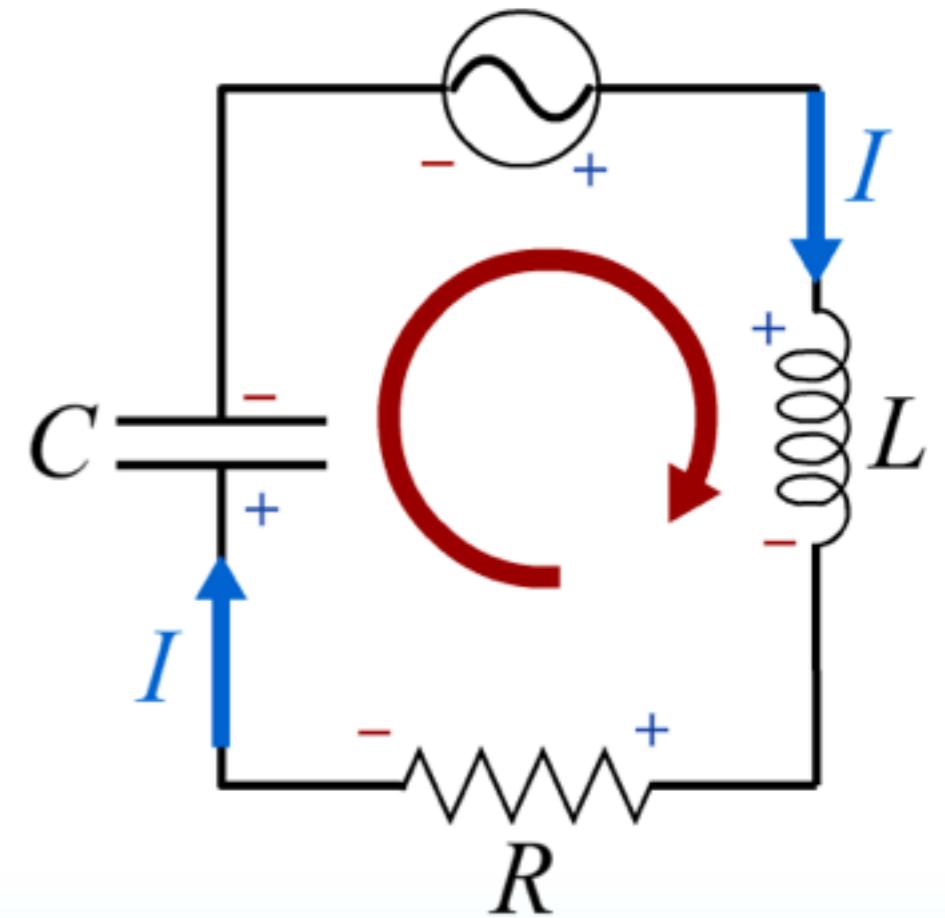

Putting it all together...

- Unknowns:
 I_{\max}, ϕ
- Choose unknowns such that:

$$\vec{V}_R + \vec{V}_C + \vec{V}_L = \vec{\mathcal{E}}$$

- Result:
$$\tan \phi = \frac{X_L - X_C}{R}$$
$$I_{\max} = \frac{\mathcal{E}_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Phasor Diagram

