
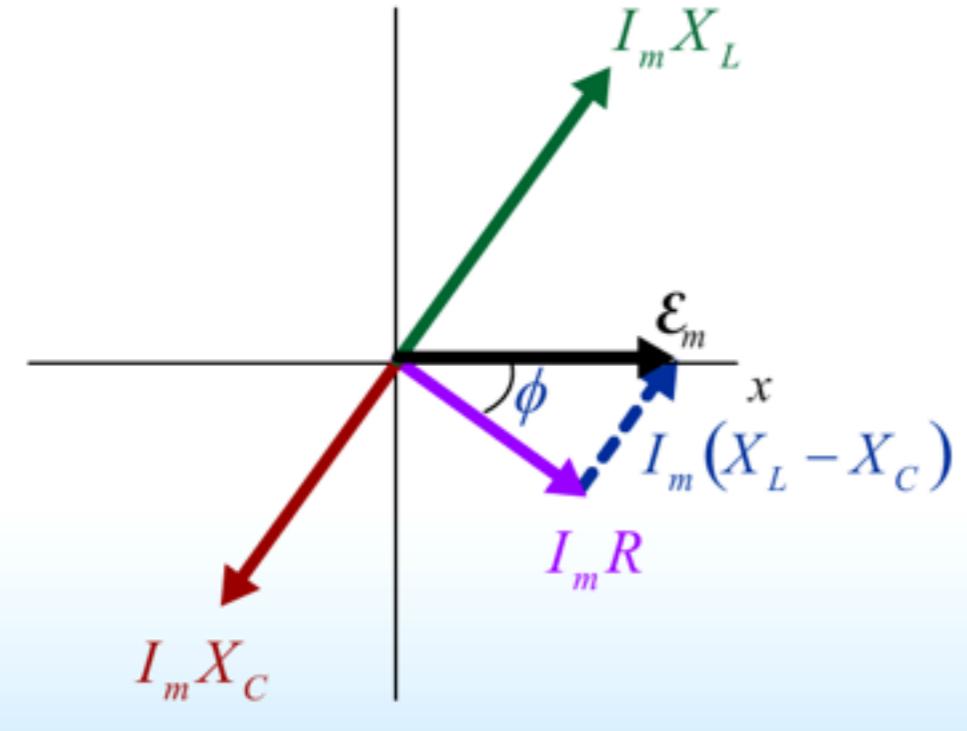


Resonance & Transformers

Lecture 26

Review: LRC driven circuits

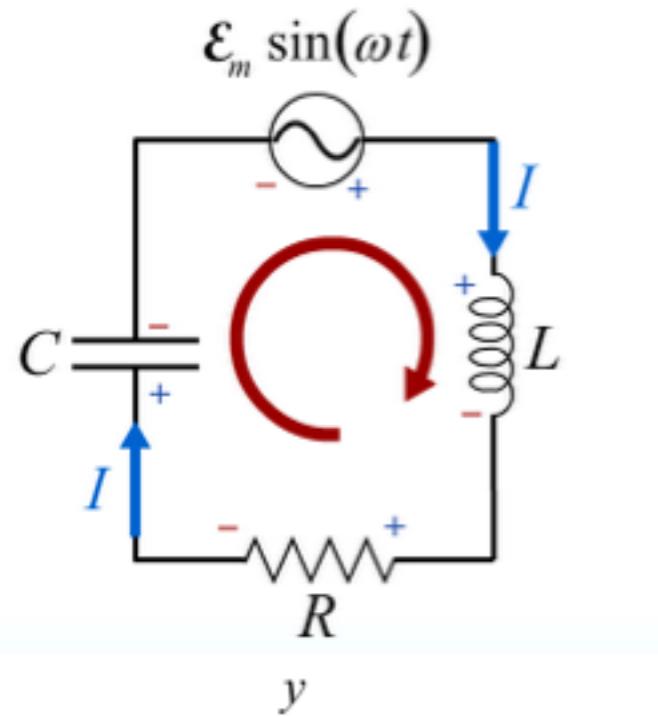

- Unknowns:
 I_{\max}, ϕ
- Choose unknowns such that:

$$\vec{V}_R + \vec{V}_C + \vec{V}_L = \vec{\mathcal{E}}$$

- Result:


$$\tan \phi = \frac{X_L - X_C}{R}$$

$$I_{\max} = \frac{\mathcal{E}_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Impedance

- Define Impedance:

Phasor Diagram

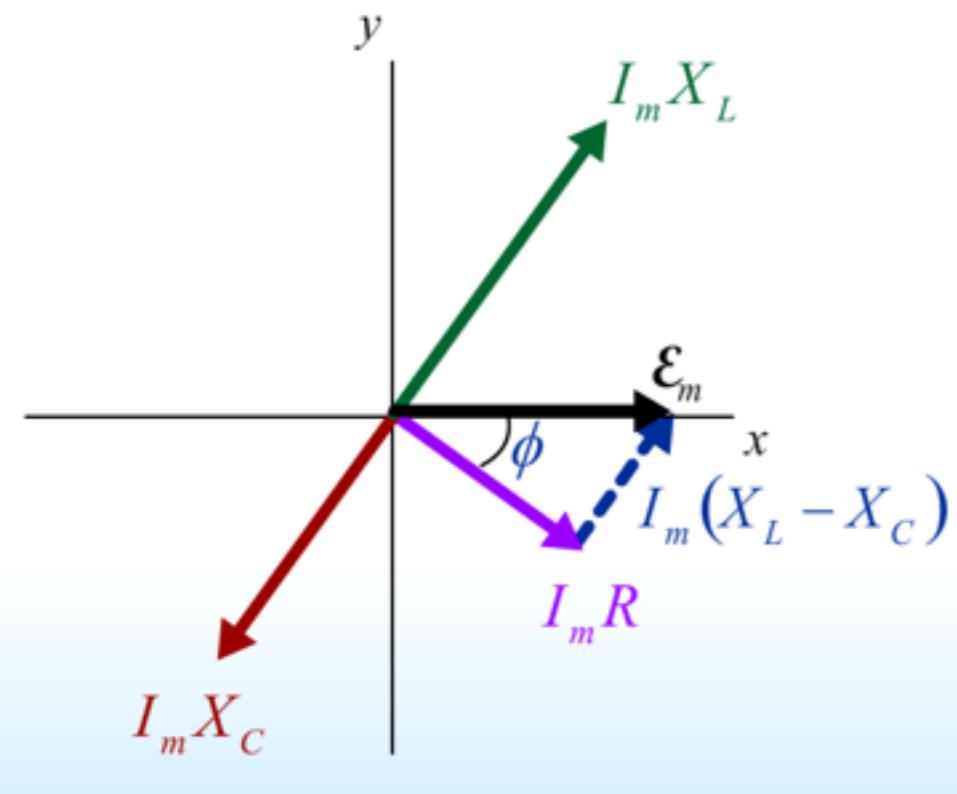

$$I_{\max} = \frac{\mathcal{E}_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$I_{\max} = \frac{\mathcal{E}_{\max}}{Z}$$

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance

- Maximize current (power):


- Minimize impedance:

$$I_{\max} = \frac{\mathcal{E}_{\max}}{Z}$$


$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = X_C$$
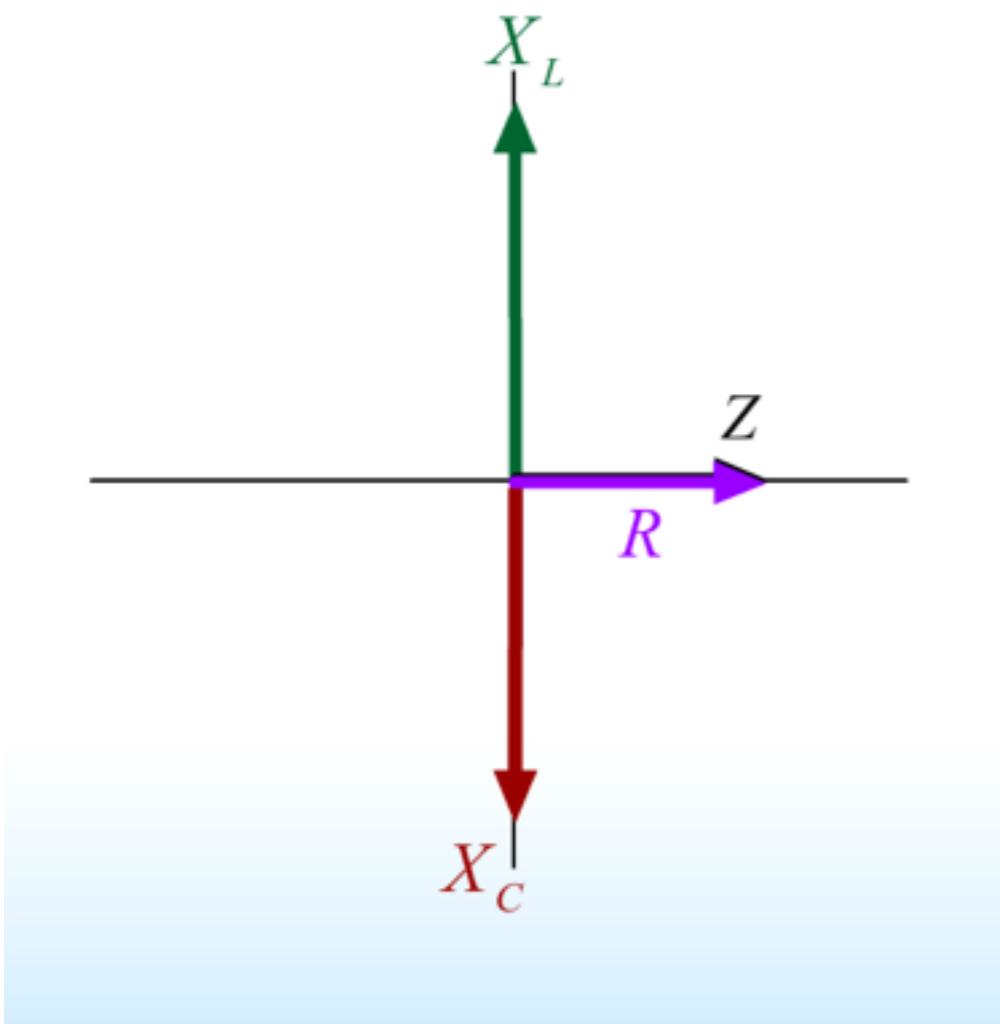
$$\omega = \omega_0 \equiv \frac{1}{\sqrt{LC}}$$



Resonance

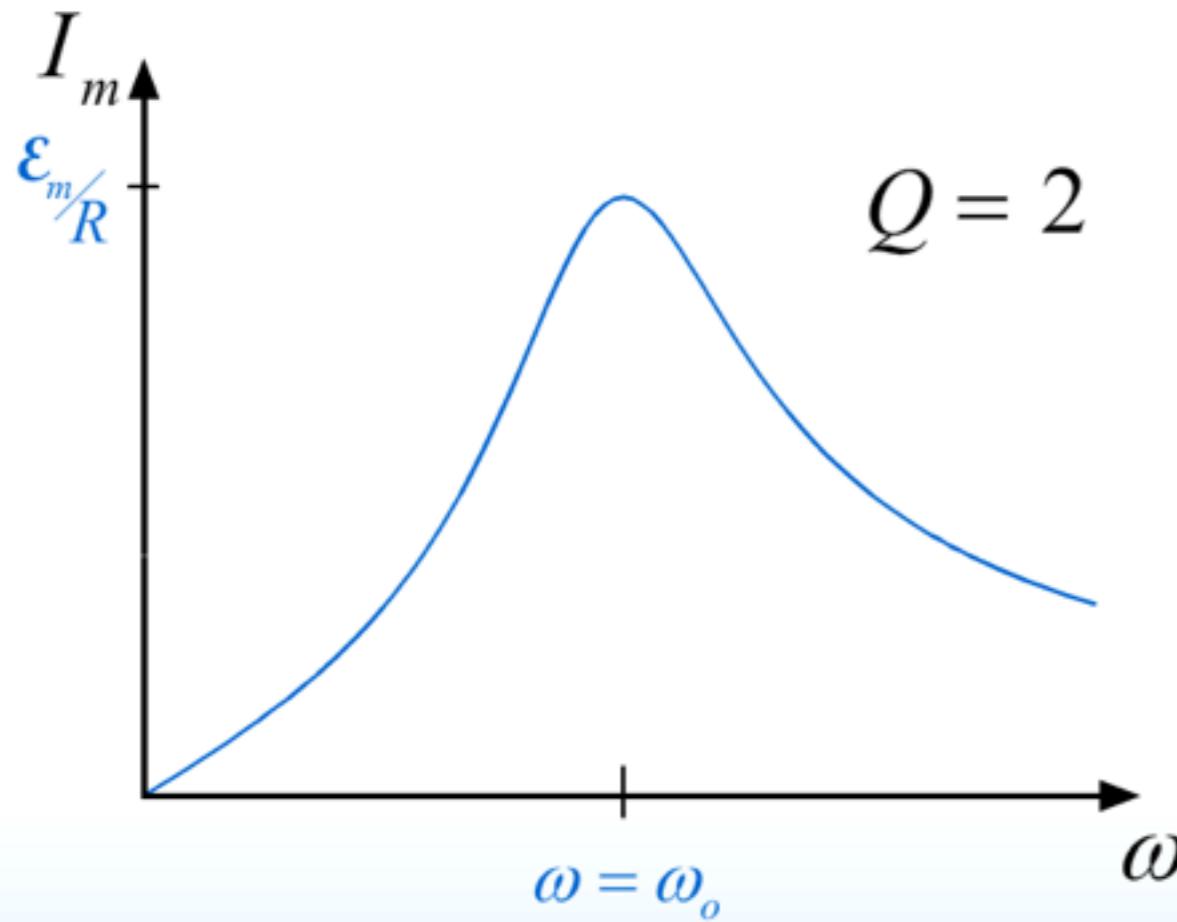


$$x \equiv \frac{\omega}{\omega_o} \quad Q^2 \equiv \frac{L}{R^2 C}$$

$$I_m = \frac{\mathcal{E}_m}{R} \frac{1}{\sqrt{1 + Q^2 \frac{(x^2 - 1)^2}{x^2}}}$$

Resonance

Average Power per Cycle
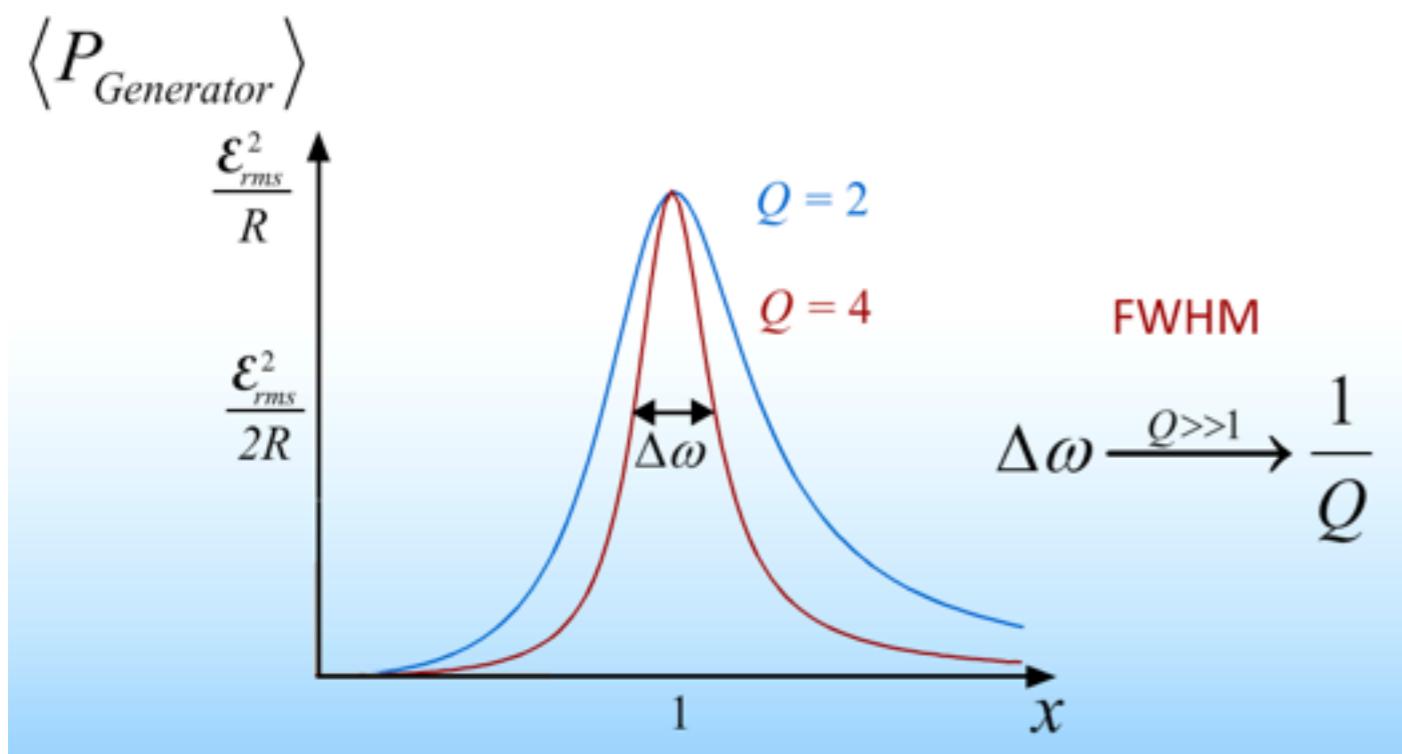
$$\langle P_{Generator} \rangle = \frac{\mathcal{E}_{rms}^2}{R} \frac{x^2}{x^2 + Q^2(x^2 - 1)^2}$$




- Root mean square values

$$\mathcal{E}_{rms} = \frac{1}{\sqrt{2}} \mathcal{E}_{max}$$


$$I_{rms} = \frac{1}{\sqrt{2}} I_{max}$$

- Quality controls the width of the peak...

AM Radio

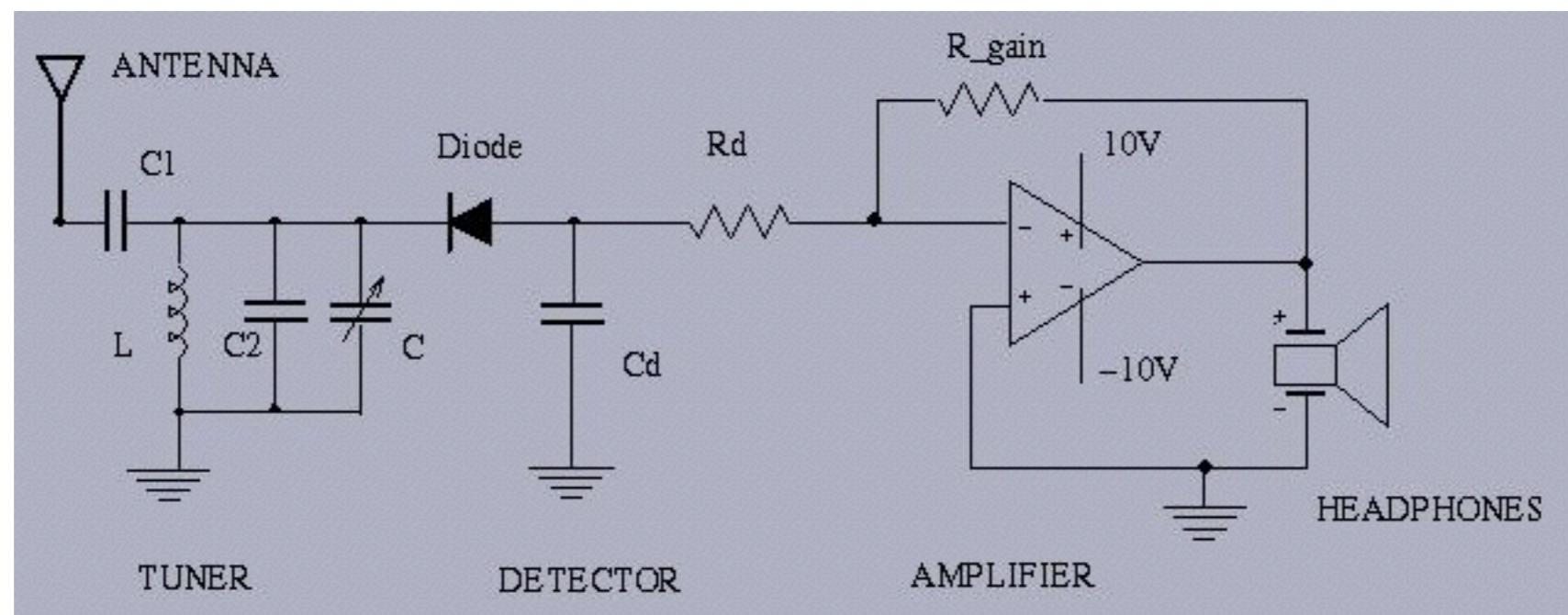


Transformers

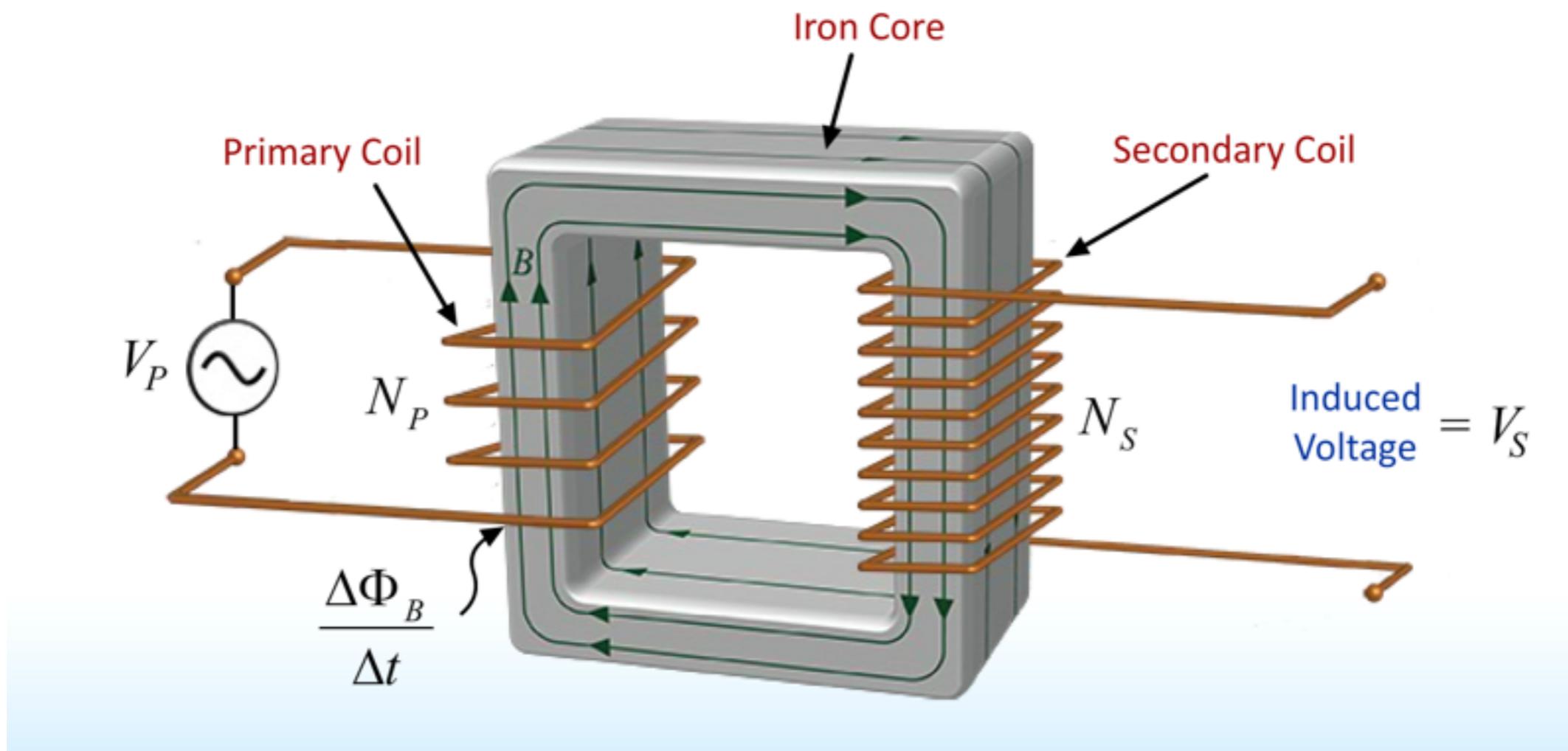

- Ideal: Ignore internal resistance...

Transformers

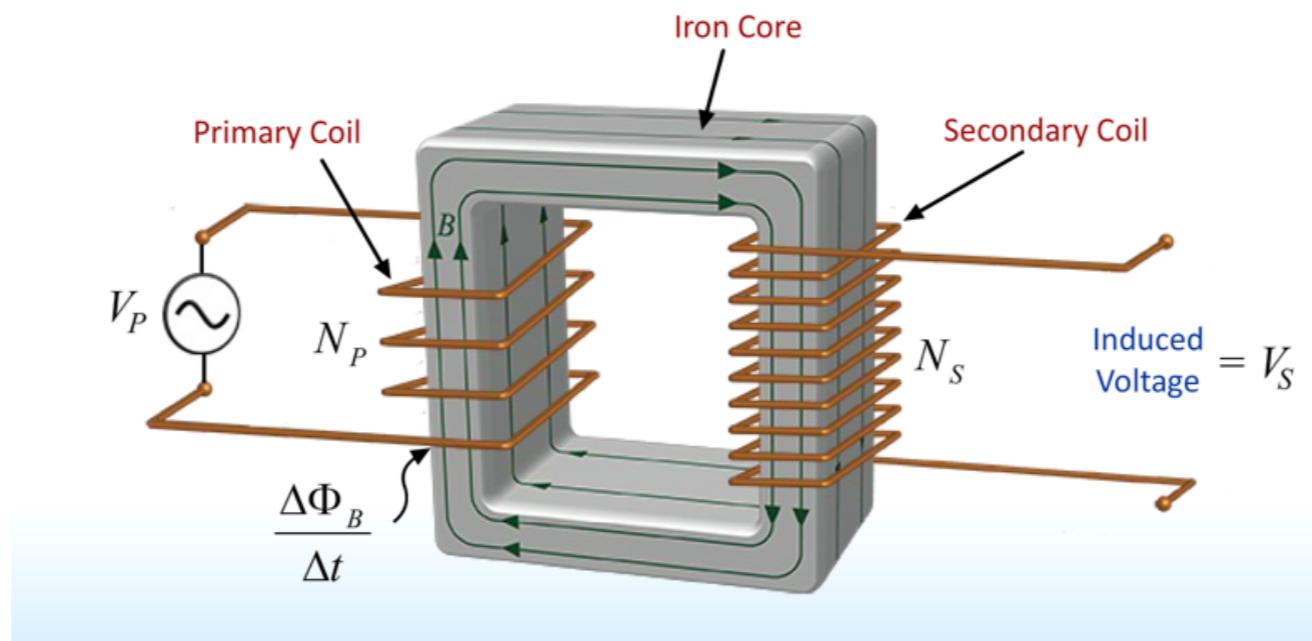


- Complicated... but:

$$\Phi_B^{(P)}(t) = N_P \Phi_B^0(t)$$

$$\Phi_B^{(S)}(t) = N_S \Phi_B^0(t)$$

- Conservation of energy: $P = IV$


Key Transformer Eqns

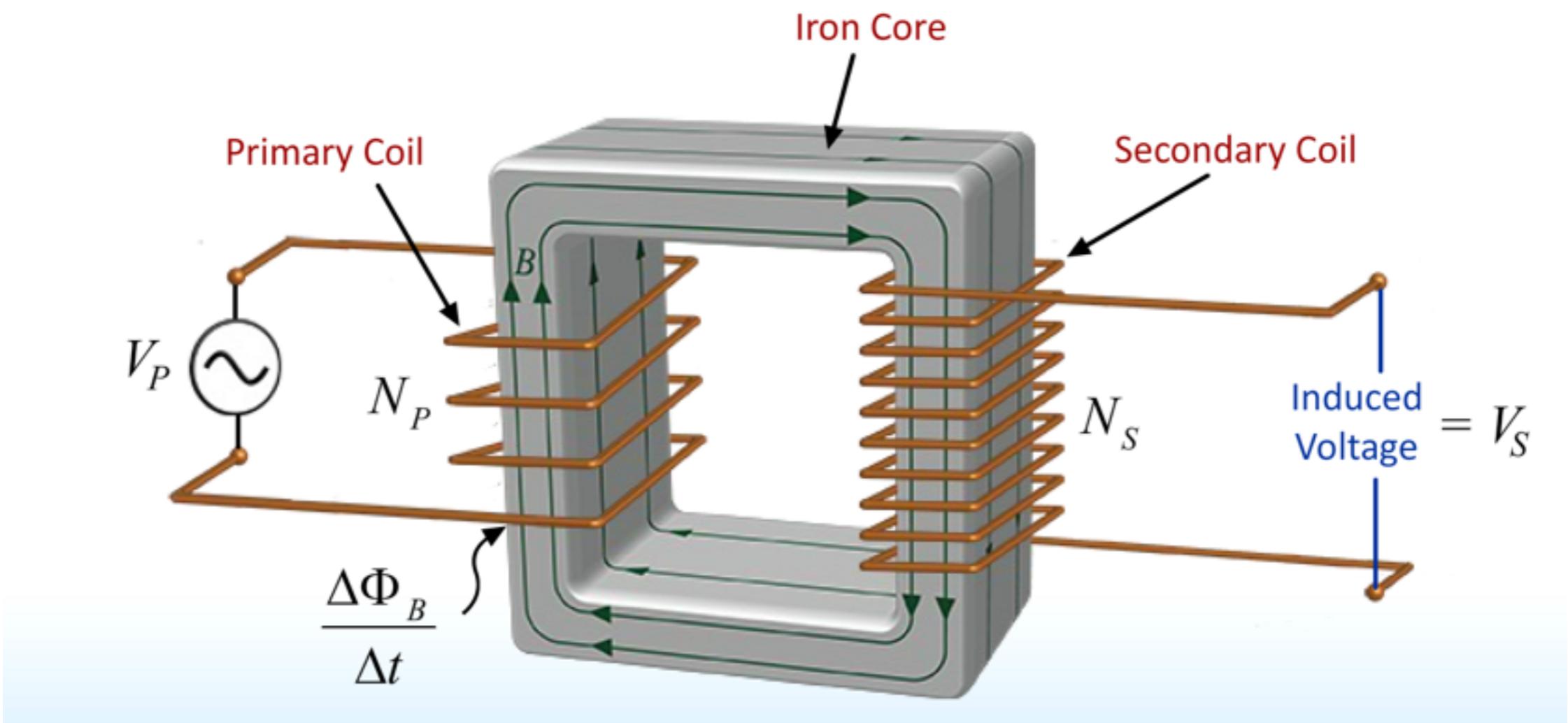


$$V_s = \frac{N_s}{N_p} V_p$$

$$I_s = \frac{N_p}{N_s} I_p$$

Tesla Coil

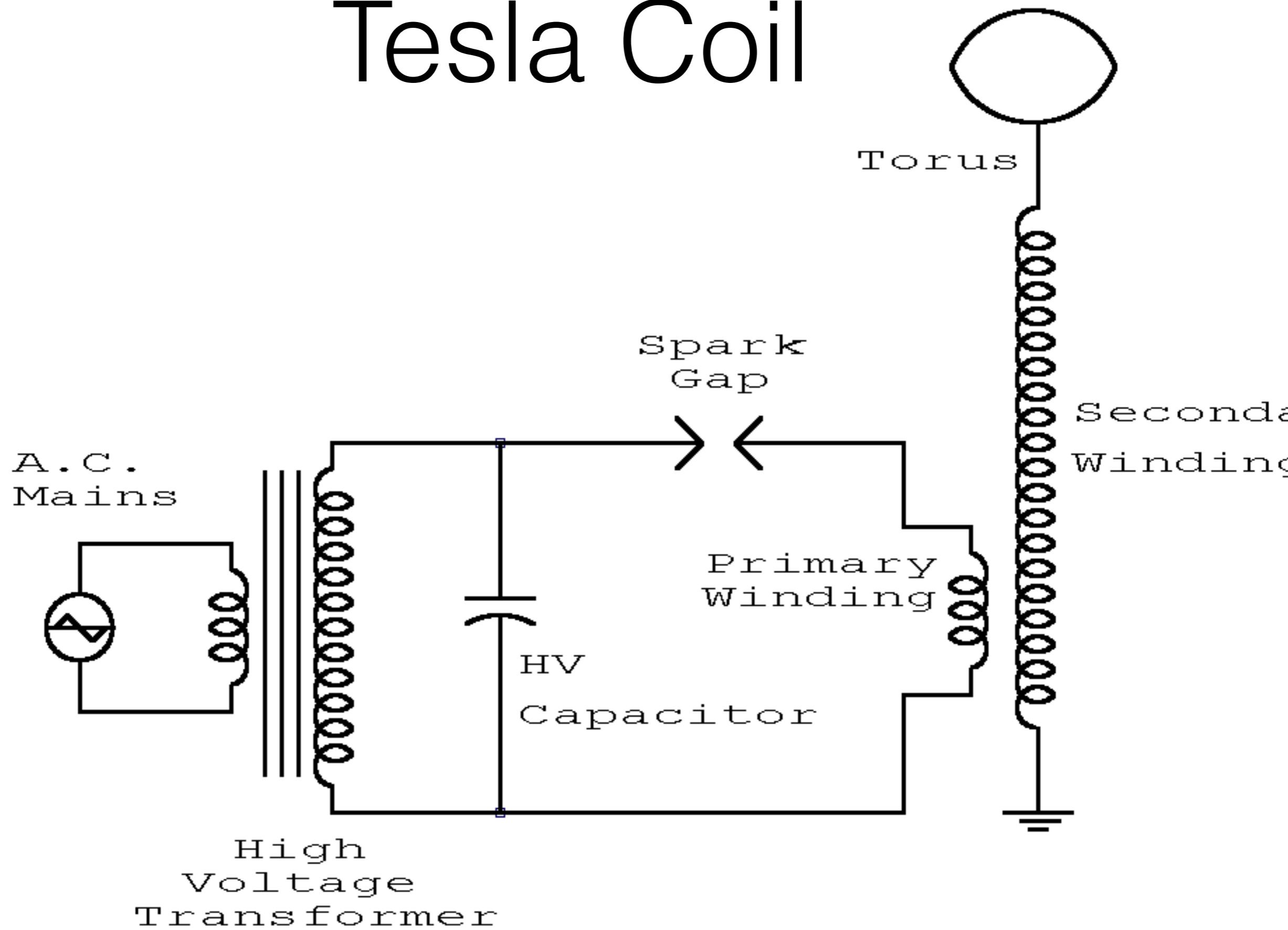

Power Transmission

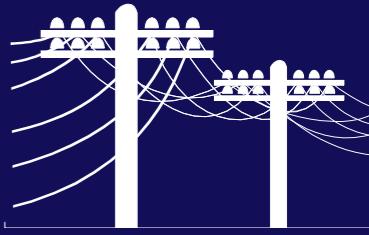

- Why use high-voltage to transport electricity ?
 - At home: 120V AC at 60Hz.
 - Transmission typically ~500 kV)
 - Transformers raise voltage for transmission; lower for use
- Why do we do that?
 - Calculate ohmic losses in the transmission lines:
 - Define **efficiency** of transmission:

$$\epsilon_{ff} = \frac{P_{out}}{P_{in}} = \frac{iV_{in} - i^2R}{iV_{in}} = 1 - \frac{iR}{V_{in}} \left(\frac{V_{in}}{V_{in}} \right) = 1 - \frac{P_{in}R}{V_{in}^2}$$

Keep R small

Make V_{in} big