

## LC Circuits:

(1)

$$\frac{Q(t)}{C} + L \frac{d^2 Q}{dt^2} = 0$$

$$0 = \left[ \left( \frac{d}{dt} \right)^2 + \frac{1}{LC} \right] Q(t)$$

Solutions:  $A \sin \omega t + B \cos \omega t$

$$\left[ -\omega^2 + \frac{1}{LC} \right] Q(t) = 0$$

$$\omega = \frac{1}{\sqrt{LC}} //$$


## AC Circuits:

AC voltage source:  $\mathcal{E}(t) = \mathcal{E}_{\max} \sin \omega t$ .

$$\vec{V}(t) = \mathcal{E}_{\max} \left[ \sin \omega t \hat{j} + \cos \omega t \hat{i} \right]$$

$$V(t) = \hat{j} \cdot \vec{V}(t).$$

Resistor:

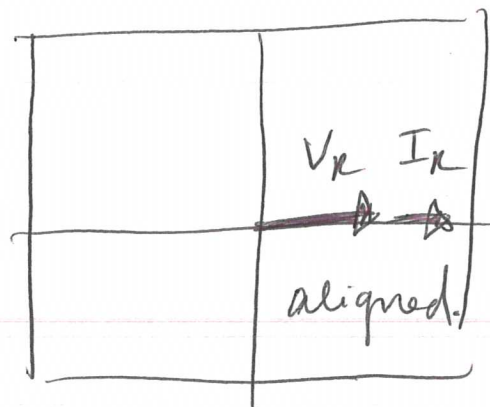

$$I_R = \frac{V_R}{R} =$$

$$\vec{I}_R = \frac{\vec{V}_R}{R} = \frac{E_{max}}{R} [\sin \omega t \hat{j} + \cos \omega t \hat{i}]$$


Define reactance:  $X_R \equiv R.$

Capacitor:

$$Q_c = CV_c \rightarrow I_c = C \frac{dV_c}{dt}$$

$$\begin{aligned} \vec{I}_c &= \omega C E_{max} [\cos \omega t \hat{j} - \sin \omega t \hat{i}] \\ &= \frac{E_{max}}{X_c} \left[ \sin(\omega t + \frac{\pi}{2}) \hat{j} + \cos(\omega t + \frac{\pi}{2}) \hat{i} \right] \end{aligned}$$

$$X_c \equiv \frac{1}{\omega C}$$

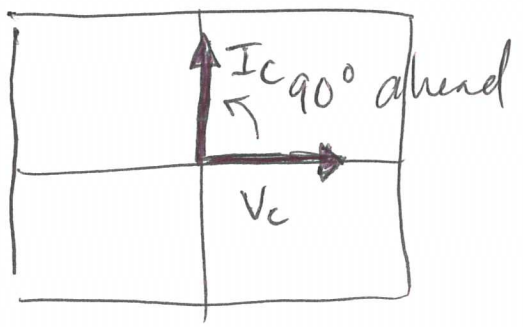

$$\begin{aligned} \sin(\alpha + \beta) &= \sin \alpha \cos \beta + \sin \beta \cos \alpha \\ \cos(\alpha + \beta) &= \cos \alpha \cos \beta - \sin \alpha \sin \beta \end{aligned}$$

## Inductor :


(3)

$$V_L = L \frac{dI_L}{dt}$$

$$I_L = \frac{1}{L} \int dt V_L$$

$$= + \frac{E_{\max}}{L\omega} \left[ -\cos \omega t \hat{j} + \sin \omega t \hat{i} \right]$$
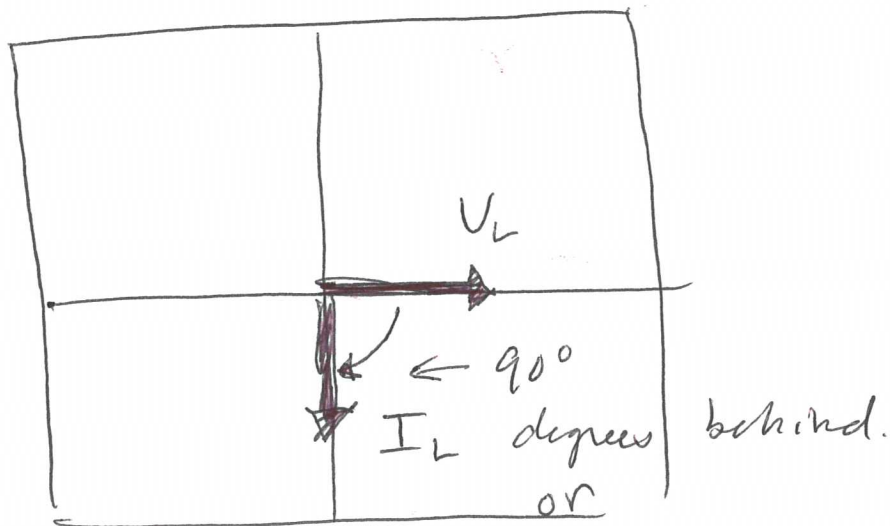
$$= \frac{E_{\max}}{X_L} \left[ \cos \left( \omega t - \frac{\pi}{2} \right) \hat{j} + \sin \left( \omega t - \frac{\pi}{2} \right) \hat{i} \right]$$




$V_L$  is  $90^\circ$  ahead of  $I_L$ .

Putting it all together:

(4)

$$\vec{V}_R + \vec{V}_C + \vec{V}_L = \vec{\mathcal{E}}$$

unknown:  $\vec{I}$ :

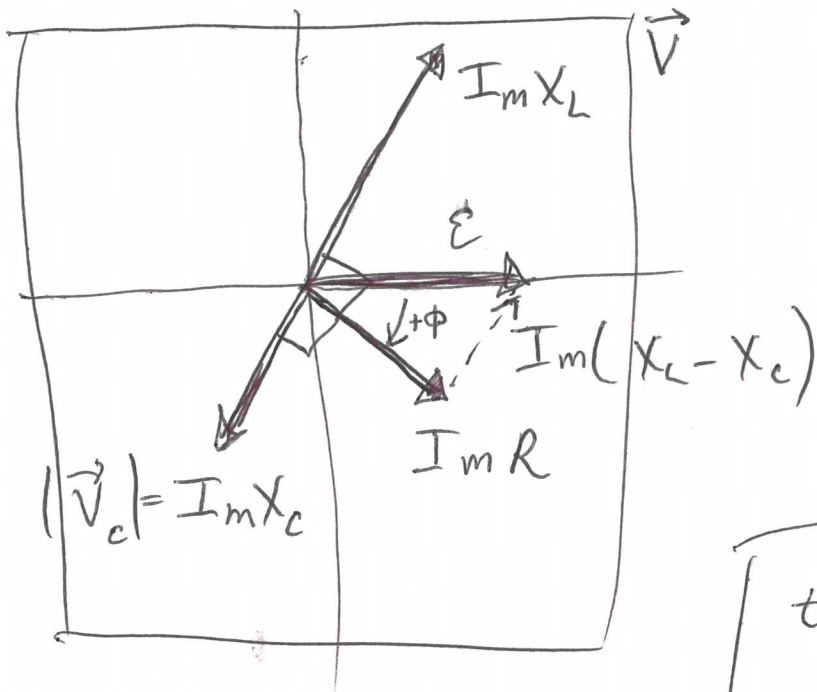

$I_{max} + \phi$   
↑  
phase.

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\mathcal{E}_{max}^2 = (I_{max} R)^2 + I_{max}^2 (X_L - X_C)^2$$

$$I_{max} = \frac{\mathcal{E}_{max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$