# Resonance & Transformers

Lecture 27

#### Announcements

- Reading for Wednesday: 30-1 to 30-2
- Exam pickup: Today
- HW: dropped last three problems
- Instead: Please do course evaluations!

#### Review: LRC driven circuits

• Unknowns:



$$I_{\max}, \phi$$

Choose unknowns such that:

$$\vec{V}_R + \vec{V}_C + \vec{V}_L = \vec{\mathcal{E}}$$

• Result:



#### Impedance

• Define Impedance:



#### Resonance

• Maximize current (power):



#### Resonance



#### Resonance



 Root mean square values

$$\mathcal{E}_{\rm rms} = \frac{1}{\sqrt{2}} \mathcal{E}_{\rm max}$$
$$I_{\rm rms} = \frac{1}{\sqrt{2}} I_{\rm max}$$

• Quality controls the width of the peak...

#### AM Radio



### Transformers



• Ideal: Ignore internal resistance...

#### Transformers



• Complicated... but:

$$\Phi_B^{(P)}(t) = N_P \Phi_B^0(t)$$
$$\Phi_B^{(S)}(t) = N_S \Phi_B^0(t)$$

• Conservation of energy: P = IV

## Key Transformer Eqns



$$V_s = \frac{N_s}{N_p} V_p$$

 $I_s = \frac{N_p}{N_s} I_p$ 



#### **Power Transmission**

- Why use high-voltage to transport electricity ?
  - At home: 120V AC at 60Hz.
  - Transmission typically ~500 kV)
  - Transformers raise voltage for transmission; lower for use
- Why do we do that?
  - Calculate ohmic losses in the transmission lines:
  - Define efficiency of transmission:

