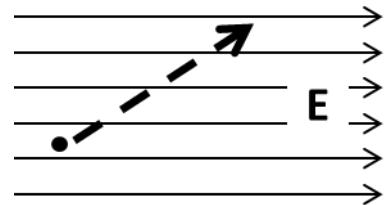


1. (4 pts.) Charges  $Q$  and  $q$  ( $Q > q$ ), separated by a distance  $d$ , produce a potential  $V_P = 0$  at point  $P$ . This means that


- A) no force is acting on a test charge placed at point  $P$ .
- B)  $Q$  and  $q$  must have the same sign.
- C) the electric field must be zero at point  $P$ .
- D) the net work in bringing  $Q$  to distance  $d$  from  $q$  is zero.
- E) the net work needed to bring a charge from infinity to point  $P$  is zero.

2. (4 pts.) A charge of  $5.0 \mu\text{C}$  is located in a uniform electric field of intensity  $3.5 \times 10^5 \text{ N/C}$ . How much work is required to move this charge at constant speed  $50 \text{ cm}$  along a path making an angle of  $33^\circ$  with respect to the electric field direction?



- A)  $0.16 \text{ J}$
- B)  $0.27 \text{ J}$
- C)  $0.54 \text{ J}$
- D)  $0.73 \text{ J}$
- E)  $7.3 \text{ mJ}$

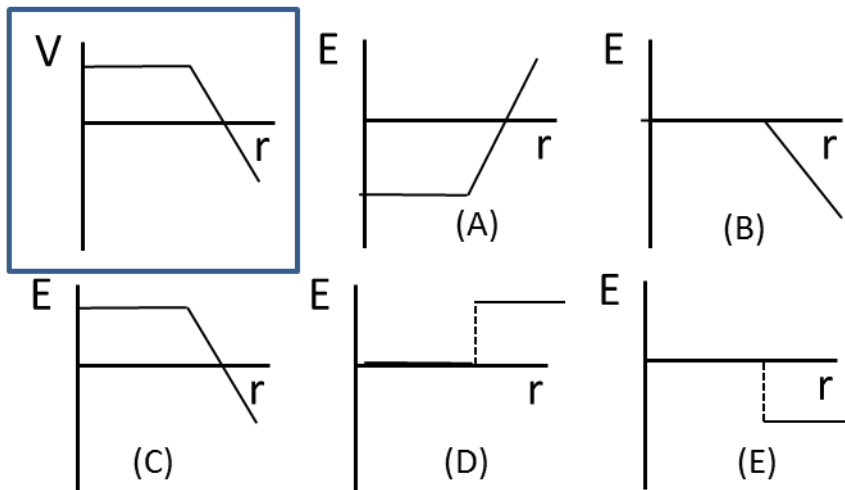
3. (4 pts.) Which graph below best shows the electric field  $E(r)$  corresponding to the potential  $V(r)$  shown in upper left graph?



Choose: (A) (B) (C) (D) (E)

4. (3 pts.) The vector that best represents the direction of the electric field at point  $x$  on the 200 V equipotential line is

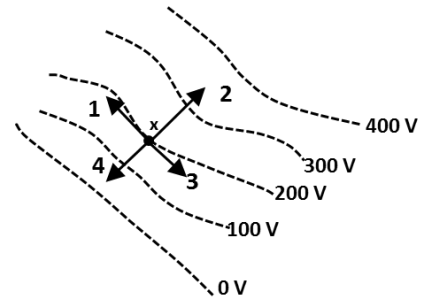- A) 1
- B) 2
- C) 3
- D) 4
- E) None of these is correct.



5. (3 pts.) Three charges are brought from infinity and placed at the corners of an equilateral triangle. Which of the following statements is true?


- A. The work required to assemble the charges is always positive.
- B. The electrostatic potential energy of the system is always positive.
- C. The electrostatic potential energy does not depend on the order the charges are placed at the corners.
- D. The work required to assemble the charges depends on which charge is placed at which corner.
- E. The electrostatic potential energy depends on which charge is placed at which corner.



6. (4 pts.) If you increase the charge on a parallel-plate capacitor from  $3 \mu\text{C}$  to  $9 \mu\text{C}$  and increase the plate separation from 1 mm to 3 mm, the energy stored in the capacitor changes by a factor of

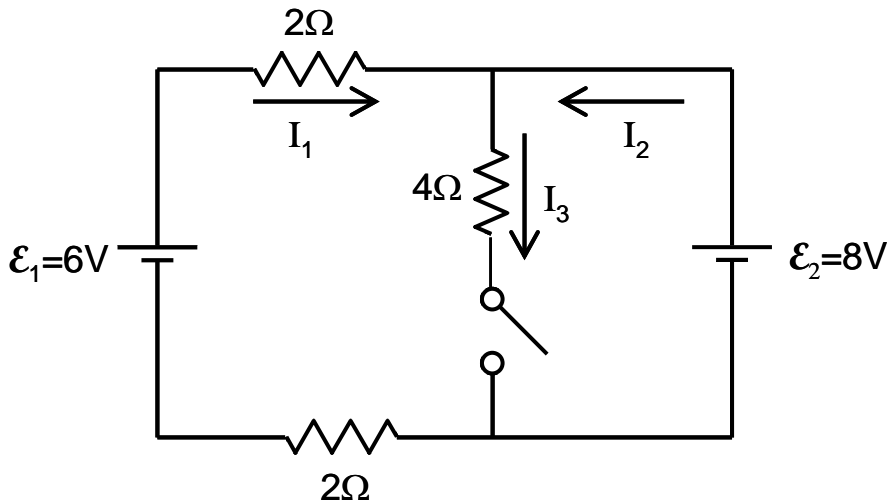- A) 27
- B) 9
- C) 8
- D) 3
- E) 1/3

The next three questions pertain to the following circuit.



7. (4 pts.) With the switch open as shown, what is the current  $I_1$ ?

- (A)  $I_1 = -7/2$  A
- (B)  $I_1 = -1/2$  A
- (C)  $I_1 = 1/2$  A
- (D)  $I_1 = 3/2$  A
- (E)  $I_1 = 7/2$  A

For the next two questions the switch is closed.

8. (4 pts.) What is the voltage across the 4 ohm resistor?

- (A) 2 V
- (B) 6 V
- (C) 7 V
- (D) 8 V
- (E) 14 V


9. (3 pts.) Which of the currents have changed in magnitude after the switch is closed?

- (A) Only  $I_3$  has changed in magnitude.
- (B) Only  $I_2$  and  $I_3$  have changed in magnitude.
- (C)  $I_1$ ,  $I_2$ , and  $I_3$  have all changed in magnitude.
- (D) No currents have changed in magnitude.

*The next three questions pertain to the following situation.*

Four capacitors are connected as shown in the figure below. The gaps between the plates of all three capacitors are filled with air ( $\kappa = 1.0$ ); the values of the capacitances are:

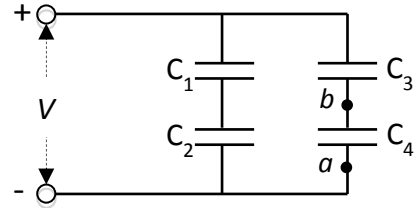- $C_1 = 2 \mu\text{F}$
- $C_2 = 3 \mu\text{F}$
- $C_3 = 8 \mu\text{F}$
- $C_4 = 6 \mu\text{F}$



A constant potential difference,  $V = 12 \text{ V}$ , is maintained across the circuit, as shown.

10. (4 pts.) What is  $C_{\text{tot}}$ , the total equivalent capacitance of the four capacitors?

- A)  $0.89 \mu\text{F}$
- B)  $3.68 \mu\text{F}$
- C)  $4.63 \mu\text{F}$
- D)  $4.75 \mu\text{F}$
- E)  $19.0 \mu\text{F}$

11. (5 pts.) What is  $V_b - V_a$ , the potential difference between points  $b$  and  $a$  (i.e., the voltage across capacitor  $C_4$ )?

- A)  $5.14 \text{ V}$
- B)  $6.00 \text{ V}$
- C)  $6.86 \text{ V}$
- D)  $9.00 \text{ V}$
- E)  $16.00 \text{ V}$

12. (3 pts.) If capacitors  $C_1$  and  $C_2$  are removed from the circuit, how will the energy stored in  $C_4$  change?

- A) Increase
- B) No change
- C) Decrease